

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

20ELD31

Third Semester M.Tech. Degree Examination, Jan./Feb. 2023 Synthesis Optimization of Digital Circuits

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. State and illustrate the different quality measures used in the optimization of the circuit used in the computer aided synthesis and optimization. (10 Marks)
- b. Write a structural representation on verilog for a 5 bit ripple carry adder using 1 bit full adder. (10 Marks)

OR

- 2 a. Bring out the difference between different levels in the synthesis task used in computer aided synthesis and optimization. (10 Marks)
- b. What are the different structural representations used in case of abstract models used to represent different circuit views at the logic and architectural levels which are based on the graphs. (10 Marks)

Module-2

- 3 a. For the function $f = ab + bc + ac$, find Boolean difference, consensus and smoothing with respect to 'a'. Represent the function and the above in the 3D Boolean space diagram. (10 Marks)
- b. Comment on the components of the data path in the area estimation of the general circuits. (10 Marks)

OR

- 4 a. For shown in Fig.Q4(a), find the size of the maximum clique, clique cover number, largest stable set, stability number, minimum coloring and chromatic number. What is the condition for a graph is said to be perfect and graph is perfect? (10 Marks)

 


Fig.Q4(a)

(10 Marks)

- b. Show the scheduled sequencing graph under resource constraints for the graph show in Fig.Q4(b).

 


Fig. Q4(b)

(10 Marks)

Module-3

- 5 a. For the function $f_1 = a'b' + b'c + ab$ and $f_2 = b'c$, show the Tabular representation and transistor-level schematic representation. (10 Marks)
- b. Consider a networks with the following expression :
- $$f_x = ace + bce + de + g$$
- $$f_y = ad + bd + cde + ge$$
- $$f_z = abc$$
- Compute the Kernal set. (10 Marks)

OR

- 6 a. Consider three-input, two output function : $f = \begin{bmatrix} f_1 \\ f_2 \end{bmatrix}$
- where $f_1 = a'b'c' + a'b'c + ab'c + abc + abc$ and $f_2 = a'b'c + ab'c$,
Find minimum cover, irredundant cover and minimal cover. Also represent the minimum cover in 3D Boolean space diagram. (10 Marks)
- b. What are the different transformation used in logic networks and describe how they different from one another by giving the definitions of each. (10 Marks)

Module-4

- 7 a. Explain state Encoding problem for two level logic minimization. (10 Marks)
- b. Explain the concept of implicit state minimization. (10 Marks)

OR

- 8 a. For the following set of equations, write, the synchronous circuit and synchronous logic network.

$$a^{(n)} = i^{(n)} \oplus i^{(n-1)} ; b^{(n)} = i^{(n-1)} \oplus i^{(n-2)} ;$$

$$c^{(n)} = a^{(n)} b^{(n)} ; d^{(n)} = c^{(n)} + d^{(n-1)}$$

$$e^{(n)} = d^{(n)} e^{(n-1)} + d^{(n)} b^{(n)}$$

$$v^{(n)} = c^{(n)} ; s^{(n)} = e^{(n-1)}.$$

(10 Marks)

- b. Explain modeling and assumptions for retiming for the sequential network models. (10 Marks)

Module-5

- 9 a. For the data flow graph shown on Fig.Q9(a), write ASAP schedule diagram and ALAP schedule under latency constraints.

 


Fig.Q9(a)

(10 Marks)

- b. Explain sharing and binding for resource, dominated circuits. (10 Marks)

OR

- 10 a. Explain relative scheduling under timing constraints. (10 Marks)
- b. Explain unconstrained minimum area binding for general circuits. (10 Marks)
