

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, June/July 2024

Electrical and Electronic Measurements

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*Module-1

- 1 a. With a neat circuit diagram, explain the principle of operation of Kelvin's Double Bridge and derive its balance equation. (10 Marks)
- b. With a neat circuit diagram and phasor diagram, explain the operation of Anderson's Bridge. Also obtain the balance equation. (10 Marks)

OR

- 2 a. With a neat sketch, explain the construction and working of Megger. (10 Marks)
- b. The four arms of an ac bridge have impedance values of $Z_1 = 400 \angle 50^\circ \Omega$, $Z_2 = 200 \angle 40^\circ \Omega$, $Z_3 = 800 \angle -50^\circ \Omega$ and $Z_4 = 400 \angle 20^\circ \Omega$. Find whether the bridge is balanced under this working condition. (04 Marks)
- c. With neat circuit diagram and phasor diagram, explain the operation of low voltage Schering Bridge. Also obtain the balance equation. (06 Marks)

Module-2

- 3 a. Explain the working and operation of Low Power Factor (LPF) Wattmeter. (05 Marks)
- b. The constant of energy meter is 750 rev/KWh. Calculate the number of revolutions made by it. When connected to a load carrying 100 A at 230 V and 0.8 power factor in 30 seconds. If it makes 110 revolutions in 30 seconds. Find the percentage error. (05 Marks)
- c. With a neat sketch, explain the construction and working of Western frequency meter. (10 Marks)

OR

- 4 a. Derive the torque equation of a single phase dynamometer type wattmeter. (07 Marks)
- b. What is creeping in energy meter? How it is prevented? (03 Marks)
- c. With neat sketch, explain the construction and working of a single phase dynamometer type power factor meter. (10 Marks)

Module-3

- 5 a. Explain the construction of CT and PT with necessary phasors. (10 Marks)
- b. Obtain an expression for ratio and phase angle error in a current transformer. (10 Marks)

OR

- 6 a. Explain Silsbee's method of testing current transformer with the help of neat sketch and phasor diagram. (10 Marks)
- b. Explain the method of measurement of flux density in a ring specimen of magnetic material using ballistic galvanometer. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-4

- 7 a. With a neat block diagram, explain the working of true RMS reading voltmeter. (10 Marks)
b. Explain integrating type digital voltmeter with a neat block diagram. (10 Marks)

OR

- 8 a. With neat block diagram, explain the principle of operation of electronic energy meter. (10 Marks)
b. Explain the construction and working of successive approximation type digital voltmeter. (10 Marks)

Module-5

- 9 a. Explain with suitable sketch, working of a Cathode Ray Tube (CRT). (10 Marks)
b. Explain the principle and operation of:
(i) Strip chart recorders
(ii) Galvanometer recorders (10 Marks)

OR

- 10 a. Write notes on: (i) LEDs (ii) Nines (10 Marks)
b. With a neat block diagram, explain X-Y recorders. (10 Marks)
