

CBCS SCHEME

USN

18EC32

Third Semester B.E. Degree Examination, Dec.2023/Jan.2024

Network Theory

Time: 3 hrs.

Max. Marks: 100

Note: Answer any **FIVE** full questions, choosing **ONE** full question from each module.

Module-1

- 1 a. Define the following network terminology
 i) Network element ii) Branch iii) Node iv) Mesh. (08 Marks)
- b. Determine the voltage at node 2 in the circuit shown in Fig Q1(b) source transformation.

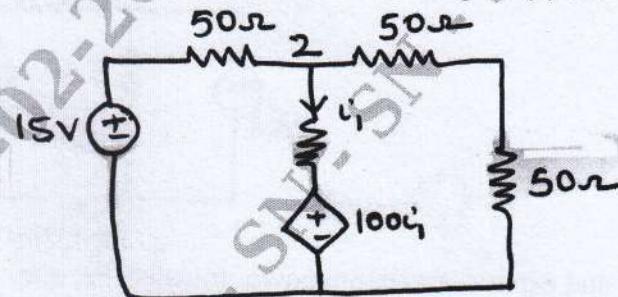


Fig Q1(b)

(06 Marks)

- c. Determine the equivalent resistance between the terminals A and B for the circuit shown in Fig Q1(c).

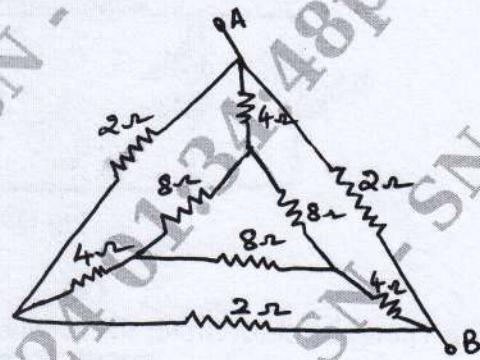


Fig Q1(c)

(06 Marks)

OR

- 2 a. Obtain expressions to convert star connected impedances into equivalent delta connected impedances. (06 Marks)
- b. Determine V_2 which results in zero current 8Ω resistor using mesh analysis for the circuit shown in Fig Q2(b)

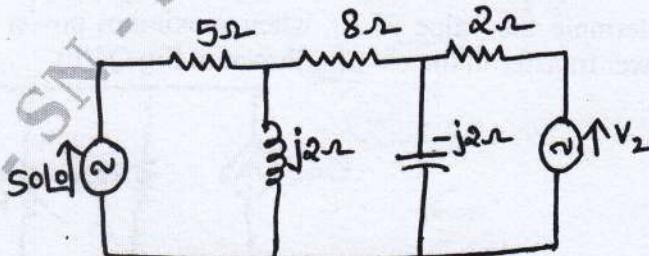


Fig Q2(b)

(07 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, $42+8 = 50$, will be treated as malpractice.

- c. Determine V_1 , V_2 , V_3 for the network shown in Fig Q2(c) using nodal analysis.

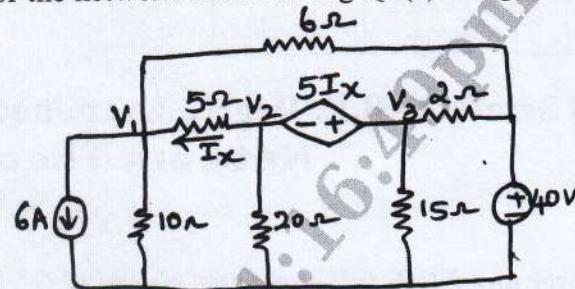


Fig Q2(c)

(07 Marks)

Module-2

- 3 a. Obtain Thevenins and Nortan's equivalent circuit for the network shown in Fig Q3(a)

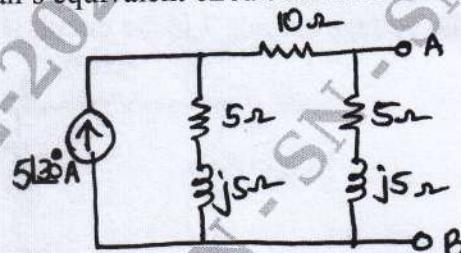


Fig Q3(a)

(08 Marks)

- b. State and explain maximum power transfer theorem. (05 Marks)

- c. Determine the voltage V_x across 30Ω resistor using superposition theorem for the network shown in Fig Q3(c)

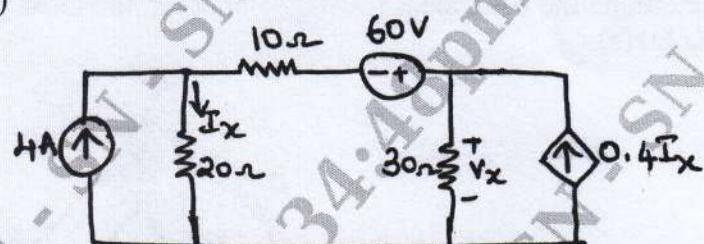


Fig Q3(c)

(07 Marks)

OR

- 4 a. Find V_x using Thevenins theorem for the network shown in Fig Q4(a)

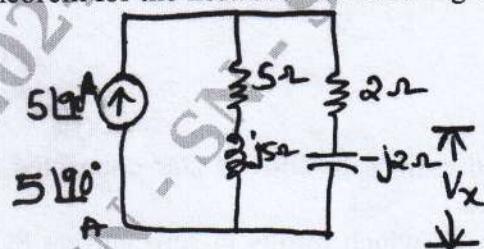


Fig Q4(a)

(06 Marks)

- b. Determine the value of R_L when maximum power is transferred across it. Also find the power transfer in the circuit. Shown in Fig Q4(b)

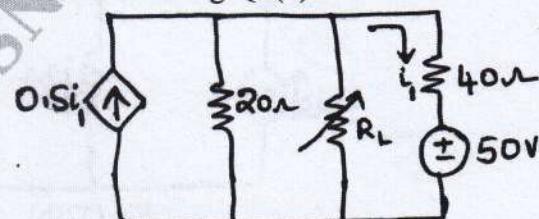


Fig Q4(b)

(08 Marks)

- c. Determine current through R_L using Nortan's theorem for the network shown in Fig Q4(c)

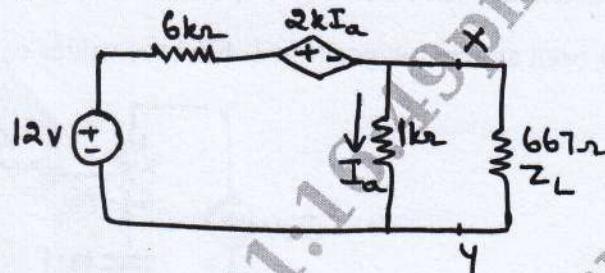


Fig Q4(c)

(06 Marks)

Module-3

- 5 a. Explain the behaviour of R, L and C elements for transients. Mention their representation at the instant of switching. (06 Marks)
- b. Determine i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$ for the network shown in Fig Q5(b) when switch K is changed from position 1 to 2 at $t = 0$, steady state condition having reached before switching.

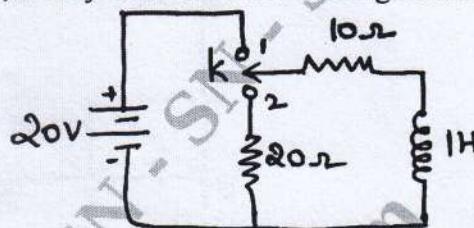


Fig Q5(b)

(07 Marks)

- c. For the network shown in Fig Q5(c), steady state is reached with switch K-open. Switch is closed at $t = 0$, solve for i_1 , i_2 , $\frac{di_1}{dt}$, $\frac{di_2}{dt}$ at $t = 0^+$.

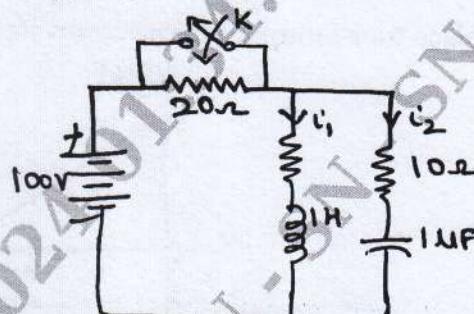
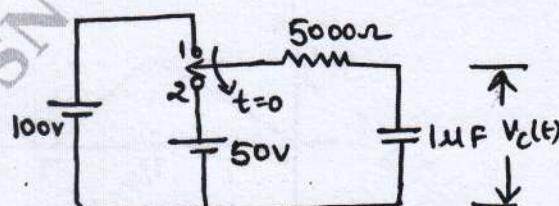


Fig Q5(c)

(07 Marks)

OR

- 6 a. Derive an expression for transient response of series RC circuit for DC excitation. (06 Marks)
- b. Determine the voltage $V_R(t)$ and $V_c(t)$ for $t \geq 0$ when switch is moved from position 1 to 2 for the network shown in Fig Q6(b)

Fig Q6(b)
3 of 5

(08 Marks)

- c. For the network shown in Fig Q6(c), switch K is changed from 1 to 2 at $t = 0$, steady state having been attained in position 1. Find the values of i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0$.

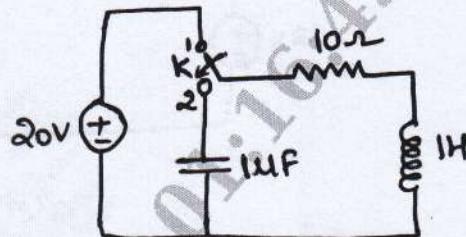


Fig Q6(c)

(06 Marks)

Module-4

- 7 a. State and prove initial and final value theorem.
b. Determine Laplace transform of the function shown in Fig Q7(b)

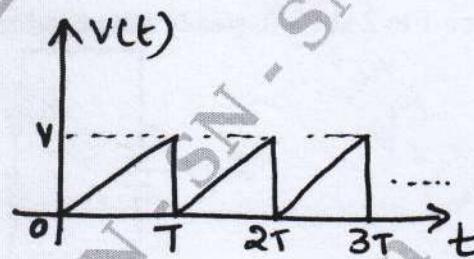


Fig Q7(b)

(06 Marks)

- c. Obtain Laplace transform of (i) $\delta(t)$ (ii) $u(t)$ (iii) t (iv) $\sin wt$

(08 Marks)

OR

- 8 a. Obtain Laplace transform for the waveform shown in Fig Q8(a)

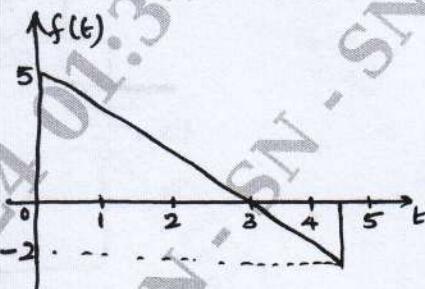


Fig Q8(a)

(08 Marks)

- b. Determine the relation between unit step and unit ramp function.

(04 Marks)

- c. Synthesize the waveform and find the Laplace transform of the waveform shown in Fig Q8(c)

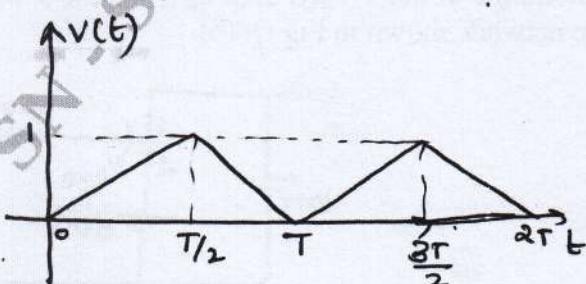


Fig Q8(c)

(08 Marks)

Module-5

- 9 a. Obtain Z-parameters in terms of Y-parameters. (06 Marks)
 b. A series RLC circuit has $R = 4\Omega$, $L = 1\text{mH}$, $C = 10\mu\text{F}$, calculate Q-factor, Bandwidth, resonating frequency half power frequency. (06 Marks)
 c. Determine ABCD parameters for the network shown in Fig Q9(c)

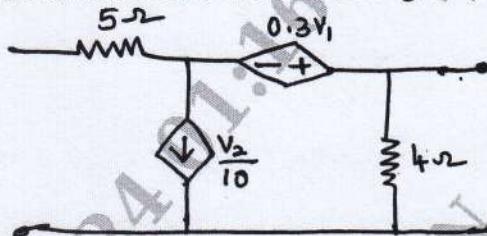


Fig Q9(c)

(08 Marks)

OR

- 10 a. Derive an expression for resonant frequency of the circuit shown in Fig Q10(a)

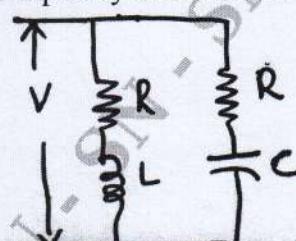


Fig Q10(a)

(06 Marks)

- b. Determine H-parameters and Y-parameters for the network shown in Fig Q10(b)

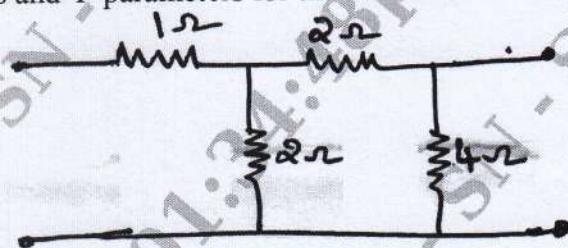


Fig Q10(b)

(08 Marks)

- c. Determine the value of R such that the circuit in Fig Q10(c) is resonant.

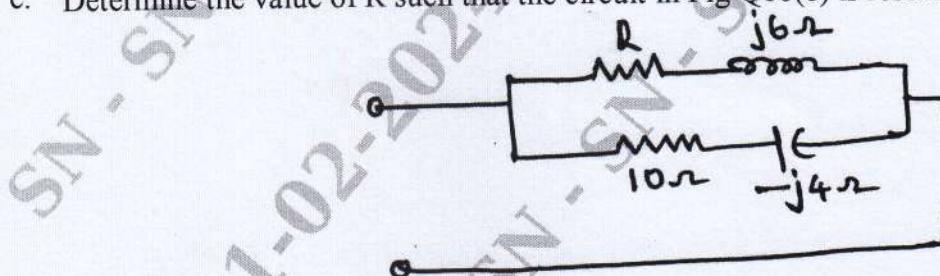


Fig Q10(c)

(08 Marks)
