

CBGS SCHEME

USN

| | | | | | | |
|--|--|--|--|--|--|--|
| | | | | | | |
|--|--|--|--|--|--|--|

18EC32

Third Semester B.E. Degree Examination, Jan./Feb. 2021

Network Theory

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Using source transformation and source shifting techniques, find voltage across 2Ω resistor as shown in Fig.Q.1(a). (07 Marks)

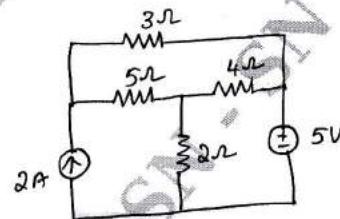


Fig.Q.1(a)

- b. For the network shown in Fig.Q.1(b), find the equivalent resistance between A and B using Star-Delta transformation. (05 Marks)

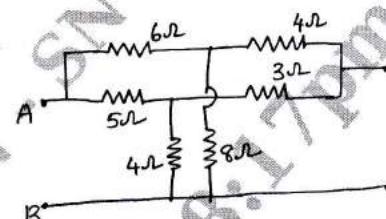


Fig.Q.1(b)

- c. Determine the node voltages V_1 and V_2 by nodal analysis for the network in Fig.Q.1(c). (08 Marks)

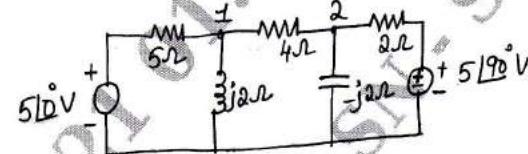


Fig.Q.1(c)

- 2 a. Find the potential difference between M and N using source transformation, for the network shown in Fig.Q.2(a). (05 Marks)

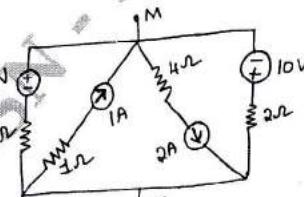


Fig.Q.2(a)

- b. Find V_x using nodal analysis for the network shown in Fig.Q.2(b). (08 Marks)

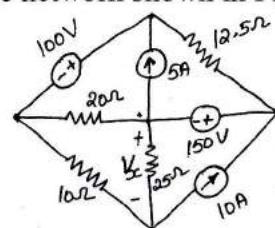


Fig.Q.2(b)

- c. Determine V_0 using mesh analysis for the network shown in Fig.Q.2(c).

(07 Marks)


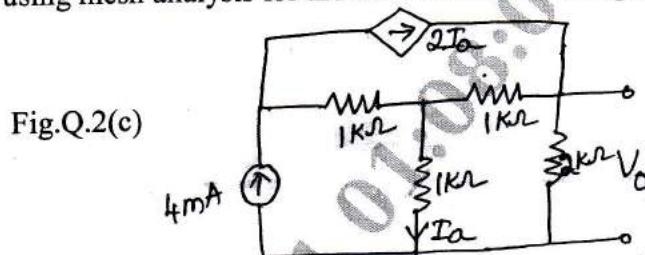


Fig.Q.2(c)


Module-2

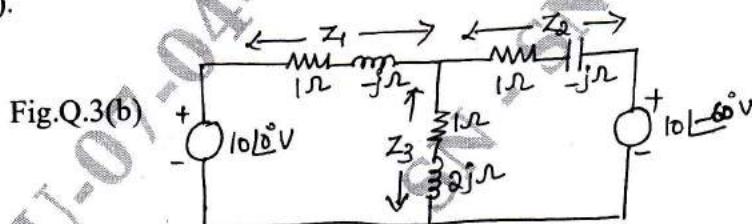- 3 a. State and prove Millman's theorem. (06 Marks)
 b. Find the current through Z_3 using superposition theorem for the network shown in Fig.Q.3(b). (10 Marks)



- c. Find the value of Z_L for which maximum power transfer occurs in the network shown in Fig.Q.3(c). (04 Marks)


Fig.Q.3(c)

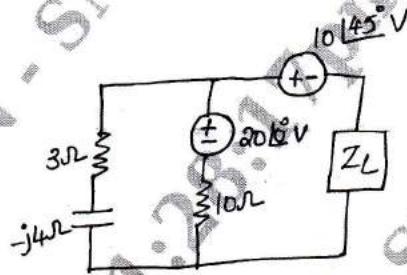

OR


- 4 a. Obtain Thevenin's and Norton's equivalent circuit at terminals AB for the network shown in Fig.Q.4(a). Hence, find the current through 10Ω resistor across AB. (12 Marks)

Fig.Q.4(a)

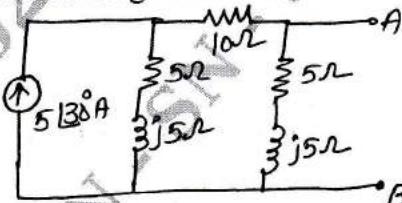


- b. Find the value of R_L for which maximum power is delivered. Also find the maximum power that is delivered to the load R_L . Refer Fig.Q.4(b). (08 Marks)

Fig.Q.4(b)

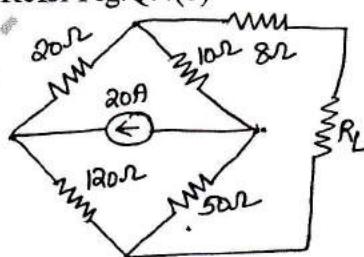


Module-3

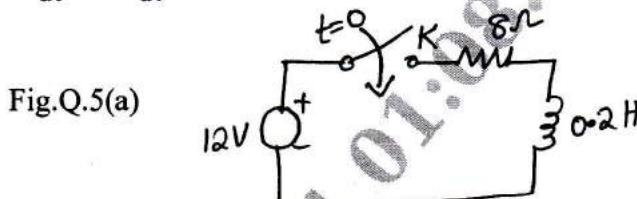- 5 a. In the given network Fig.Q.5(a), K is closed at $t = 0$, with zero current in the inductor. Find the values of i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$. (05 Marks)




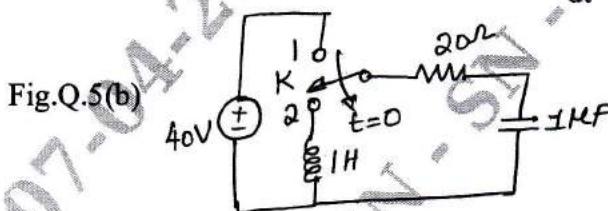- b. In the network Fig.Q.5(b), the switch is moved from position 1 to position 2 at $t = 0$. The steady-state has been reached before switching. Calculate i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$. (07 Marks)




- c. In the network Fig.Q.5(c), the switch K is opened at $t = 0$. At $t = 0^+$, solve for v , $\frac{dv}{dt}$ and $\frac{d^2v}{dt^2}$. (08 Marks)

$$\frac{d^2v}{dt^2}$$

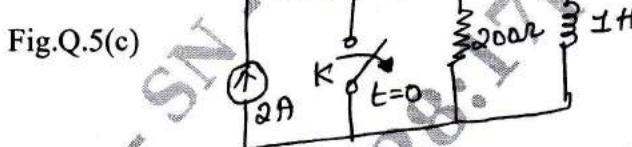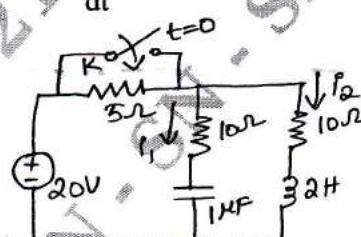**OR**

- 6 a. For the circuit shown in Fig.Q.6(a), steady state is reached with switch K open. The switch is closed at $t = 0$. Find i_1 , i_2 , $\frac{di_1}{dt}$ and $\frac{di_2}{dt}$ at $t = 0^+$. (10 Marks)




- b. For the circuit in Fig.Q.6(b). Find:

i) $v(0^+)$ and $i(0^+)$

ii) $\frac{dv(0^+)}{dt}$ and $\frac{di(0^+)}{dt}$

iii) $v(\infty)$ and $i(\infty)$.

(10 Marks)

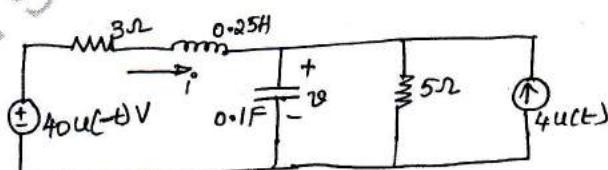


(10 Marks)

- 7 a. Determine the current $i_L(t)$ for $t \geq 0$ for the circuit in Fig.Q.7(a).

Module-4


Fig.Q.7(a)

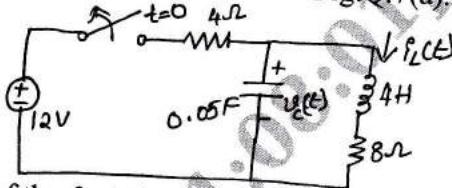

- b. Find the Laplace transform of the function $f(t)$ shown in Fig.Q.7(b).

(10 Marks)


Fig.Q.7(b)

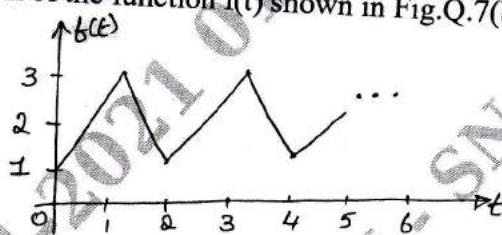**OR**

- 8 a. Determine the voltage $v_c(t)$ and the current $i_c(t)$ for $t \geq 0$ for the circuit shown in Fig.Q.8(a).

(10 Marks)


Fig.Q.8(a)

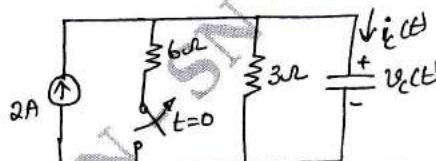

- b. Find the Laplace transform of $f(t)$ shown in Fig.Q.8(b).

(10 Marks)

Fig.Q.8(b)

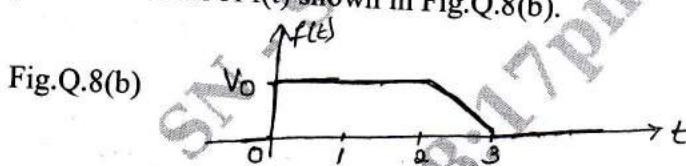**Module-5**


- 9 a. Express Y parameters in terms of h-parameters.

(06 Marks)

- b. Find Z-parameters for the network shown in Fig.Q.9(b).

(06 Marks)

Fig.Q.9(b)

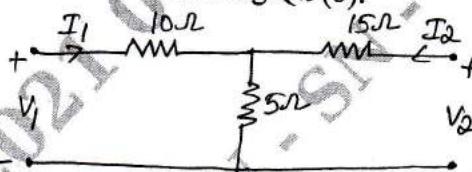

- c. The Z-parameters of a two port network are $z_{11} = 20\Omega$, $z_{22} = 30\Omega$, $z_{12} = z_{21} = 10\Omega$. Find Y and ABCD parameters of the network.

(08 Marks)

- 10 a. Prove that the resonant frequency is the geometric mean of the two half power frequencies.

(06 Marks)


- b. A series RLC circuit has $R = 10\Omega$, $L = 0.01H$ and $C = 0.01\mu F$ and it is connected across 10mv supply. Calculate: i) f_0 ii) Q_0 iii) bandwidth iv) f_1 and f_2 v) I_0 .

(06 Marks)

- c. Find the value of R_1 such that the circuit shown in Fig.Q.10(c) is resonant.

(08 Marks)

Fig.Q.10(c)

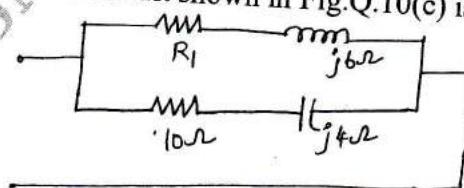

* * * * *