

--	--	--	--	--	--	--	--	--	--

Fourth Semester B.E. Degree Examination, June/July 2024

Analog Circuits

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1
 - a. Explain the design concept of common emitter collector to Base feedback resistor biasing circuit and explain how collector to base feedback resistor provides a negative feedback in the circuit. (07 Marks)
 - b. Considering the conceptual circuit of common source MOSFET amplifier, derive the expression for transconductance g_m and voltage gain A_v . (08 Marks)
 - c. For common emitter voltage divider circuit having $\beta = 100$, $R_1 = 10 \text{ K}\Omega$, $R_2 = 5 \text{ K}\Omega$, $R_C = 1 \text{ K}\Omega$ and $R_E = 500 \Omega$ is provided with DC biasing voltage $V_{CC} = 10 \text{ V}$, Calculate V_{CE} and I_C . (05 Marks)

OR

- 2
 - a. Derive an expression for small signal collector current, transconductance g_m and voltage gain A_v in BJT, when small signal V_{bc} is applied between base and emitter. (10 Marks)
 - b. Design voltage divider bias circuit using MOSFET to establish $I_D = 0.5 \text{ mA}$ and MOSFET parameter are $V_t = 1 \text{ V}$ and $K'_n \left(\frac{W}{L} \right) = 0.5 \text{ mA/V}^2$. Assume $V_{DD} = 15 \text{ V}$. (10 Marks)

Module-2

- 3
 - a. Explain Three basic configurations of MOSFET amplifier and derive expression for characteristic parameter of amplifiers. (08 Marks)
 - b. Briefly explain the Barkhausen criteria for oscillation. (04 Marks)
 - c. For an n-channel MOSFET with $t_{ox} = 10 \text{ nm}$, $L = 1 \mu\text{m}$, $W = 10 \mu\text{m}$, $L_{ov} = 0.05 \mu\text{m}$, $C_{sbo} = C_{dbo} = 10 \text{ fF}$, $V_O = 0.6 \text{ V}$, $V_{SB} = 1 \text{ V}$, $V_{DS} = 2 \text{ V}$. Calculate the following capacitance when the transistor is operating in saturation,

(i) C_{ox}
(ii) C_{ov}
(iii) C_{gs}
(iv) C_{gd}
(v) C_{sb} and C_{db}

 Consider $\epsilon_{ox} = 3.45 \times 10^{-11}$ (08 Marks)

OR

- 4
 - a. Explain the working of RC phase shift oscillator and show how RC network provides 180° of phase shift. (08 Marks)
 - b. In a transistor Colpitts oscillator $C_1 = 1 \text{ nF}$ and $C_2 = 1000 \text{ nF}$. Find the value of L for a frequency of 100 kHz . (04 Marks)
 - c. Explain the High frequency response of common source MOSFET amplifier with its equivalent circuit. (08 Marks)

Module-3

- 5 a. Explain the effect of negative feedback on input and output resistance of voltage series feedback amplifier. (10 Marks)
- b. Explain transformer coupled Class A power amplifier and show that the maximum efficiency of transformer coupled Class A power amplifier is 50%. (10 Marks)

OR

- 6 a. Draw the block diagram of four types of feedback topologies and compare them with respect to input and output resistance. (10 Marks)
- b. Compare Class B pushpull and complementary symmetry power amplifiers. (04 Marks)
- c. In a Class B push pull amplifier operating with $V_{CC} = 25V$ provides a 22 V peak signal to an $8\ \Omega$ load. Find
- (i) Peak load current (ii) dc current drawn from the supply (iii) input power (06 Marks)
- (iv) Output current efficiency (v) power dissipation

Module-4

- 7 a. State the ideal op-amp characteristics. (06 Marks)
- b. Design a linear combination circuit using op-amp to obtain output $V_0 = -2V_1 - 8V_2 - V_3$ with $R_{in} \geq 20\text{ k}\Omega$ at all the inputs and all the resistances $\leq 200\text{ k}\Omega$ (04 Marks)
- c. Draw the circuit of 3 op-amp instrumentation amplifier and derive the expression for its output voltage. (10 Marks)

OR

- 8 a. Explain the working of voltage follower using op-amp and show that its gain is unity. State its advantages. (06 Marks)
- b. Explain the working of zero crossing detectors. (06 Marks)
- c. Design an inverting Schmitt trigger to have trigger voltages of $\pm 4V$ using op-amp 741 with supply of $\pm 15V$. Consider $I_{B(max)} = 500\text{ nA}$. (08 Marks)

Module-5

- 9 a. With neat circuit diagram, explain the operation of R-2R D/A converter. (10 Marks)
- b. Explain the working of pulse width modulation circuit using 555 IC. (06 Marks)
- c. Design a low pass filter using op-amp at a cut off frequency of 1 kHz with pass gain of 2 and choose $C = 0.01\ \mu F$ (04 Marks)

OR

- 10 a. Explain with neat circuit diagram the working of positive precision Half Wave Rectifier. (06 Marks)
- b. Design a monostable 555 timer circuit to produce an output pulse of 10 sec wide and draw the circuit diagram. Choose $C = 100\ \mu F$. (04 Marks)
- c. Draw the circuit of second order low pass filter and explain its operation. (10 Marks)

* * * * *