

USN

## NEW SCHEME

**M.Tech. Degree Examination, May / June 2006**

# CMOS VLSI Design


Time: 3 hrs.]

[Max. Marks:100

**Note:** Answer any *FIVE* full questions.

1.
  - a. Explain the trends in transfer characteristics with  $\beta_n/\beta_p$  ratio's, using suitable mathematical analysis. (10 Marks)
  - b. Write an expression for threshold voltage of n - channel E-MOSFET and hence explain the role of each term in the equation. Modify this equation suitably so as to express the same for  $V_{SB} = 0$  (10 Marks)
2.
  - a. Estimate the ON state resistance of the inverter circuit shown in figure 2(a), using the concepts of sheet resistance. Assume  $5\ \mu\text{m}$  technology. Given the following data, also estimate current between power lines. Derive the formula used for calculations.

LAYER	$R_s$ ohm per square		
n-transistor channel	$5 \mu m$ $10^4$	orbit $2 \times 10^4$	orbit $1.2 \mu m$ $2 \times 10^4$
p-transistor channel	$2.5 \times 10^4$	$4.5 \times 10^4$	$4.5 \times 10^4$

 

- 3 a. Explain the operation of MOSFET in CS configuration when the load to the devices are i) Resistive load, ii) Diode – connected load, iii) Current source load.

**(15 Marks)**

Contd...2

- b. For the circuit shown in figure 3(b), calculate the small signal voltage gain of the circuit.

 


Fig 3(b)

(05 Marks)

4.
  - a. Explain the fabrication process of P well CMOS inverter with neat sketches where ever necessary. (10 Marks)
  - b. What are lambda based design rules? Bring out the merits and demerits there of. (10 Marks)
5.
  - a. Draw symbol diagram of a two bit CMOS shift registers, reducing the number of transistors wherever possible. (10 Marks)
  - b. Draw nMOS, CMOS version of the circuit to realise the boolean expression.  

$$Z = (D + E + A)(B + C)$$
 (10 Marks)
6.
  - a. Derive an expression for figure of merit of n channel E-MOSFET. (10 Marks)
  - b. Explain the working of CMOS transmission gate with its equivalent resistance curve. What are the advantages of transmission gate ? (10 Marks)
7.
  - a. What is domino CMOS logic? Compare it with conventional CMOS logic. Justify the same with one example each. (10 Marks)
  - b. Explain how clock signal can be generated, distributed and stored in dynamic CMOS inverter circuits. (10 Marks)
8. Write technical note on the following :
  - a. Bi-CMOS inverter
  - b. Pass transistor circuit
  - c. Punch through conditions in MOS transistor.
  - d. CMOS D latch.

(20 Marks)

\*\*\*\*\*