

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18ELN14/24

## First/Second Semester B.E. Degree Examination, Feb./Mar. 2022 Basic Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Explain the operation of PN junction diode under forward and reverse bias conditions. (06 Marks)
- b. A full wave bridge rectifier with an input of 100V (rms) feeds a load of  $1K\Omega$ ,  $V_T = 0.7V$ .
- If the diodes employed are silicon, what is the DC voltage across the load?
  - Determine the PIV rating of each diode
  - Determine the maximum current that each diode conducts and the diode power rating. (06 Marks)
- c. Write a short note on :
- Light emitting diode
  - Photodiode
  - Photo coupler. (08 Marks)

OR

- 2 a. What is Zener diode? With a neat circuit diagram, explain the operation of a voltage regulator. (08 Marks)
- b. A silicon diode has  $I_S = 10nA$  at  $25^\circ C$ . Calculate  $I_D$  for a forward bias of  $0.6V$ . (04 Marks)
- c. Define rectifier. Sketch a half wave rectifier with waveforms derive the following :
- Average voltage
  - Average current
  - Efficiency
  - Ripple factor. (08 Marks)

### Module-2

- 3 a. Explain the construction and operation of N-channel JFET (06 Marks)
- b. With a neat diagram, explain the operation of CMOS inverter. (08 Marks)
- c. With a neat diagram, explain the VI characteristics of SCR. (06 Marks)

OR

- 4 a. Explain the characteristics of n-channel JFET. (06 Marks)
- b. With a neat diagram, explain the characteristics of a enhancement type MOSFET (N-channel). (08 Marks)
- c. With neat diagram, explain the two transistor model of an SCR. (06 Marks)

### Module-3

- 5 a. For an op-amp :
- List the characteristics of an ideal op-amp
  - Draw the three input summing circuit (inverting amplifier) and derive the expression for its output voltage. (08 Marks)
- b. Define the terms with respect to op-amp
- Slew rate
  - CMRR
  - Common mode gain  $A_{cm}$  or  $A_c$  of op-amp. (06 Marks)
- c. Design an adder circuit using an op-amp to obtain the output voltage of  $-(2V_1 + 3V_2 + 5V_3)$ . (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg,  $42+8=50$ , will be treated as malpractice.

OR

- 6 a. Draw the circuit of non-inverting op-amp. Derive the expression for its voltage gain. (08 Marks)
- b. With a neat circuit diagrams, explain how an op-amp can be used as a :  
i) differentiator ii) an integrator. (06 Marks)
- c. Find the output  $V_0$  for the following op-amp circuit.

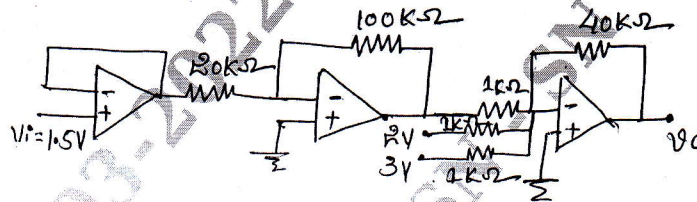


Fig. Q6(c)

(06 Marks)

**Module-4**

- 7 a. What is an amplifier? Explain the operation of transistor amplifier circuit. (08 Marks)
- b. Define feedback amplifier? With a necessary diagram and equation explain different types of feedback. (12 Marks)

OR

- 8 a. Briefly explain how a transistor is used as an electronic switch. (06 Marks)
- b. Explain how 555 timer can be used as an oscillator. (06 Marks)
- c. Define an oscillator? Derive the equation for Wein bridge oscillator. (08 Marks)

**Module-5**

- 9 a. Convert the following :  
i)  $(725.25)_{10} = (?)_2 = (?)_{16}$   
ii)  $(111100111110001)_2 = (?)_{10} = (?)_{16}$  (08 Marks)
- b. Simplify the following :  
i)  $AB + \bar{A}C + A\bar{B}C(AB + C)$   
ii)  $(A + \bar{B})(CD + E)$ . (06 Marks)
- c. Realize a full adder using 2-half adders. (06 Marks)

OR

- 10 a. What is multiplex? Explain the working of 4 : 1 MUX. (06 Marks)
- b. With the help of a logic diagram and truth table, explain the working of a clocked SR flip-flop. (06 Marks)
- c. What is a shift register? Explain the working a 4-bit SISO shift register. (08 Marks)

\*\*\*\*\*