

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18ELN14/24

## First/Second Semester B.E. Degree Examination, July/August 2021 Basic Electronics

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions.

- Explain the operation of p-n junction Diode under unbiased condition with a neat diagram. (08 Marks)
  - In a full wave rectifier, input is from 30 – 0 – 30V. The load and  $R_f$  are 100Ω and 10Ω respectively. Calculate area voltage, efficiency, percentage regulation. (06 Marks)
  - Determine  $I_D$ ,  $V_1$ ,  $V_2$  and  $V_0$  for the given circuit.

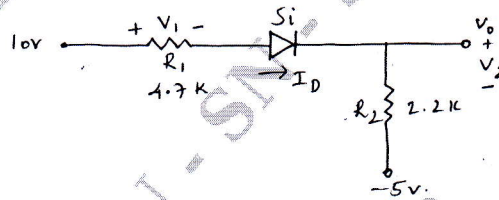


Fig.Q1(c)

(06 Marks)

- With a neat diagram and waveforms explain the working of a bridge rectifier. (08 Marks)
  - Explain the operation of a zener diode with line regulation and load regulation. (08 Marks)
  - For a zener regulator shown in Fig.Q2(c), calculate the range of input voltage for which output remain constant.  $V_Z = 6.1V$ ,  $I_{Zmin} = 2.5mA$ ,  $I_{Zmax} = 25mA$ ,  $r_Z = 0\Omega$ .

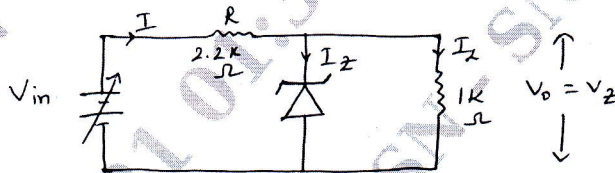


Fig.Q2(c)

(04 Marks)

- Explain the characteristics of N-channel JFET (Drawn and transfer characteristics). (12 Marks)
  - For a N-channel JFET,  $I_{DSS} = 8mA$ ,  $V_P = -5V$ . Find :
    - $I_D$  @  $V_{GS} = -2V$  and  $-3V$
    - $V_{GS}$  @  $I_D = 3mA$  and  $5mA$ . (06 Marks)
  - List out classification of FET with symbols. (02 Marks)
- Draw and explain forward and reverse characteristics of an SCR. (07 Marks)
  - Sketch the transfer and drain characteristics for an n-channel depletion – type MOSFET for the range of values of  $V_{GS} = -6V$  to  $+1V$  with  $I_{DSS} = 8mA$ ,  $V_P = V_{GS(off)} = -6V$ . (08 Marks)
  - With a neat diagram, explain the 2 transistor model of SCR. (05 Marks)
- Explain following with respect to OP-Amp.
    - Virtual ground
    - CMRR
    - Slew rate
    - Offset voltage
    - Matched transistors. (10 Marks)
  - Derive the expression for output voltage of an
    - integrator
    - inverting summing amplifier. With a neat circuit diagram. (10 Marks)

- 6 a. Explain the ideal characteristics of an op-Amp. (08 Marks)  
 b. Derive the expression for output voltage of an non-inverting amplifier with a neat circuit and waveform. (08 Marks)  
 c. Design an adder circuit using an op-Amp to obtain output expression.  
 $V_0 = -2(0.1V_1 + 0.5V_2 + 20V_3)$ . (04 Marks)
- 7 a. Explain the operation of BJT as an amplifier and as a switch. (10 Marks)  
 b. Draw and explain the operation of a voltage series -ve feedback amplifier and derive an expression for its input impedance. (10 Marks)
- 8 a. Define an oscillator. Explain Barkhausen's criteria for oscillations with block diagram. (06 Marks)  
 b. Derive the expression for frequency of oscillations of Wien bridge oscillator. (08 Marks)  
 c. With a neat diagram, explain the working of RC phase shift oscillator. (06 Marks)
- 9 a. Subtract  $(111001)_2$  from  $(101011)_2$  using 2's complement method. (04 Marks)  
 b. State and prove Demorgan's theorem for 3 variables. (04 Marks)  
 c. Simplify the following Boolean expression :
- i)  $A + \overline{AB} = A + B$   
 ii)  $\overline{XYZ} + \overline{XYZ} + \overline{XY} + \overline{XY}$   
 iii)  $\overline{\overline{XY + XYZ + X(Y + XY)}}$   
 iv)  $ABC + \overline{ABC} + \overline{ABC} + \overline{ABC}$   
 v)  $\overline{\overline{AB + ABC + A(B + AB)}}$   
 vi)  $AB + \overline{AC} + \overline{AB}C(AB + C)$ . (12 Marks)
- 10 a. With block diagram and truth table, explain the operation of full ladder using 2 half adder. (08 Marks)  
 b. Explain the operation NOT, AND and OR gates using analogous switch equivalent circuit. (09 Marks)  
 c. Implement Ex - OR gate using only NOR gate. (03 Marks)

\*\*\*\*\*