

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EE34

Third Semester B.E. Degree Examination, Aug./Sept.2020 Analog Electronic Circuits

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- Explain the working of series clipper to clip the input sinusoidal signal:
(i) above V_R (ii) below V_R . Draw the input and output waveforms and transfer characteristic. Neglect cut in voltage V_r . Assume clipping action in positive half cycle of input signal. (06 Marks)
 - Define operating point in a transistor and explain its significance. (04 Marks)
 - Explain the dc analysis of emitter stabilized bias circuit, for this circuit if $R_c = 1 \text{ k}\Omega$, $R_B = 220 \text{ k}\Omega$, $R_E = 1 \text{ k}\Omega$, calculate I_B , I_C , I_E , V_{CE} and V_B . Assume $\beta = 200$. (10 Marks)

OR

- For collector to base bias circuit obtain expressions for stability factors S_{ICO} , S_{UBE} and S_{β} . (10 Marks)
 - Design a voltage divider bias circuit if $V_{CC} = 12\text{V}$, $V_{CE} = 6\text{V}$, $V_E = 1\text{V}$, $I_C = 1 \text{ mA}$, $S_{ICO} = 20$, $\beta = 100$. Draw the circuit (10 Marks)

Module-2

- Develop h-parameter model for transistor amplifier, hence draw h-parameter model for CB, CE and CC modes. (10 Marks)
 - For a single stage CE amplifier, $R_s = 1 \text{ k}\Omega$, $R_1 = 50 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, $R_c = 2 \text{ k}\Omega$, $R_L = 2 \text{ k}\Omega$, $h_{fe} = 50$, $h_{oe} = 25 \mu\text{A/V}$, $h_{ie} = 1.1 \text{ k}\Omega$ and $h_{re} = 2.5 \times 10^{-4}$. Calculate A_V , R_i , A_i , A_{IS} , A_{VS} and R_o . Draw the circuit diagram. Use approximate hybrid model. Across R_E , bypass capacitor is used. (10 Marks)

OR

- For common emitter amplifier with collector to base bias circuit, determine A_i , Z_i , A_V , A_{VS} , A_{IS} and Z_o . Draw circuit diagram. $R_B = 200 \text{ k}\Omega$, $R_c = 10 \text{ k}\Omega$, $h_{ie} = 1.1 \text{ k}\Omega$, $h_{fe} = 50$, $h_{oe} = h_{re} = 0$ and $R_s = 1 \text{ k}\Omega$. (10 Marks)
 - For emitter voltage follower circuit, obtain expression for A_i , Z_i , A_V , R_o and R_o' . Use approximate hybrid model. Also state features of emitter follower circuit. (10 Marks)

Module-3

- For the Darlington connection, obtain expression for A_{i2} , R_{i2} for II stage and A_{i1} , R_{i1} for I stage. (10 Marks)
 - Consider a 2 stage RC coupled amplifier for the I stage $R_s = 1 \text{ k}\Omega$, $R_{C1} = 15 \text{ k}\Omega$, $R_{E1} = 100 \Omega$, $R_1 = 200 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$. For II stage $R_{C2} = 4 \text{ k}\Omega$, $R_{E2} = 330 \Omega$, biasing resistors $R_3 = 47 \text{ k}\Omega$, $R_4 = 4.7 \text{ k}\Omega$. Bypass capacitor is connected across R_{E1} and R_{E2} . Assume $h_{ie} = 1.2 \text{ k}\Omega$, $h_{fe} = 50$, $h_{oe} = 25 \mu\text{A/V}$, $h_{re} = 2.5 \times 10^{-4}$, Determine the overall A_V , A_{VS} , R_{o1}' and R_{o2}' . Draw the circuit diagram. (10 Marks)

OR

- 6 a. Explain the concept of voltage amplifier, current amplifier, transconductance amplifier and transresistance amplifier using Thevenin's or Norton's equivalent circuit. (10 Marks)
- b. For voltage shunt feedback amplifier topology, obtain expressions for R_{if} and R_{of} . (10 Marks)

Module-4

- 7 a. Obtain an expression for 2nd harmonic distortion in a power amplifier using 3-point method. (10 Marks)
- b. A class-B push pull amplifier supplies power to a resistive load of 12 Ω . The turns ratio of output transformer is 3:1 and $\eta = 78.5\%$. Determine the maximum power output, maximum power dissipation in each transistor maximum base and collector current in each transistor. Assume $V_{cc} = 20$ V and $h_{fe} = 25$. (10 Marks)

OR

- 8 a. Obtain expression for f_0 and h_{fe} in Colpitt's RF oscillator. (10 Marks)
- b. Compare RC phase shift and Wein bridge oscillator. (05 Marks)
- c. Calculate the values of R and C in a RC phase shift oscillator if $f_0 = 500$ Hz. Draw the circuit diagram. Assume $C = 0.1$ μ F. (05 Marks)

Module-5

- 9 a. Explain construction, operation and characteristics of enhancement MOSFET. (10 Marks)
- b. Compare D-MOSFET and E-MOSFET. (05 Marks)
- c. Define transconductance " g_m " in FET and Show that $g_m = g_{m_0} \left(1 - \frac{V_{GS}}{V_P} \right)$ (05 Marks)

OR

- 10 a. Consider voltage divider bias circuit of JFET. If $R_D = 1.2$ k Ω , $R_S = 2$ k Ω , $R_1 = 20$ k Ω , $R_2 = 10$ k Ω , $V_{DD} = 12$ V, $I_{DSS} = 12$ mA, $V_P = -4$ V, calculate I_D , V_{GS} , V_G , V_{DS} and V_S . Draw the circuit diagram. (10 Marks)
- b. Consider JFET in fixed bias mode. Derive expressions for Z_{in} , Z_0 and A_v . If $R_G = 1$ M Ω , $r_d = 50$ k Ω , $g_m = 2$ m s , calculate Z_i , A_v and Z_0 . Draw the circuit diagram $R_D = 5.1$ k Ω . (10 Marks)
