

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EE32

Third Semester B.E. Degree Examination, Dec.2023/Jan.2024 Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Reduce the network shown in Fig.Q1(a) to a single voltage source in series with a resistance.

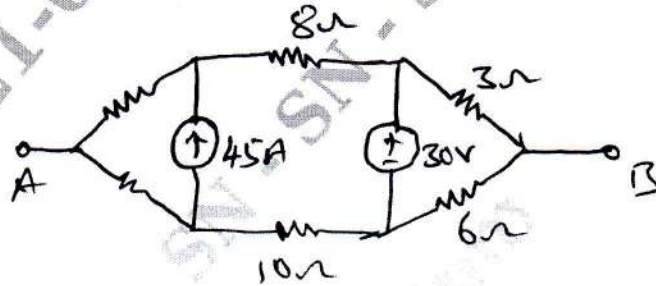


Fig.Q1(a)

(08 Marks)

- b. Determine the nodal voltages V_1, V_2, V_3 and V_4 in the circuit shown in Fig.Q1(b).

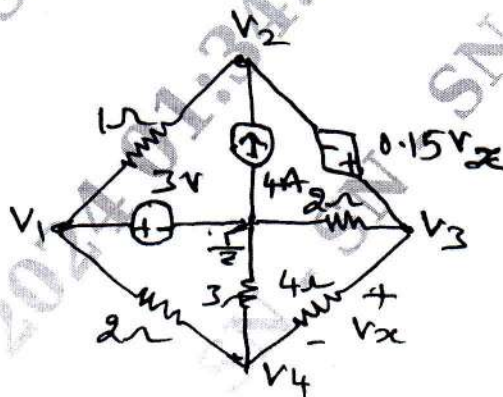


Fig.Q1(b)

(08 Marks)

- c. Compute the resistance between A and B in network shown in Fig.Q1(c) using star - Delta transformation.

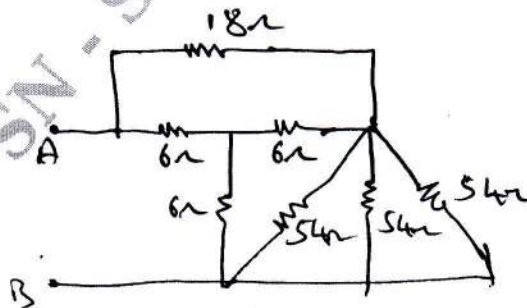


Fig.Q1(c)

(04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 2 a. For the circuit shown in Fig.Q2(a) determine I_x using Mesh analysis.

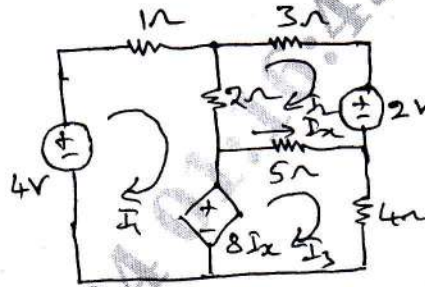


Fig.Q2(a)

- b. Determine node voltages in network shown in Fig.Q2(b).

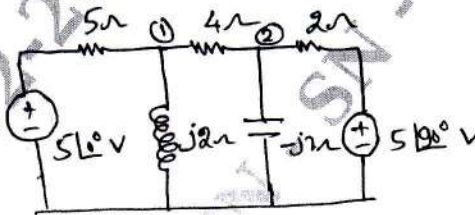


Fig.Q2(b)

(06 Marks)

- c. Find current I using Mesh analysis in the network shown in Fig.Q2(c).

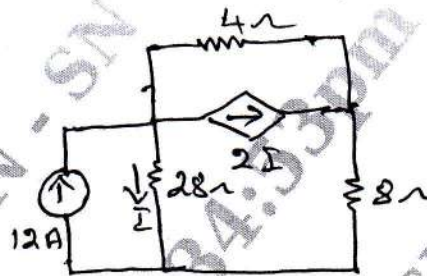


Fig.Q2(c)

(06 Marks)

Module-2

(06 Marks)

- 3 a. State and explain super Position theorem.
 b. Determine the current I in the network shown in Fig.Q3(b) and verify reciprocity theorem.

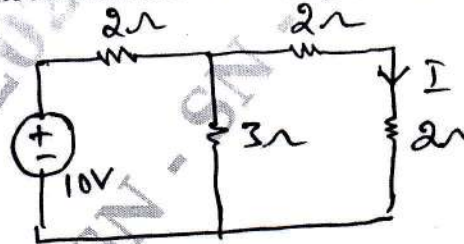


Fig.Q3(b)

(06 Marks)

- c. Obtain Thevenin's equivalent of the network shown in Fig.Q3(c) between terminals A and B and find the power dissipation in load resistance 4Ω .

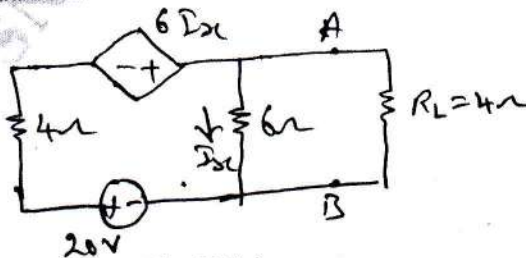


Fig.Q3(c)

(08 Marks)

OR

- 4 a. State and prove Norton's theorem. (06 Marks)
 b. Using Millman's theorem find I_L through R_L for the network shown in Fig.Q4(b).

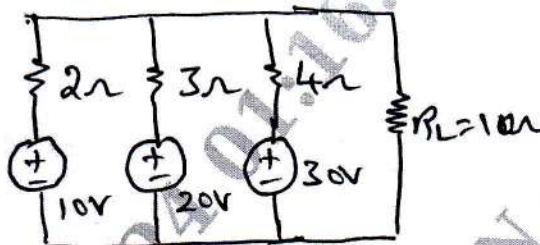


Fig.Q4(b)

(06 Marks)

- c. Find the value of load resistance when maximum power is transferred across it also find the value of maximum power transferred. (Refer Fig.Q4(c)).

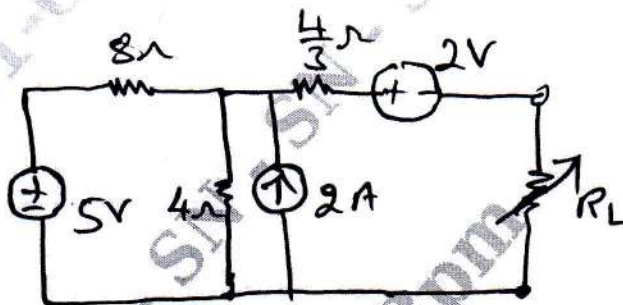


Fig.Q4(c)

(08 Marks)

Module-3

- 5 a. Define the following terms with respect to resonant circuit :
 i) Resonant frequency
 ii) Q Factor
 iii) Bandwidth
 iv) Selectivity. Write the expression of each. (08 Marks)
- b. A series RLC circuit has $R = 1\Omega$, $L = 0.01\text{H}$ and $C = 0.01\mu\text{F}$ and it is connected across θ variable frequency source. Determine :
 i) Resonant frequency
 ii) Quality factor
 iii) Bandwidth
 iv) Cut off frequencies f_1 and f_2 . (06 Marks)
- c. Find $i(0^+)$, $\frac{di}{dt}(0^+)$ and $\frac{d^2i}{dt^2}$ in the network shown in Fig.Q5(c).

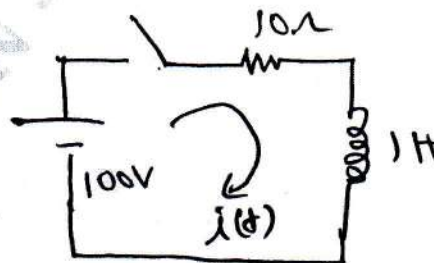


Fig.Q5(c)

(06 Marks)

OR

- 6 a. In the network shown in Fig.Q6(a) switch 'K' is changed from position 'a' to 'b' at $t = 0$. Solve for i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$, if $R = 1000\Omega$, $L = 1H$, $C = 0.1$ and $v = 1000V$. Assume capacitor is initially uncharged.

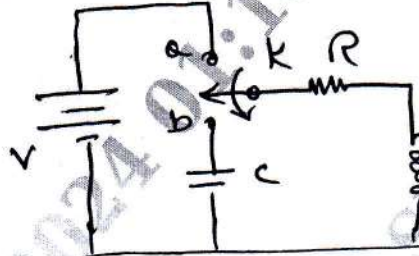


Fig.Q6(a)

(08 Marks)

- b. Show that the resonant frequency at a series RLC circuit is equal to geometric mean of two half power frequencies. (06 Marks)
- c. For the circuit shown in Fig.Q6(c) find two values of capacitor for the reasonable. Consider $f = 50Hz$.

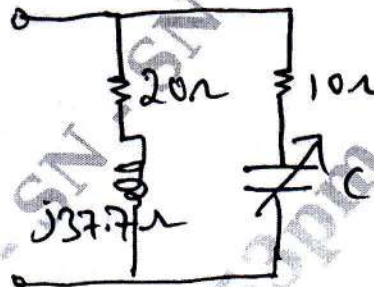


Fig.Q6(c)

(06 Marks)

Module-4

- 7 a. Find $i(t)$ for $t \geq 0$ for the network shown in Fig.Q7(a) using Laplace transformers.

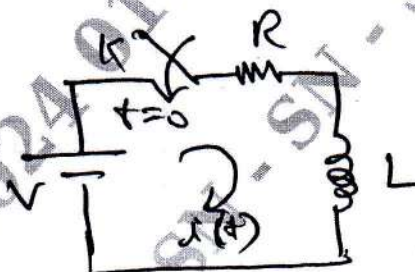
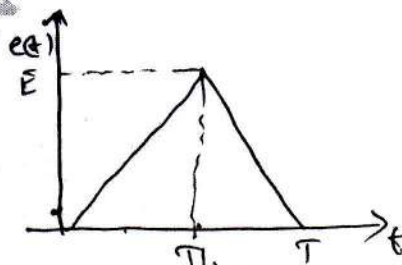


Fig.Q7(a)

(06 Marks)

- b. State and prove :
 i) Initial value theorem
 ii) Final value theorem. (06 Marks)
- c. Obtain the Laplace transform of triangular waveform shown in Fig.Q7(c).

Fig.Q7(c)
4 of 6

(08 Marks)

OR

- 8 a. Find the Laplace transform of the waveform shown in Fig.Q8(a).

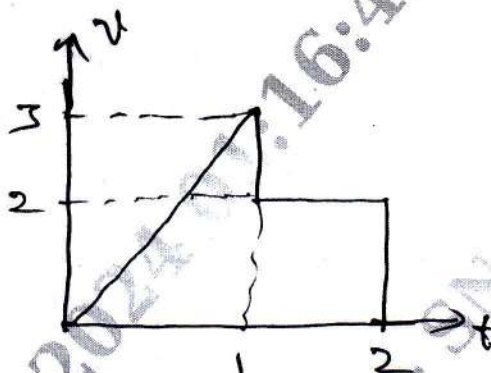


Fig.Q8(a)

(08 Marks)

- b. Find the Laplace transform of periodic waveform shown in Fig.Q8(b).

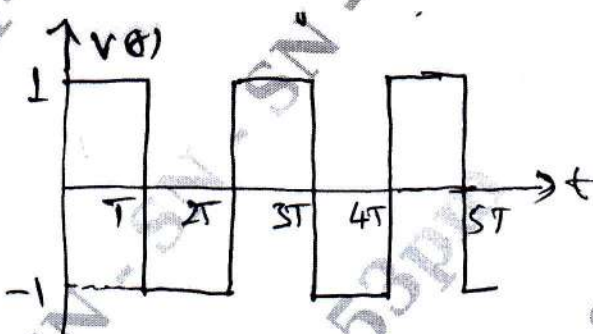


Fig.Q8(b)

(08 Marks)

- c. Find the laplace transform of the following function : i) $u(t)$ ii) $\delta(+)$.

(04 Marks)

Module-5

- 9 a. Find the open circuit impedance parameters for the current shown in Fig.Q9(a).

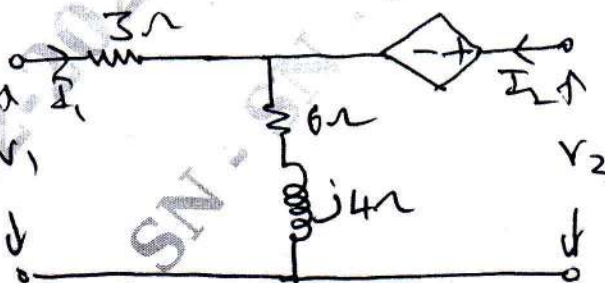


Fig.Q9(a)

(06 Marks)

- b. Derive expressions for 'Y' parameters in terms of Z - parameters.

(06 Marks)

- c. A 3 - phase 400V, 4 wire system has a star connected load with $Z_R = 10\Omega$, $Z_Y = (15 + j10)\Omega$ and $Z_B = j5\Omega$. Find the line current and current through natural conductor. Draw the vector diagram.

(08 Marks)

OR

- 10 a. Find 'Y' parameters of the two port network shown in Fig.10(a). Also find 'Z' parameters.

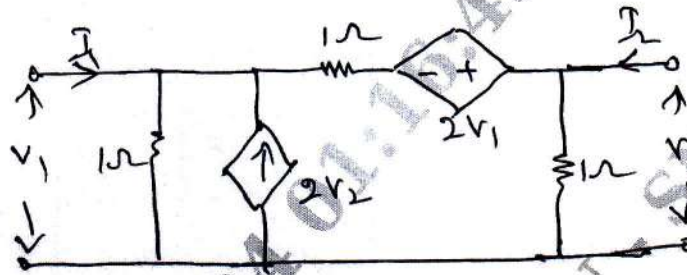


Fig.Q10(a)

- b. A balanced set of three phase voltages is connected to an unbalanced set of 'Y' connected impedances. $V_{RY} = 212 \angle 90^\circ \text{V}$, $V_{YB} = 212 \angle -150^\circ \text{V}$ and $V_{BR} = 212 \angle -30^\circ \text{V}$, $Z_R = (10 + j0)\Omega$, $Z_Y = (10 + j0)\Omega$ and $Z_C = (0 - j20)\Omega$.

Find :

- The line current
- Phase voltages
- Power dissipated in each phase.

(10 Marks)
