

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EE32

Third Semester B.E. Degree Examination, Jan./Feb. 2021 Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define :
- i) Linear and non linear circuit
 - ii) Active and passive circuit
 - iii) Unilateral and bilateral circuit. (06 Marks)
- b. For the circuit shown in Fig.Q1(b) determine resistance between M and N using star/delta transformation.

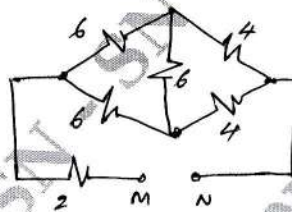


Fig.Q1(b)

(06 Marks)

- c. Use node voltage analysis to find node voltages in the network shown in Fig.Q1(c).

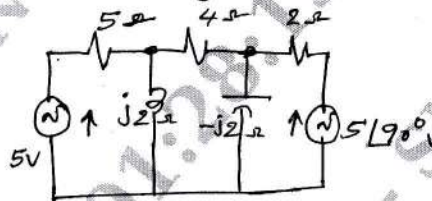


Fig.Q1(c)

(08 Marks)

OR

- 2 a. Derive an expression for converting Delta to Star. (06 Marks)
- b. Determine potential difference between M and N using source transformation of circuit shown in Fig.Q2(b).

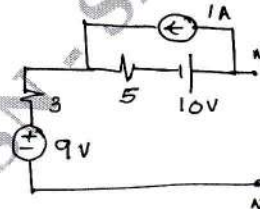


Fig.Q2(b)

(06 Marks)

- c. Use Mesh current analysis to find the current flowing in 30Ω resistor of circuit shown in Fig.Q2(c).

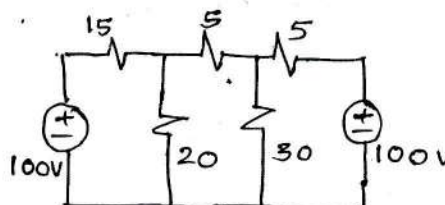


Fig.Q2(c)

(08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-2

- 3 a. State and prove reciprocity theorem.
 b. For the circuit shown in Fig.Q3(b) find ' I_x ' using super position theorem.

(06 Marks)

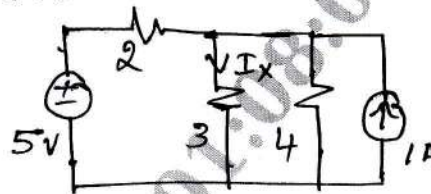


Fig.Q3(b)

(07 Marks)

- c. Use Milliman's theorem to find current in the circuit shown in Fig.Q3(c).

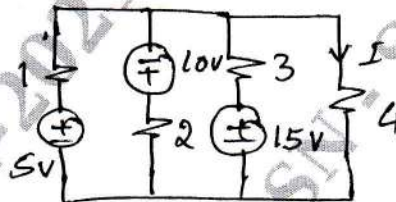


Fig.Q3(c)

(07 Marks)

OR

- 4 a. State and obtain condition for maximum power when load impedance is equal to pure variable resistance.
 b. For the network shown in Fig.Q4(b), find current ' I ' using Norton's theorem.

(06 Marks)

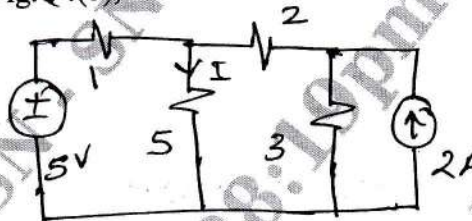


Fig.Q4(b)

(07 Marks)

- c. For the network shown in Fig.Q4(c). Draw Thevenin's equivalent circuit.

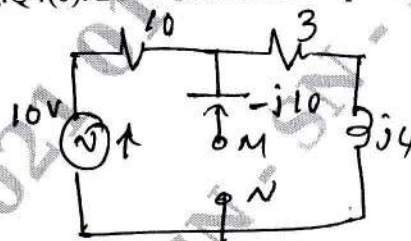


Fig.Q4(c)

(07 Marks)

Module-3

- 5 a. Show that resonant frequency is the geometric mean of cut-off frequencies. (07 Marks)
 b. A series RLC circuit has a resistance of 100Ω , an inductance of $0.5H$ and capacitance of $0.4\mu F$. Find the resonant frequency, half power frequencies, band width and quality factor. (07 Marks)
 c. For the circuit shown in Fig.Q5(c), find the value of inductance take $\omega = 500\text{r/s}$.

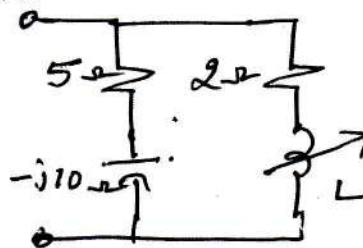


Fig.Q5(c)

(06 Marks)

OR

- 6 a. Explain the behavior of R, L and C for initial condition. (07 Marks)
 b. For the network shown in Fig.Q6(b) switch is closed at $t = 0$. Determine current and its first and second derivative at $t = 0^+$.

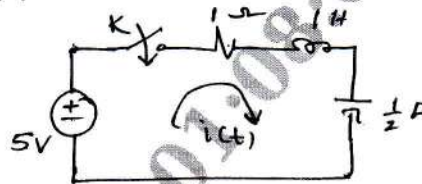


Fig.Q6(b)

(07 Marks)

- c. For the R - L circuit shown in Fig.Q6(c). Obtain the expression for current $i(t)$ for $t \geq 0$.

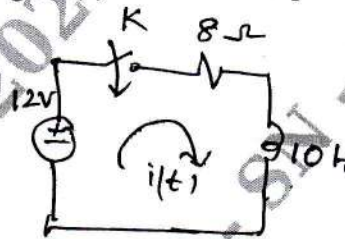


Fig.Q6(c)

(06 Marks)

Module-4

- 7 a. State and prove initial value theorem. (06 Marks)
 b. Find the inverse Laplace transform of

$$V(s) = \frac{10}{s(s+1)(s+2)}$$
 (07 Marks)
 c. For the network shown in Fig.Q7(c), draw the transformed circuit and obtain the expression for current $i(t)$ for $t \geq 0$.

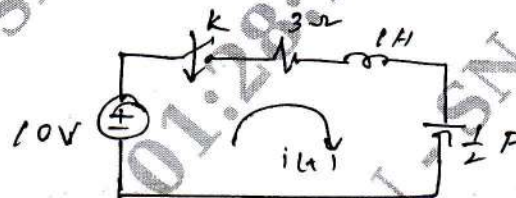


Fig.Q7(c)

(07 Marks)

OR

- 8 a. Find the ILT of: i) step signal ii) Ramp iii) impulse signal. (06 Marks)
 b. For the waveform shown in Fig.Q8(b) obtain the Laplace transform.

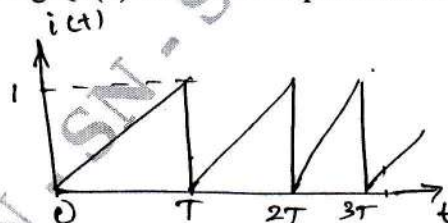


Fig.Q8(b)

(08 Marks)

- c. Find the initial and final value of following functions :

i) $V_1(s) = \frac{s^2 + 3s + 2}{s^3 + 3s^2 + 3s + 1}$

ii) $V_2(s) = \frac{10}{s(s+3)}$

(06 Marks)

Module-5

- 9 a. A 3 phase supply with line voltage of 250V has a unbalanced Delta connected load as shown in Fig.Q9(a). Determine line currents, active and reactive power for phase sequence A B C.

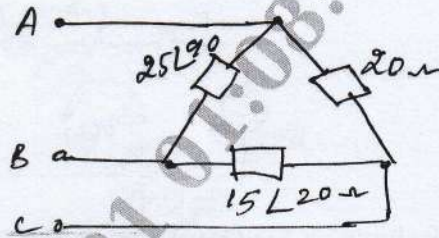


Fig.Q9(a)

(10 Marks)

- b. An unbalanced 4 wire star connected load has a balanced supply of 400V. For the phase sequence ABC, calculate the line currents and total power of the circuit shown in Fig.Q9(b).

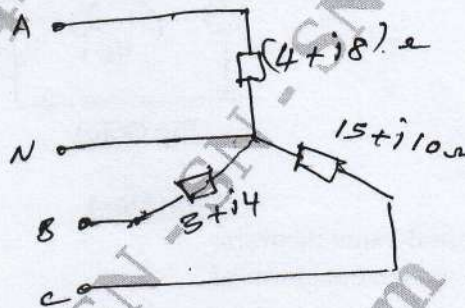


Fig.Q9(b)

(10 Marks)

OR

- 10 a. Obtain the Impedance parameters in terms of Admittance parameters.
 b. For the network shown in Fig.Q10(b) determine z-parameters.

(10 Marks)

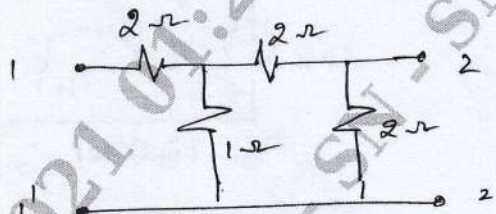


Fig.Q10(b)

(10 Marks)
