

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EE36

## Third Semester B.E. Degree Examination, Dec.2023/Jan.2024 Electrical and Electronic Measurement

Time: 3 hrs.

Max. Marks: 100

**Note:** Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Explain Maxwell's inductance and capacitance bridge. (10 Marks)  
b. Explain Fall off potential method to measure Earth resistance. (10 Marks)

OR

- 2 a. Explain Anderson's bridge. (10 Marks)  
b. Explain Megger. (10 Marks)

### Module-2

- 3 a. Explain Dynamometer type of Wattmeter. (10 Marks)  
b. Explain measurement of  $3\phi$  power using 2 Wattmeter method. (10 Marks)

OR

- 4 a. Explain Dynamometer type power factor meter. (10 Marks)  
b. Explain Single phase induction type energy meter. (10 Marks)

### Module-3

- 5 a. Explain Shunt's and Multipliers. (10 Marks)  
b. Explain Silsbee's method of testing CT. (10 Marks)

OR

- 6 a. Explain Measurement of flux / flux density. (10 Marks)  
b. A CT has a single turn primary and 400 secondary turns. The magnetizing current is 90A while core loss current is 40A. Secondary circuit phase angle is  $28^\circ$ , calculate the actual primary current and ratio error when secondary current carries 5A current. (10 Marks)

### Module-4

- 7 a. Explain Ramp type DVM. (10 Marks)  
b. Explain true rms reading voltmeter. (10 Marks)

OR

- 8 a. Explain integrating type DVM. (10 Marks)  
b. Explain Q meter. (10 Marks)

### Module-5

- 9 a. Explain Dot matrix displays. (10 Marks)  
b. Explain Cathode ray tubes. (10 Marks)

OR

- 10 a. Explain Electro cardio graph. (10 Marks)  
b. Explain Nixie tubes and LVD. (10 Marks)

\* \* \* \* \*

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg,  $42+8=50$ , will be treated as malpractice.