

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EC32

## Third Semester B.E. Degree Examination, Aug./Sept. 2020 Network Theory

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

### Module-1

- 1 a. Using source shifting and source transformation techniques, find the value of  $V_x$  for the circuit in Fig.Q1(a).

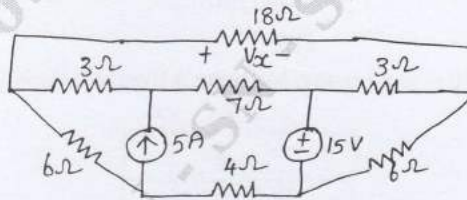


Fig.Q1(a)

(10 Marks)

- b. Use Mesh analysis to the circuit shown in Fig.Q1(b) to find the power supplied by 4V source.

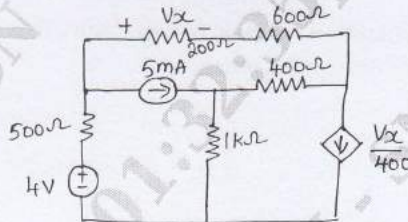


Fig.Q1(b)

(10 Marks)

OR

- 2 a. Find the resistance  $R_{xy}$  for the circuit shown in Fig.Q2(a) using star-delta transformation.

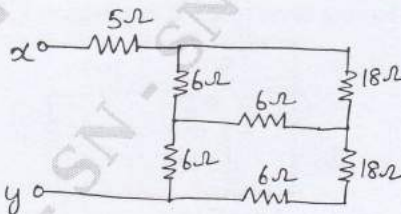


Fig.Q2(a)

(10 Marks)

- b. Find  $I_1$  in the circuit of Fig.Q2(b) using nodal analysis.

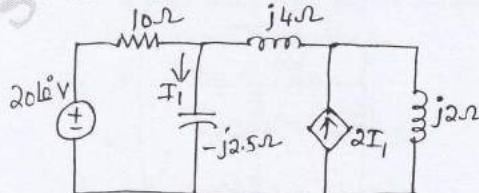


Fig.Q2(b)  
1 of 4

(10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42-8 = 50, will be treated as malpractice.

**Module-2**

- 3 a. Use superposition theorem to find  $i_0$  in the circuit shown in Fig.Q3(a).

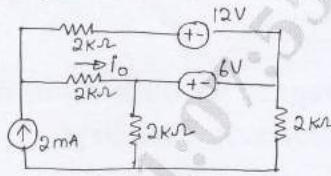


Fig.Q3(a)

(10 Marks)

- b. Find the Thevenin's and Norton's equivalent circuits at the terminals a-b for the circuit in Fig.Q3(b).

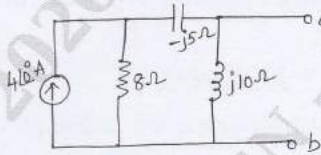


Fig.Q3(b)

(10 Marks)

**OR**

- 4 a. Find the current through  $(10 - j3)\Omega$  using Millman's theorem Refer Fig.Q4(a).

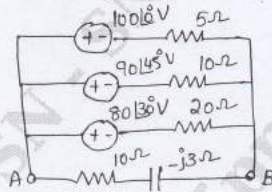


Fig.Q4(a)

(10 Marks)

- b. Find the value of  $R_L$  for the network shown in Fig.Q4(b) that results in maximum power transfer. Also find the value of maximum power.

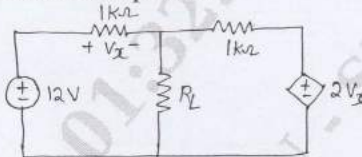


Fig.Q4(b)

(10 Marks)

**Module-3**

- 5 a. For the circuit shown in Fig.Q5(a), the switch K is changed from position 1 to position 2 at  $t = 0$ . Steady-state condition having been reached at position 1. Find the values of

$i, \frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$

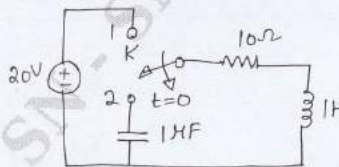


Fig.Q5(a)

(10 Marks)

- b. For the circuit shown in Fig.Q5(b), steady-state is reached with switch K open. At  $t = 0$ , the switch is closed. Determine the values  $V_a(0^-)$  and  $V_a(0^+)$ .

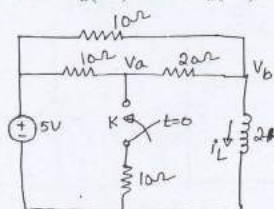


Fig.Q5(b)

(10 Marks)



OR

- 6 a. In the network shown in Fig.Q6(a), the switch K is opened at  $t = 0$ . Find  $v$ ,  $\frac{dv}{dt}$  and  $\frac{d^2v}{dt^2}$  at  $t = 0^+$ .

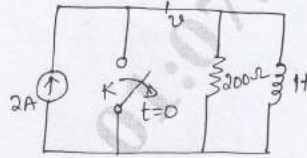


Fig.Q6(a)

(10 Marks)

- b. For the circuit shown in Fig.Q6(b) find :

- i)  $i(0^+)$  and  $v(0^+)$       ii)  $\frac{di(0^+)}{dt}$  and  $\frac{dv(0^+)}{dt}$       iii)  $i(\infty)$  and  $v(\infty)$ .

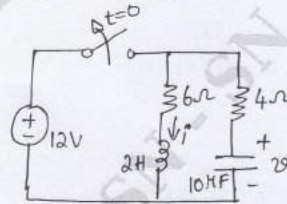


Fig.Q6(b)

(10 Marks)

**Module-4**

- 7 a. State and prove initial-value theorem and final-value theorem. (10 Marks)  
 b. For the circuit of Fig.Q7(b).  
 i) Write a differential equation for  $i_L(t)$     ii) find  $I_L(s)$     iii) solve for  $i_L(t)$ .

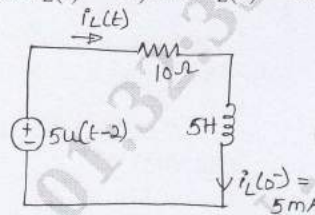


Fig.Q7(b)

(10 Marks)

OR

- 8 a. Find the Laplace transform of the periodic signal  $x(t)$  shown in Fig.Q8(a).

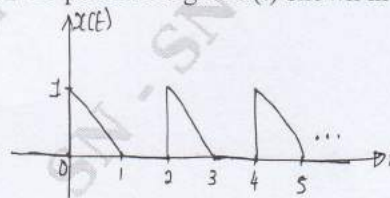


Fig.Q8(a)

(10 Marks)

- b. For the circuit shown in Fig.Q8(b), steady state is reached with the 100V source. At  $t = 0$ , switch k is opened. What is the current through the inductor at  $t = \frac{1}{2}$  seconds.

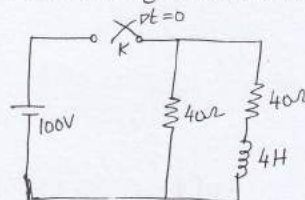


Fig.Q8(b)

(10 Marks)

**Module-5**

- 9 a. Explain h-parameters. Express h-parameters in terms of z-parameters.  
 b. Find y-parameters for the circuit shown in Fig.9(b).

(10 Marks)

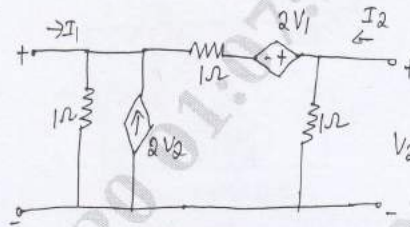


Fig.Q9(b)

(10 Marks)

**OR**

- 10 a. A series RLC circuit has  $R = 10\Omega$ ,  $L = 0.1\text{H}$  and  $C = 100\mu\text{F}$  and is connected across a 200V, variable frequency source, find :  
 i) Resonant frequency  
 ii) Impedance at this frequency  
 iii) Voltage drops across l and c at this frequency  
 iv) Quality factor  
 v) Bandwidth.  
 b. Find the value of  $R_1$  such that the circuit given in Fig.10(b) is resonant.

(07 Marks)

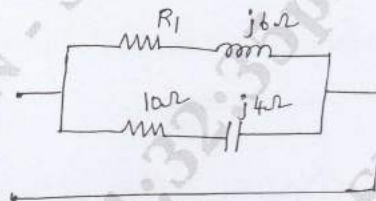


Fig.10(b)

(07 Marks)

- c. A series RLC circuit has  $R = 10\Omega$ ,  $L = 0.01\text{H}$  and  $C = 0.01\mu\text{F}$  and it is connected across 10mV supply. Calculate :  
 i)  $f_0$  ii)  $Q_0$  iii) Bandwidth iv)  $f_1$  and  $f_2$  v)  $I_0$ .

(06 Marks)

\*\*\*\*\*