

# CBCS SCHEME

USN

18EC32

## Third Semester B.E. Degree Examination, Feb./Mar. 2022 Network Theory

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Determine current through  $12\Omega$  resistor shown in Fig.Q1(a), using source transformation.

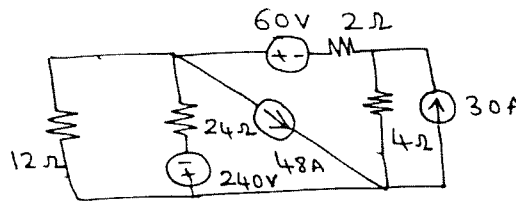


Fig.Q1(a)

(08 Marks)

- b. Find the equivalent resistance of the circuit shown in Fig.Q1(b), using star delta transformation.

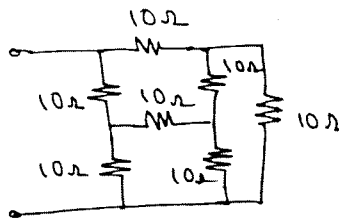


Fig.Q1(b)

(08 Marks)

- c. Discuss the dependent sources. (04 Marks)

OR

- 2 a. Using loop analysis, find the current through  $10\Omega$  resistor for the circuit shown in Fig.Q2(a).

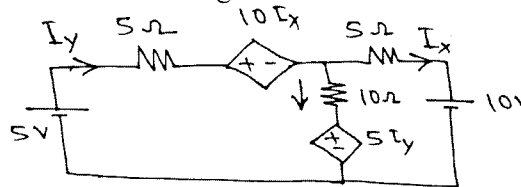


Fig.Q2(a)

(08 Marks)

- b. For the network shown in Fig.Q2(b), determine node voltages  $V_1, V_2, V_3$  and  $V_4$  using nodal analysis.

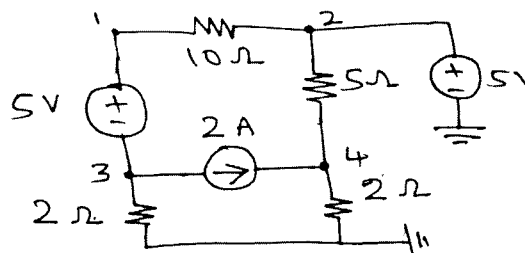


Fig.Q2(b)

(08 Marks)

- c. Explain the super Mesh with example. (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42-8-50, will be treated as malpractice.

**Module-2**

- 3 a. Using super position theorem, find the current through  $20\Omega$  resistor shown in Fig.Q3(a).

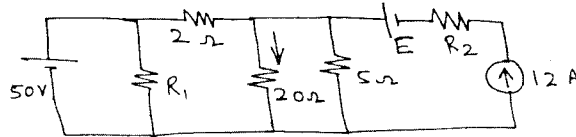


Fig.Q3(a)

(08 Marks)

- b. Using Millman's theorem, determine the current through  $(2 + j2)\Omega$  impedance for the network shown in Fig.Q3(b).

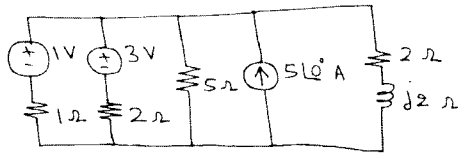


Fig.Q3(b)

(08 Marks)

- c. State the Norton's theorem and also write the procedure to be followed for solving the problem. (04 Marks)

**OR**

- 4 a. What should be the value of  $R$  such that maximum power transfer can take place from the rest of the network to  $R$ . Obtain the amount of this power for circuit shown in Fig.Q4(a).

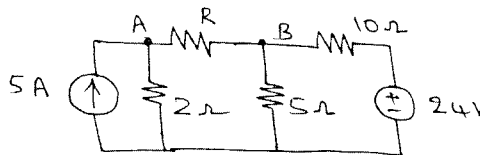


Fig.Q4(a)

(08 Marks)

- b. Obtain the Thevenin's equivalent circuit cross AB for the circuit shown in Fig.Q4(b).

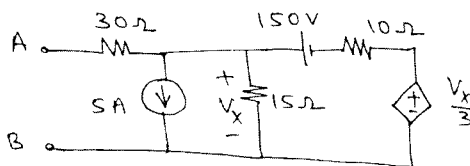


Fig.Q4(b)

(08 Marks)

- c. State the maximum power transfer theorem and also write equation of  $P_{max}$  for both DC and AC circuits. (04 Marks)

**Module-3**

- 5 a. Explain the transient behavior of the resistance, inductance and capacitor. Also write the procedure for evaluating transient behavior. (10 Marks)
- b. In the network shown in Fig.Q5(b), a steady state is reached with the switch 'K' open. At  $t = 0$  the switch is closed. Determine the value of  $V_a(0^+)$  and  $V_a(0^-)$ .

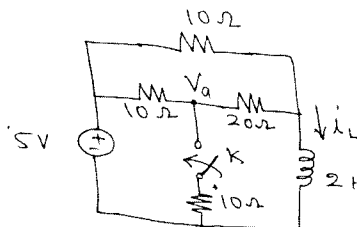


Fig.Q5(b)

(10 Marks)

OR

- 6 a. For the network shown in Fig.Q6(a)  $V_1(t) = e^{-t}$  for  $t \geq 0$  and is zero for all  $t < 0$ . If the capacitor is initially uncharged determine the value of  $\frac{d^2 V_2}{dt^2}$  and  $\frac{d^3 V_2}{dt^3}$  at  $t = 0^+$ .

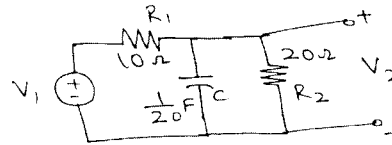


Fig.Q6(a)

(10 Marks)

- b. The switch 'S' is changed from position 1 to position 2 at  $t = 0$ . Steady state conditions have been reached in position 1. Find the value of  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2 i}{dt^2}$  at  $t = 0^+$  for the circuit shown in Fig.Q6(b).

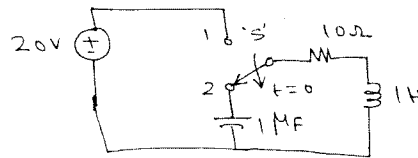


Fig.Q6(b)

(10 Marks)

**Module-4**

- 7 a. Find the Laplace transform of  $f(t)$  shown in Fig.Q7(a).

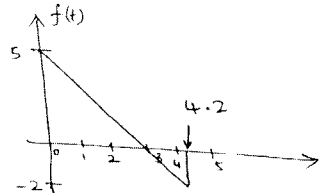


Fig.Q7(a)

(10 Marks)

- b. Find the Laplace transform of the pulse shown in Fig.Q7(b).

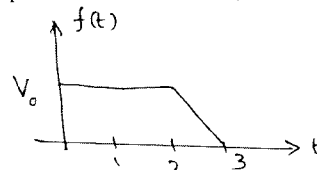


Fig.Q7(b)

(10 Marks)

OR

- 8 a. Find  $i(t)$  for the circuit shown in Fig.Q8(a).

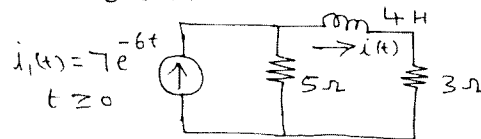


Fig.Q8(a)

(10 Marks)

- b. A voltage pulse of 10V and 5μsec duration is applied to the RC network shown in Fig.Q8(b). Find the current  $i(t)$ .

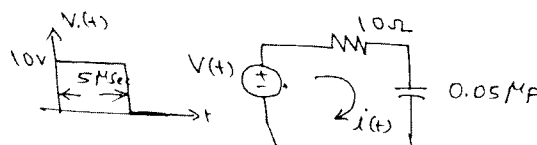


Fig.Q8 (b)

(10 Marks)

**Module-5**

- 9 a. Obtain y-parameters in terms of z-parameters and h-parameters. (10 Marks)  
 b. For the network shown in Fig.Q9(b), find the T-parameters.

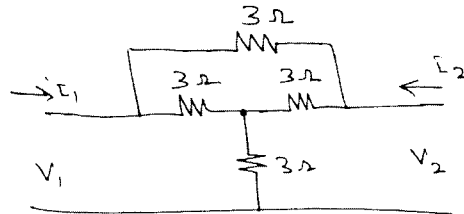


Fig.Q9(b)

(10 Marks)

**OR**

- 10 a. Derive the expression of bandwidth, half power frequencies and selectivity of a series resonance circuit. (10 Marks)  
 b. For the parallel resonant circuit shown in Fig.Q10(b), find  $I_0$ ,  $I_L$ ,  $I_C$ ,  $f_0$  and dynamic resistance.

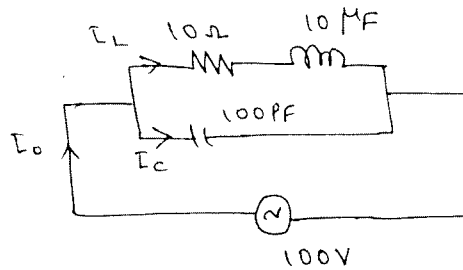


Fig.Q10(b)

(10 Marks)

\*\*\*\*\*