

# MAKE-UP EXAM

USN

--	--	--	--	--	--	--	--	--	--

BBEE103/203

## First/Second Semester B.E./B.Tech. Degree Examination, Nov./Dec. 2023 Basic Electronics for EEE Stream

Time: 3 hrs.

Max. Marks: 100

- Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.  
2. M : Marks , L: Bloom's level , C: Course outcomes.  
3. Assume any missing data suitably.*

Module – 1			M	L	C
Q.1	a.	With the help of neat circuit diagram and waveform, explain the working of full wave, rectifier with center tapped transformer.	8	L2	CO1
	b.	Explain the forward and reverse characteristics of semiconductor diode.	6	L2	CO1
	c.	A Zener regulator has the following data : $V_i = 16V$ , $V_0 = 6V$ , $I_{L(max)} = 60mA$ , $Z_z = 7\Omega$ , $R = 150\Omega$ . Calculate line regulation and ripple rejection ratio.	6	L3	CO1
<b>OR</b>					
Q.2	a.	Describe the working of a capacitor filter for a half wave rectifier with a neat circuit diagram and necessary waveforms.	8	L3	CO1
	b.	What is a DC load line? With the help of neat circuit diagram and waveform, explain the procedure of constructing a DC load line for a semiconductor diode.	8	L3	CO1
	c.	Define : i) Line regulation ii) Load regulation.	4	L2	CO1
<b>Module – 2</b>					
Q.3	a.	Explain the construction and working of n-channel JFET.	8	L3	CO2
	b.	Draw and explain output characteristics of CE configuration.	6	L3	CO2
	c.	For the base bias circuit, $R_c = 12K\Omega$ , $R_B = 470K\Omega$ , $V_{cc} = 20V$ and $V_{BE} = 0.7V$ . Construct the DC load line and indicate the values.	6	L3	CO2
<b>OR</b>					
Q.4	a.	Explain the construction and working of n-enhancement MOSFET.	8	L3	CO2
	b.	Explain the common base output characteristics.	8	L2	CO2
	c.	Describe how a transistor can be used as a voltage amplifier.	4	L2	CO2
<b>Module – 3</b>					
Q.5	a.	Explain the block diagram of a typical op-amp.	8	L2	C2
	b.	Explain the following terms : i) Input offset current ii) Input bias current iii) CMRR iv) Slew rate v) Input offset voltage vi) Voltage gain.	6	L2	C2

	c.	Construct an adder circuit using op-amp to obtain an output voltage of $V_0 = -[2V_1 + 3V_2 + 5V_3]$	6	L3	CO2
<b>OR</b>					
Q.6	a.	Describe an integrating amplifier using an op-amp in an inverting configuration.	8	L2	CO2
	b.	Explain basic differential amplifier using op-amp.	8	L2	CO2
	c.	List the characteristics of an ideal op-amp.	4	L2	CO2
<b>Module – 4</b>					
Q.7	a.	Explain full adder circuit with truth table. Realize the circuit for sum and carry using basic gates.	8	L2	CO3
	b.	Explain the Boolean function $F = A + \overline{B}C$ in a sum of minterms.	6	L3	CO3
	c.	Convert the following i) $(10AB)_{16} = (?)_{10}$ ii) $(240)_{10} = (?)_2$ iii) $(1234.56)_8 = (?)_{10}$	6	L2	CO3
<b>OR</b>					
Q.8	a.	Simplify the following Boolean expressions : i) $f(w, x, y, z) = x + xyz + \overline{x}yz + wx + \overline{w}x + \overline{x}y$ ii) $f = (A + \overline{B} + C)(\overline{A} + \overline{B} + C) + (\overline{A} + B)$	8	L3	CO3
	b.	Explain SOP and POS with examples.	6	L3	CO3
	c.	Implement half adder using basic gates.	6	L2	CO3
<b>Module – 5</b>					
Q.9	a.	With suitable diagram, explain working of Linear variable differential transducer.	8	L2	CO4
	b.	What is modulation? Describe the need of modulation in communication systems.	6	L2	CO4
	c.	Write short note on piezoelectric transducer.	6	L2	CO4
<b>OR</b>					
Q.10	a.	Explain the working of potentiometric resistive transducer with neat diagram.	8	L2	CO5
	b.	Explain the various blocks involved in an electrical communication systems.	6	L2	CO5
	c.	A parallel plate capacitive transducer has a plate area ( $\ell \times w$ ) = 40mm * 40mm and plate spacing ( $d$ ) = 0.5mm. Calculate the device capacitance and the displacement that causes the capacitance to change by 5pF. Also determine the transducer sensitivity.	6	L3	CO5