

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--	--

BEC302

## Third Semester B.E./B.Tech. Degree Examination, June/July 2024 Digital System Design using Verilog

Time: 3 hrs.

Max. Marks: 100

*Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.  
2. M : Marks , L: Bloom's level , C: Course outcomes.*

Module – 1			M	L	C
Q.1	a.	Define combinational logic. Give two examples.	4	L1	CO1
	b.	Explain the procedure to place a sum of products equation into canonical form. Express the function $P = f(a, b, c) = ab' + ac' + bc$ in canonical form.	6	L2	CO1
	c.	Solve the function $K = f(w, x, y, z) = \Sigma(0, 1, 4, 5, 9, 11, 13, 15)$ using Karnaugh map.	4	L2	CO1
	d.	Simplify the function $F = f(P, Q, R, S) = \Sigma m(0, 3, 5, 6, 7, 11, 14)$ using Quine-McCluskey method.	6	L2	CO1
<b>OR</b>					
Q.2	a.	Define canonical sum of products and canonical product of sums. Give examples.	4	L1	CO1
	b.	Explain the procedure to place a product of sums equation into canonical form. Explain the function $T = f(a, b, c) = (a + b')(b' + c)$ in canonical form.	6	L2	CO1
	c.	Solve the function $G = f(a, b, c, d) = \pi(0, 4, 5, 7, 8, 9, 11, 12, 13, 15)$ using Karnaugh map.	4	L2	CO1
	d.	Simplify the function $F = f(P, Q, R, S) = \Sigma m(1, 2, 3, 5, 9, 10, 12)$ using Quine-McCluskey method.	6	L2	CO1
<b>Module – 2</b>					
Q.3	a.	Define encoder. Write the truth table, equations and circuit diagram of 8 – to – 3 – line priority encoder.	4	L1	CO2
	b.	Explain the concept of carry-lookahead adder with related equations and block diagram.	6	L2	CO2
	c.	Design one-bit comparator with inputs $A_i, B_i$ – bits to be compared, $G_i, E_i, L_i$ – previous stage inputs and with the outputs $G_{i+1}, E_{i+1}, L_{i+1}$ .	6	L4	CO2
	d.	Implement the function $f(w, x, y, z) = \Sigma m(0, 1, 5, 6, 7, 9, 12, 15)$ using 8 – to – 1 – line multiplexer.	4	L3	CO2
1 of 3					

## OR

Q.4	a.	Define decoder. Write the truth table, equations and circuit diagram of 3 – to – 8 – line decoder.	4	L1	CO2
	b.	Explain the operation of 8 – to – 1 line multiplexer with block diagram, truth table, equation.	6	L2	CO2
	c.	Construct parallel binary adder/subtractor using full adder block and EX-OR gates. Also explain the operation of it.	6	L3	CO2
	d.	Design two-bit comparator using cascade connection of one-bit comparators and explain its operation.	4	L4	CO2

## Module – 3

Q.5	a.	State transparency property in latches. What is the need for master-slave flip flops?	4	L1	CO3
	b.	With neat block diagram and truth-table explain the operation of master-slave JK flipflop.	6	L2	CO3
	c.	Design a synchronous mod-6 counter using JK flipflops.	6	L4	CO3
	d.	Implement mod-4-ring counter using shift registers.	4	L3	CO3

## OR

Q.6	a.	Define register and shift register. Mention two applications of shift registers.	4	L1	CO3
	b.	With logic diagram and timing diagram explain the operation of positive edge triggered D-flip flop.	6	L2	CO3
	c.	Design a four-bit binary ripple up-counter with logic diagram and counting sequence and briefly explain its operation.	6	L4	CO3
	d.	Implement Mod-8 twisted ring counter using shift registers and write the count sequence.	4	L3	CO3

## Module – 4

Q.7	a.	List the different relational operators available in verilog language.	4	L1	CO4
	b.	Explain different verilog data types with examples.	6	L2	CO4
	c.	For the circuit diagram shown in Fig.Q.7(c), develop a verilog program for the output Y in: i) data flow description ii) behavioral description.	6	L3	CO4

 


Fig.Q.7(c)

	<b>d.</b>	Develop a verilog program to implement $2 \times 1$ multiplexer using conditional operator. Also write the truth table of $2 \times 1$ multiplexer.	4	L4	CO4
<b>OR</b>					
<b>Q.8</b>	<b>a.</b>	List the different styles of descriptions in verilog programming.	4	L1	CO4
	<b>b.</b>	Explain verilog shift operators and arithmetic shift operators with examples.	6	L2	CO4
	<b>c.</b>	Let $A = 5'b11011$ , $B = 5'b10101$ , $C = 4'd3$ . Determine the output of the following verilog program statements: i) $d = \&A$ ii) $e = \sim^{\wedge} 4'b1011$ iii) $f = \sim(A \& (\sim B))$ iv) $g = A \parallel B$ v) $b = 3 ** 2$ vi) $i = \{2\{A\}\}$ .	6	L3	CO4
	<b>d.</b>	Develop a verilog program for half subtractor using data flow description style by providing truth table and expressions.	4	L4	CO4
<b>Module – 5</b>					
<b>Q.9</b>	<b>a.</b>	Write the verilog format of if-else statement and explain it.	4	L1	CO4
	<b>b.</b>	Explain the operation of positive triggered JK flipflop by writing verilog code using case statement and truth table.	6	L2	CO4
	<b>c.</b>	Develop a verilog behavioral description code for calculating the factorial of positive integers.	6	L3	CO4
	<b>d.</b>	Develop a verilog program for D-latch using behavioral description style by providing truth table.	4	L4	CO4
<b>OR</b>					
<b>Q.10</b>	<b>a.</b>	Write the verilog format of case statement and explain it.	4	L1	CO4
	<b>b.</b>	Explain the operation of 2-to-1-line multiplexer by writing verilog structural description program and block diagram.	6	L2	CO4
	<b>c.</b>	Develop a verilog behavioral description code for three-bit binary up counter.	6	L3	CO4
	<b>d.</b>	Develop a verilog program for half adder using structural description style by providing truth table and expressions.	4	L4	CO4

\*\*\*\*\*