

OR

- 4 a. "A dc series motor should never be run on light or no load". Justify. (03 Marks)
 b. A shunt dc generator delivers 65kW at 250V and 500rpm. $R_a = 0.015\Omega$ and $R_{sh} = 85\Omega$. Find its speed, when running as a motor taking 40kW from 240V supply. BCD = 1V/Brush. Sketch relevant circuit diagrams. (07 Marks)
 c. With a neat schematic, describe the construction and working of a dynamometer type wattmeter. (06 Marks)

Module-3

- 5 a. Show that a pure inductor is lossless. (03 Marks)
 b. Refer Fig. Q5 (b). Find the real power, reactive power and the apparent power supplied.

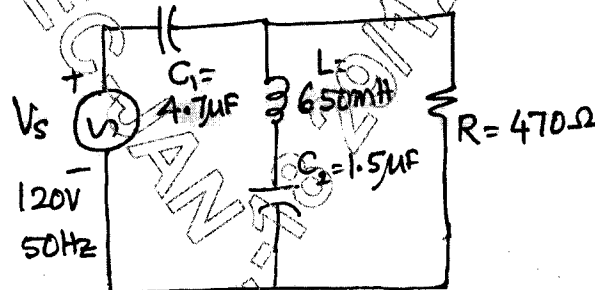


Fig. Q5(b)

(06 Marks)

- c. With a neat circuit diagram and truth table, explain the working of a 3-way control of a device. (07 Marks)

OR

- 6 a. Show that an R-C series circuit takes a leading current. Sketch a phasor diagram indicating the supply emf, the current and the two drops. (07 Marks)
 b. A resonant series circuit with $R = 5\Omega$, $L = 1\text{mH}$ and $C = 0.001\mu\text{F}$ is connected to a 100V supply. Find:
 i) the drop across L; and
 ii) drop across C. Take the supply as the reference phasor. (05 Marks)
 c. For a fuse, define i) Rated current, ii) Fusing current; and iii) Fusing factor. Why is the fusing factor greater than unity? (04 Marks)

Module-4

- 7 a. Sketch a 4-wire STAR supply and identify the phase and line voltages. With balanced supply taking $E_R = E_P \angle 0^\circ$, obtain the relationship between the phase and line voltages. Hence, sketch a phasor diagram indicating all phase and line voltages. (08 Marks)
 b. 2 wattmeters connected to measure 3 ϕ power of a balanced Δ load read 2.5 kW and 0.5 kW. Find the load pf if i) both readings are positive; and ii) the latter reading is obtained after reversing the connections of the potential coil. (04 Marks)
 c. In a 3 ϕ alternator, why is it advantageous to have the armature on the stator and the excitation on the rotor? (04 Marks)

OR

- 8 a. With a neat circuit diagram, show how 3ϕ power can be measured using two Wattmeters. State the NECESSARY CONDITION clearly. (07 Marks)
- b. A balanced Δ load of $(8+j6) \Omega$ /phase is connected to a 400V supply. Find i) the phase current ii) the line current. If the same impedances are connected in STAR, what is the reactive power consumed and at what pf? (04 Marks)
- c. A 4-pole, 3ϕ alternator driven at 1800rpm has 42 slots with 4 conductors/slot. Average flux/pole is 0.36 Wb, sinusoidally distributed. $K_p = 0.956$ and $K_d = 0.952$. Find the line voltage on no-load if connected in i) Δ ; and ii) STAR (05 Marks)

Module-5

- 9 a. Starting from expression for the efficiency of a transformer derive the condition for maximum efficiency and the expression for maximum efficiency. (05 Marks)
- b. A 135 kVA, 1ϕ transformer has primary of 2kV, 50Hz. Primary and secondary number of turns are 162 and 48 respectively. Neglecting losses, find i) no-load secondary emf; ii) full load primary and secondary currents, and iii) maximum core flux. (04 Marks)
- c. With a neat sketch, explain the working of a STAR - Δ starter, for a 3ϕ induction motor. Show that the starting inrush current is reduced by 66.7%. (07 Marks)

OR

- 10 a. "A 3ϕ induction motor can never run at N_s ". Justify (04 Marks)
- b. A single phase transformer has a maximum efficiency of 98% at 75% load, upf. The copper loss at maximum efficiency is 314W. Find its efficiency at 50% load, 0.9 pf. (04 Marks)
- c. A 6-pole, 3ϕ alternator running at 1200rpm feeds a 4-pole, 3ϕ induction motor having slips of 3% at full load and 7.5% at half load. The rotor induced emf/phase at stand still is 160V. At full load and half load, find each of the following: i) the motor speed; ii) frequency of the rotor induced emf and (iii) the rotor induced emf/phase. (08 Marks)
