

First/Second Semester B.E. Degree Examination, June/July 2013

Basic Electrical Engineering

Time: 3 hrs.

Max. Marks:100

- Note:** 1. Answer any FIVE full questions, choosing at least two from each part.
 2. Answer all objective type questions only on OMR sheet page 5 of the answer booklet.
 3. Answer to objective type questions on sheets other than OMR will not be valued.

PART – A

- 1 a. Choose the correct answer: (04 Marks)
- Ohm's law is applicable to only


A) Linear circuits	B) Non-linear circuits
C) Non-linear elements	D) None of these
 - The direction of dynamically induced emf in a conductor can be found by

A) Fleming's right hand rule	B) Fleming's left hand rule
C) Lenz's law	D) Cork screw rule
 - In parallel circuit, the potential difference across each branch remain ____

A) Different	B) Same	C) Varies with time	D) None of these
--------------	---------	---------------------	------------------
 - A coil of 500 turns is linked by a flux of 0.4 milli meter. If the flux is reversed in 0.01 sec, then the emf induced in a coil is ____

A) 20 volts	B) 30 volts	C) 40 volts	D) zero volts.
-------------	-------------	-------------	----------------
- b. The voltage drop across the 15Ω resistor in the circuit shown in Fig.Q.1(b) is 30V having the polarity indicated. Find R. (06 Marks)

Fig.Q.1(b)

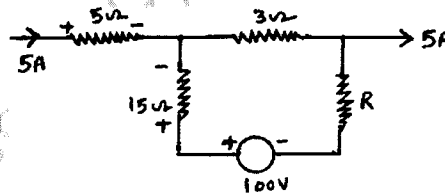

- State and explain Kirchoff's laws. (05 Marks)
 - Derive the expression for dynamically induced emf. (05 Marks)
- 2 a. Choose the correct answer: (04 Marks)
- The power factor of pure inductive circuit is ____

A) Unity	B) Zero	C) Lagging	D) Leading
----------	---------	------------	------------
 - When the frequency of the applied voltage in series RL circuit is increased, then inductive reactance will ____

A) Increase	B) Decrease	C) Becomes zero	D) Remains same
-------------	-------------	-----------------	-----------------
 - A sinusoidal voltage is represented by $v = 283 \sin 100\pi t$. Then frequency of supplied voltage is ____

A) 60 c/s	B) 40 c/s	C) 50 c/s	D) 30 c/s
-----------	-----------	-----------	-----------
 - The power factor of the ac circuit is given by ____

A) Z/R	B) R/Z	C) RZ	D) None of these
----------	----------	---------	------------------
- b. The instantaneous values of the current and voltage in ac circuit are given by $i = 28.28 \sin(314t - \pi/3)$ Amps, $v = 282.8 \sin(314t)$ volts. Find: i) RMS value of current and voltage; ii) Average value of current and voltage; iii) Frequency of supply voltage; iv) Power in the circuit. (08 Marks)
- c. A resistance of 25Ω , an inductive reactance of 20Ω and a capacitive reactance of 50Ω are all connected in parallel across 100V as supply. Calculate: i) Current in each branch; ii) Total current drawn from the supply; iii) Circuit power factor and power consumed. (08 Marks)

- 3 a. Choose the correct answer: (04 Marks)
- In a 3ϕ , 4 wire system, under balanced condition, neutral conductor carries
 - Maximum current
 - Zero current
 - Minimum current
 - Either maximum or minimum
 - In measurement of 3ϕ power by two wattmeter method, if the two wattmeter readings are equal but of opposite sign, then the power factor of the circuit is ____
 - 0.9 lag
 - 0.8 lead
 - Unity
 - Zero
 - The reactive power taken by the 3ϕ loads is given by the expression
 - $3V_L I_L \cos \phi$
 - $\sqrt{3} V_L I_L \cos \phi$
 - $\sqrt{3} V_L I_L \sin \phi$
 - $3V_L I_L \sin \phi$
 - The current coil of a wattmeter is connected in series with line is made up of
 - High resistance
 - Low resistance
 - Medium resistance
 - Very high resistance
- b. Obtain the relationship between the phase and line values of voltages and currents in a delta connected system. (08 Marks)
- c. The power input to 2000V, 50Hz, 3ϕ motor running on full load at an efficiency of 90% is measured by two watt meters which indicate 300 kW and 100 kW respectively. Calculate: i) The input; ii) The power factor; iii) The line current; iv) The output. (08 Marks)
- 4 a. Choose the correct answer: (04 Marks)
- Earthing brings the body of the equipment to
 - High potential
 - Low potential
 - Medium potential
 - Zero potential
 - The fuse can protect the electrical circuit under
 - Over loading
 - Under loading
 - No load
 - None of these
 - In a dynamometer wattmeter the fixed coil is
 - Current coil
 - Potential coil
 - Current or potential coil
 - None of these
 - The average torque acting on the aluminum disc of an energy meter is proportional to the ____ consumed by the circuit:
 - Current
 - Voltage
 - Power
 - None of these
- b. Explain with a neat diagram the working of dynamometer type wattmeter. (08 Marks)
- c. Explain the two-way position and three-way position control of lamp. (08 Marks)

PART – B

- 5 a. Choose the correct answer: (04 Marks)
- The relationship between the terminal voltage and generated emf in DC generator is ____
 - $E_g = V - I_a R_a$
 - $E_g = V + I_a R_a$
 - $E_g = V$
 - None of these
 - Brushes in DC machines made up of
 - Mica
 - Cast iron
 - Carbon
 - None of these
 - Which DC motor will be preferred for variable speed?
 - Shunt motor
 - Compound motor
 - Series motor
 - Cumulative compound motor
 - In DC machine series field winding made up of
 - Low resistance
 - High resistance
 - Very high resistance
 - None of these.
- b. An 8-pole, lap connected armature has 960 conductors, a flux of 40 mwb/pole and speed of 400 rpm. Calculate the emf generated. If the armature were wave connected, at what speed must it be driven to generate 400V? (08 Marks)
- c. Explain the characteristics of DC shunt motor. Also mention its applications. (08 Marks)

