2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8=50, will be treated as malpractice, Important Note: 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.

First/Second Semester B.E. Degree Examination, June/July 2013 Basic Electrical Engineering

Time: 3 hrs.

Max. Marks:100

Note: 1. Answer any FIVE full questions, choosing at least two from each part.

2. Answer all objective type questions only on OMR sheet page 5 of the answer booklet.

3. Answer to objective type questions on sheets other than OMR will not be valued.

PART - A

1 a. Choose the correct answers for the following:

(04 Marks)

- i) The condition for the validity under Ohm's law is that the
 - A) temperature should remain constant
 - B) current should be proportional to voltage
 - C) resistance must be wire wound type
 - D) all of the above.
- ii) A linear resister is one which obey's
 - A) Ampere's law B) Lenz's law
- C) ohms law
- D) Kirchhoff's law
- iii) The resistance of a conductor having length ℓ , area of cross section a and resistivity ρ is given as

A)
$$R = \frac{\rho a}{\ell}$$


B)
$$R = \frac{\rho \ell}{a}$$

C)
$$R = \rho \ell a$$

D)
$$R = \frac{\ell}{a\rho}$$

- iv) Resistance of a wire always increases if
 - A) temperature is reduced
 - B) temperature is increased
 - C) number of free electrons available become less
 - D) number of free electrons available become more.
- b. Find the resistance of the circuit shown (R_{AD}) .

(05 Marks)

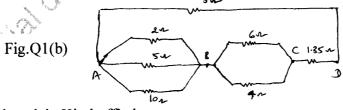

c State and explain Kirchoff's laws.

(05 Marks)

d. In the parallel arrangement of resistors shown the current flowing in the 8Ω resistor is 2.5amperes. Find i) current in other resistors ii) resistor X iii) the equivalent resistance. Refer fig. Q1(d). (06 Marks)

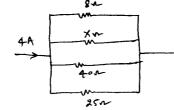


Fig.Q1(d)

2	а	Choose the correct answers for the following	, ·	(04 Marks)		
-	u.	i) The law that finds application in electroly		(04 (1141 K3)		
		A) Faraday's law B) Coulomb's law		nz's law		
		ii) According to Faraday's law of electro				
		conductor whenever it	magnetic madetion an emi is i	naacea m a		
		A) lies in a magnetic field	B) lies perpendicular to the mag	onetic field		
		C) cuts the magnetic flux	b) hes perpendicular to the mag	shelle held		
		D) moves parallel to the direction of mag	onetic field			
	f.	iii) "In all cases of electromagnetic induction, an induced voltage will cause a current to				
		flow in a closed circuit in such a direction				
that current will oppose the change that produces the current" is						
		statement of		· · · · · · · · · · · · · · · · · · ·		
		A) Lenz's law	B) Faraday's law of magnetic	e induction		
		C) Fleming's law of induction	D) Ampere's law			
		iv) Which law is synonymous to the occurre				
		A) Ampere's law B) Maxwell's law		nz's law.		
	b.	State and explain Faraday's laws of electrom		(08 Marks)		
	c.	Derive the expression for energy stored in an	- X 1 1 X	(08 Marks)		
				,		
3	a.	Choose the correct answers for the following	5 ·	(04 Marks)		
		i) The form factor is the ratio of				
		A) average value to rms value	B) rms value to average value	e		
		C) peak value to average value	D) peak value to rms value			
		ii) In an R – L series circuit the pf is				
		A) leading B) lagging	C) zero D) unit	ty ·		
		iii) The power factor of an ac circuit is equa				
		A) cosine of the angle	B) sine of the phase angle			
		C) unity for a resistive circuit	D) unity for a reactive circuit			
		iv) In a pure capacitive circuit, the current w				
		A) lag behind the voltage by 90°	B) lead the voltage by 90°			
	h	C) remain in phase with voltage Derive an expression for the impedance of	D) None of these	agistanaa an		
	υ.	η ₁ ± Δ.ν."				
inductance and a capacitance connected in series. c. 125 volts at 60Hz is applied across a capacitance connected in series				(10 Marks)		
	c.	inductive resistor. The combination carries a	-			
		96.8 w in the resistor. Power loss in the cap				
		and capacitance.	action is negligible. Calculate in	(06 Marks)		
		and capacitance.		e e e		
4	a.	Choose the correct answers for the following	; ·	(04 Marks)		
		i) In a 3 phase balanced star – connected lo	ad, neutral current is equal to			
	A) Zero B) I_P C) I_L D) Unpred					
	hase voltage of a delta connect	ed circuit is				
		$A) V_1 = V_2 \qquad B)V_2 = \sqrt{3} V_2$	$C) V_1 = V_0 \qquad D) V_2$	$=$ 2 $_{V_{-}}$		
		A) $V_L = V_P$ B) $V_L = \sqrt{3} V_P$	$\frac{1}{\sqrt{2}}$ D) $\sqrt{1}$	$\frac{-}{\pi}$ \mathbf{v}_{P}		
	is the phase					
	the phase					
		angle betweenA) line voltage and line current	B) phase voltage and phase co	urrent		
		C) line voltage and phase current	D) phase voltage and line cur			

(08 Marks)

		 iv) Three equal impedances are first connections. A) phase currents will be one - third C) power consumed will be one - third 	ected in star across the same supply B) line currents will be one - third	nced
	ć.	Derive the relationship between a line current phase voltage related to a star connected load. Mention different types of wiring used in don Explain construction and working principle of	d. (07 Ma mestic dwellings. (03 Ma	rks) irks)
			(06 Ma	
		PART -	<u>- B</u>	
5	a.	Choose the correct answers for the following		rks)
		i) The emf generated in a dc generator depe		
		A) brush contact drop	B) commutation	
		C) number of parallel paths ii) The de generator beying residual magnet	D) terminal voltage	:11
		ii) The dc generator having residual magnet be	usin gives zero induced emi, the speed	WIII
		A) zero B) very small	C) rated one D) any	
		iii) The field coils of a dc machine are made		
		A) carbon B) copper	C) mica D) steel	
		iv) The rotating part of a dc machine is calle	d the	
		A) rotor B) field	,	
	b.	The emf generated in the armature of a shunt		
		full load current of 400 A to the external c	E.F	
		armature resistance is 0.06Ω . What is the term		
	c.	A 220 volts series motor is taking a current o		
		resistance of series field is 0.25ohm. Calcula emf iii) Power wasted in armature iv)	· 11 \1 · 1	
		em m) rower wasted in armature iv)	1 Ower wasted in series field. (08 Ma	rksj
6	a.	Choose the correct answers for the following	: (04 Ma	rks)
		i) Transformer is used	And the state of t	
		A) to step up the voltage	B) to step down the voltage	
		C) on dc	D) to step up or step down the voltage	e
		ii) A transformer does not transfrom		
	4	A) power B) voltage	C) current D) impedance	
	(iii) In a transformer, electrical power is trans		
. 4	N., 2	A) through airC) through insulating medium	B) by magnetic flux D) none of these	TE .
		iv) The two windings of a transformer are	D) none of these	
*		A) conductively linked	B) inductively linked	
		C) not linked at all	D) electrically linked	
	b.	Explain principle of operation of a single	· · · · · · · · · · · · · · · · · · ·	MF
		equation.	(08 Ma	
	c.	A single phase, 20 KVA transformer has 100	00 primary turns and 2500 secondary tu	rns.
		The net cross sectional area of the core is		
		connected to 500V, 50Hz supply, calculate		

in the core ii) the voltage induced in the secondary winding and iii) the primary

and secondary full load currents.

(04 Marks)

		A) Stain steel	B) CRC _o GS	
		C) Cast iron or welded steel plates	D) Laminated silicon steel	₩ L2.
		ii) The stator core of a synchronous machine i	is laminated so as to reduce,	
ey It iz		A) Eddy current loss		
	jë 1	B) Hysteresis		
	er ²¹	C) Both eddy current and hysteresis loss		
	Comi.	D) The size and weight of the machine		(4) t
	ŝ	iii) The stator slot insulations in synchronous r	nade of,	*
		for the state of		of these
		iv) The machine that supplies dc to the rotor is A) Rectifier B) Exciter	C) Convertor D) Inver	tor
	b.	Derive EMF equation of an alternator.		(08 Marks)
	c.	Explain construction and working principle of	synchronous generator.	(08 Marks)
8	a.	Choose the correct answers for the following:		(04 Marks)
		i) If a single phase induction motor runs at a	a speed lower than the rated on	e, the most
		likely defect is,		
		A) improper size fuses		
		B) Worn-out bearings or low voltage or ov	er load	
		C) Open-circuit in the winding		
		ii) If the starting winding of a single phase inc	duction motor is left in the circu	uit,
		A) the motor will run faster		
		B) the motor will run slower		
		C) there will be undue sparking		
		D) the auxillary winding will get over-hea	ated due to continuous flow of	current and
		may get damaged.		
		iii) Which of the following types of motors are		
			B) Commutator type motors	
		in the state of th	D) Schrage motors	
		iv) Which of the following types of motors are	and the second s	
		or the control of th	B) Split phase motors	
			Repulsion start induction motors	
	b.	Explain construction and working principle of		(08 Marks)
	c.	3 1	otor? Under what circumstance	•
		i) unity and ii) zero.		(08 Marks)
				e e e e e e e e e e e e e e e e e e e

a. Choose correct answers for the following:

**** ***