

USN

--	--	--	--	--	--	--	--	--	--

06ELN15/25

First/Second Semester B.E. Degree Examination, December 2011
Basic Electronics

Time: 3 hrs.

Max. Marks:100

- Note:** 1. Answer FIVE full questions choosing at least TWO from each part.
 2. Answer all objective type questions only in OMR sheet page 5 of the Answer Booklet.
 3. Answer to objective type questions on sheets other than OMR will not be valued.

PART – A

- 1 a. Select the correct answer :
- The peak inverse voltage is the peak voltage across the diode when the diode is _____ biased.
 A) forward B) Reverse C) Unbiased D) All of these.
 - The reverse saturation current doubles at every _____ rise in temperature.
 A) 20°C B) 40°C C) 10°C D) None of these.
 - The ripple factor of full wave rectifier without filter is about
 A) 40.6 B) 0.483 C) 1.21 D) 0.812
 - The average dc voltage of a full wave rectifier is
 A) V_m/π B) $V_m/2$ C) $2V_m/\pi$ D) V_m (04 Marks)
- b. With a neat circuit diagram and relevant waveforms, explain the operation of a full wave bridge rectifier. (07 Marks)
- c. A diode with a 700 mW maximum power dissipation at 25°C has a 5 mW/°C devating factor. If the forward voltage drop remains constant at 0.7V, calculate the maximum forward current at temperatures 25°C and 65°C. (05 Marks)
- d. Define line regulation and load regulation. (04 Marks)
- 2 a. Select the correct answer :
- The arrow in the graphic symbol of a transistor defines the direction of _____ current.
 A) base B) collector C) emitter D) None of these.
 - In the cutoff region, emitter-base junction is
 A) forward biased B) reverse biased C) unbiased D) None of these.
 - The common-base current gain (α_{dc}) of a transistor is given by
 A) I_C/I_B B) I_C/I_E C) I_E/I_C D) None of these.
 - In the common-emitter configuration, I_{CEO} is given by
 A) I_{CBO} B) βI_{CBO} C) $(1 + \beta) I_{CBO}$ D) None of these. (04 Marks)
- b. Sketch the typical transistor input and output characteristics for the CE configuration. Briefly explain the three regions of operation. (07 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

- c. Explain the procedure for drawing the DC load line on the transistor CE output characteristics. In the circuit shown in Fig.Q2(c), a silicon transistor with $\beta_{dc} = 100$ is used. Draw the DC load line on output characteristics and indicate Q-point. (09 Marks)

 


Fig.Q2(c)

- 3 a. Select the correct answer :
- The Q-point will shift if _____ changes.
 A) temperature B) β_{dc} C) I_{CBO} D) All the these.
 - For the base-bias circuit, if the base current is $30 \mu A$ and β_{dc} is 100, then the value of I_C is
 A) 3 mA B) 30 mA C) $3 \mu A$ D) 100 mA.
 - The stability factor S for the base bias circuit is
 A) β B) $1/\beta$ C) $1 + \beta$ D) None of these.
 - The value of R_T in voltage divider bias circuit is
 A) $R_1 + R_2$ B) $\frac{R_1 R_2}{R_1 + R_2}$ C) $R_1 R_2$ D) None of these. (04 Marks)
- b. Sketch the circuit of voltage divider bias and discuss its approximate analysis. (08 Marks)
- c. Calculate the maximum and minimum levels of I_C and V_{CE} for the bias circuit shown in Fig.Q3(c), when $h_{FE(min)} = 50$ and $h_{FE(max)} = 200$. Assume $V_{BE} = 0.7$. (08 Marks)

 


Fig.Q3(c)

- 4 a. Select the correct answer :
- SCR is a _____ device.
 A) bidirectional B) unidirectional
 C) both unidirectional and bidirectional D) None of these.
 - _____ is the minimum current that should flow through a SCR to maintain it in the ON state.
 A) Maximum RMS current B) Gate trigger current
 C) Holding current D) None of these.

- a. iii) UJT is a three terminal device with a _____ pn-junction.
 A) double B) single C) three D) None of these.
- iv) FET is a _____ controlled device.
 A) Current B) power C) voltage D) None of these. (04 Marks)
- b. Draw the circuit diagram to show how an SCR can be triggered by application of a pulse to the gate terminal. Sketch the circuit waveforms and explain its operation. (08 Marks)
- c. Draw and explain the family of drain characteristics for a n-channel JFET. (08 Marks)

PART - B

- 5 a. Select the correct answer :
- i) Two amplifiers with voltage gains 10 and 100, are connected in cascade. The overall voltage gain is
 A) 100 B) 90 C) 1000 D) 10
- ii) To obtain the sustained oscillations in a sinusoidal oscillator, the loop gain should be equal to
 A) 1 B) ∞ C) 0 D) None of these.
- iii) For a RC phase shift oscillator, the frequency of oscillations is given by
 A) $1/2\pi RC$ B) $1/2\pi RC\sqrt{6}$ C) $1/2\pi RC\sqrt{3}$ D) None of these.
- iv) An oscillator uses _____ type of feedback.
 A) negative B) positive C) zero D) None of these. (04 Marks)
- b. Draw and explain the circuit of a two stage RC coupled common-emitter amplifier. Explain the frequency response of this amplifier. (08 Marks)
- c. Draw the circuit of a transistor Colpitt's oscillator and explain its operation. Calculate the frequency of oscillations with $C_1 = C_2 = 400$ PF and $L = 2$ mH. (08 Marks)
- 6 a. Select the correct answer :
- i) An ideal op-amp has _____ slew rate.
 A) 0 B) ∞ C) unity D) None of these.
- ii) The supply voltage or power supply rejection ratio of an ideal op-amp is
 A) ∞ B) 0 C) 1 D) None of these.
- iii) An op-amp can be used as
 A) adder B) integrator C) voltage follower D) All of these.
- iv) In an inverting amplifier, there is _____ phase shift with input and output.
 A) 90° B) 180° C) 0° D) 360° (04 Marks)
- b. Explain how an op-amp can be used as a differentiator. (04 Marks)
- c. For the circuit shown in Fig.Q6(c), calculate the output voltage. V_o . (06 Marks)

 


Fig.Q6(c)

- d. Explain how the amplitude, frequency and time period are measured using a CRO. (06 Marks)

- 7 a. Select the correct answer :
- i) $(76.6)_8 = (?)_2$
 A) $(111110.110)_2$ B) $(110110.110)_2$ C) $(111100.110)_2$ D) $(101100.100)_2$
- ii) $(15)_{10} = (?)_{BCD}$
 A) $(11010110)_{BCD}$ B) $(00010101)_{BCD}$ C) $(10010101)_{BCD}$ D) $(00100101)_{BCD}$
- iii) 2's complement of binary number 10101 is
 A) 00011 B) 01010 C) 01011 D) 10010
- iv) $(39)_{10} = (?)_2$
 A) $(100111)_2$ B) $(100110)_2$ C) $(110101)_2$ D) $(111001)_2$ (04 Marks)
- b. Explain the principle of amplitude modulation with the suitable waveforms. Derive the expression for AM wave. (08 Marks)
- c. Compare AM and FM. (04 Marks)
- d. Subtract using 2's complement:
 i) $(111001)_2 - (101011)_2$ ii) $(11010)_2 - (1010110)$ (04 Marks)
- 8 a. Select the correct answer :
- i) The basic gates are
 A) NAND and NOR B) NOT, AND and OR
 C) EXOR and EXNOR D) None of these.
- ii) $A + \bar{A}$ is
 A) A B) 0 C) 1 D) None of these.
- iii) To add $(1010)_2$ and $(1101)_2$ binary numbers, we need _____ full adders.
 A) 1 B) 2 C) 3 D) 4
- iv) The output expression for EX-OR is
 A) $A + B$ B) $A\bar{B} + \bar{A}B$ C) $\bar{A}\bar{B} + AB$ D) None of these. (04 Marks)
- b. Simplify the following Boolean expressions:
 i) $Y = (A + \bar{B} + \bar{C})(A + \bar{B} + C)$
 ii) $Y = A [B + C (AB + AC)]$ (06 Marks)
- c. Explain the operation of DTL NOR gate. (06 Marks)
- d. Realize a parallel binary adder for the following binary numbers:
 i) $(1011)_2$ ii) $(1101)_2$ (04 Marks)
