

# CBCS Scheme

USN

17ELN15

## First Semester B.E. Degree Examination, Dec.2017/Jan.2018 Basic Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing one full question from each module.

### Module-1

1. a. Explain the operation of PN junction diode under forward and reverse biased conditions, with the help of VI characteristics curve. (06 Marks)
- b. Derive the relation between  $\alpha$  and  $\beta$ . Calculate  $I_C$  and  $I_E$  for transistor that has  $\alpha_{dc} = 0.98$  and  $I_B = 100 \mu A$ . (06 Marks)
- c. With a neat circuit diagram and waveforms, explain the working of centre-tap full wave rectifier and derive the efficiency for the same. (08 Marks)

**OR**

2. a. With a neat diagram, explain the operation of PNP and NPN transistor. (08 Marks)
- b. A half wave rectifier from a supply 230 V 50 Hz with step down transformer ratio 3:1 to a resistive load of  $10 K\Omega$ . The diode forward resistance is  $75 \Omega$  and transformer secondary is  $10 \Omega$ . Calculate the DC current, DC voltage, efficiency and ripple factor. (06 Marks)
- c. With neat circuit diagram, explain the common emitter circuit and sketch the input and output characteristics. (06 Marks)

### Module-2

3. a. With a necessary equation and circuit, explain the base bias transistor circuits. (06 Marks)
- b. Design an Adder using op-amp to give the output voltage,  
$$V_o = -[2V_1 + 3V_2 + 5V_3]$$
 (06 Marks)
- c. Derive the equations for output voltage for an inverting amplifier and an integrator. (08 Marks)

**OR**

4. a. Explain the characteristics of an ideal op-amp. Mention the applications. (06 Marks)
- b. Accurately analyze the voltage divider bias which has  $V_{CC} = 18 V$ ,  $R_1 = 33 K\Omega$ ,  $R_2 = 12 K\Omega$  and  $R_E = 1 K\Omega$ . Determine  $V_E$ ,  $V_C$ ,  $V_{CE}$ ,  $I_C$  and  $Q$  point, when transistor  $h_{fe} = 200$ . (08 Marks)
- c. Write short notes on op-amp virtual ground concept. (06 Marks)

### Module-3

5. a. Perform the following:
  - i) Convert  $(57345)_{10} = (?)_{16}$  (06 Marks)
  - ii) Subtract  $(28)_{10} - (19)_{10}$  using 2's complement method. (06 Marks)
- b. Realize  $Y = AB + CD + E$  using NAND gate. (06 Marks)
- c. Explain the full adder circuit with truth table. Realize the circuit for sum and carry using logic gates. (08 Marks)

**OR**

- 6 a. Perform the following:  
 i) Convert  $(FA27D)_{16} = (\quad)_2 \rightarrow = (\quad)_8 = (\quad)_{10}$   
 ii) Subtract  $10.0101 - 101.1110$  using 1's compliment method.  
 b.  $Y = A + AB + ABC$  simplify and implement using logic gates and NOR gates.  
 c. State and prove De Morgan's theorem using two variable.
- (06 Marks)  
 (06 Marks)  
 (08 Marks)

**Module-4**

- 7 a. Bring out differences between flip flops and latches.  
 b. Explain SR flip flop with circuit diagram and truth table.  
 c. With a neat block diagram explain the architecture of 8051 microcontroller.
- (04 Marks)  
 (06 Marks)  
 (10 Marks)

**OR**

- 8 a. Explain the operation of NAND gate latch with circuit and truth table.  
 b. What is stepper motor? With a neat block diagram, explain the working principle of microcontroller based stepper motor control system.
- (10 Marks)  
 (10 Marks)

**Module-5**

- 9 a. Define communication. With neat block diagram, explain the elements of communication system.  
 b. Derive an expression for amplitude modulation and draw the necessary waveforms.  
 c. What is transducer? Compare the active and passive transducers.
- (06 Marks)  
 (08 Marks)  
 (06 Marks)

**OR**

- 10 a. Bring out the difference between amplitude modulation and frequency modulation.  
 b. If a FM wave represented by the equation  $V = 10\sin(8 \times 10^8 + 4\sin 1000t)$ , calculate:  
 i) Carrier frequency      ii) Modulating frequency  
 iii) Modulation index      iv) Band width  
 c. With necessary diagram and equations, explain the following:  
 i) Piezo-electric transducer  
 ii) LVDT.
- (06 Marks)  
 (06 Marks)  
 (08 Marks)

\* \* \* \* \*