

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17ELN15/25

## First/Second Semester B.E. Degree Examination, Dec.2019/Jan.2020 Basic Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- Define the following diode parameters :
    - Static resistance
    - Dynamic resistance
    - Reverse saturation current
    - Peak Inverse voltage
    - Knee voltage. (05 Marks)
  - With circuit diagram and neat sketch, explain the common base input and output characteristics for pnp transistor. (08 Marks)
  - A full wave rectifier with a transformer secondary voltage  $60V - 0 - 60V$ , supplies a load resistance  $R_L = 2k\Omega$ . The diode forward resistance  $R_f$  is  $10\Omega$ . Determine
    - maximum value of current in conducting diodes
    - dc value of current through  $R_L$
    - output dc voltage and
    - PIV across each diode. (07 Marks)

OR

- With a neat circuit diagram and waveforms, explain the working of Bridge rectifier. (08 Marks)
  - A 9V reference source is to use a series connected zener diode and a resistor connected to 30V supply. If zener diode with  $V_Z = 9V$ ,  $I_{ZT} = 20mA$  is selected, then determine the value of series resistance and calculate the circuit current when the supply voltage drops to 27V. (05 Marks)
  - Define Common - base current gain and Common - emitter current gain of transistor. Derive the relationship between them. If a transistor has  $I_C = 3mA$ ,  $I_E = 3.03mA$ , then find  $\beta$  of transistor. (07 Marks)

### Module-2

- With circuit diagram and necessary equations, explain the base bias circuit. (05 Marks)
  - For the voltage divider bias circuit using silicon transistor,  $V_{cc} = 18V$ ,  $R_1 = 33K\Omega$ ,  $R_2 = 12K\Omega$ ,  $R_c = 1.2K\Omega$  and  $R_E = 1K\Omega$ . Using approximate analysis, determine  $V_E$ ,  $V_C$ ,  $V_B$ ,  $I_C$  and  $V_{CE}$ . (08 Marks)
  - With a neat circuit diagram, derive an equation for output voltage of non inverting amplifier using op - amp. (07 Marks)

OR

- For the circuit shown in fig.Q4(a), find the Q - point values and draw the dc load line. The transistor has  $V_{BE} = 0.7V$  and  $\beta = 50$ . (07 Marks)

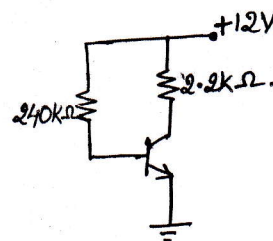
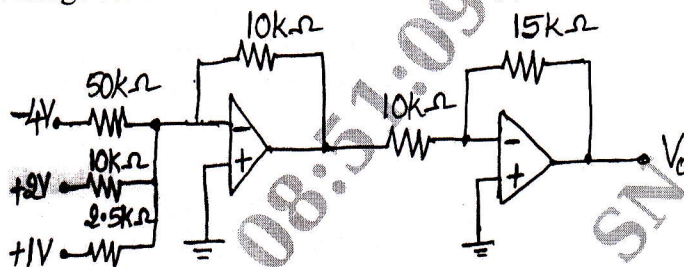


Fig.Q4(a)

- b. Mention the characteristics of ideal op – amp. (05 Marks)  
 c. Calculate the output voltage for the circuit shown in fig.Q4(c). (08 Marks)

Fig.Q4(c)

**Module-3**

- 5 a. Convert the following : i)  $(283.728)_{10} = (?)_8$ . ii)  $(AB.5E)_{16} = (?)_8$ . (06 Marks)  
 b. Simplify  $Y = \bar{A}BC + A\bar{B}C + ABC$  and then realize using  
 i) basic gates only ii) NOR gates only. (08 Marks)  
 c. Explain half adder circuit and realize using basic gates. (06 Marks)

**OR**

- 6 a. Subtract i)  $(1011)_2 - (110)_2$  using 1's complement  
 ii)  $(1001)_2 - (1110)_2$  using 2's complement. (06 Marks)  
 b. Draw the symbol and write the truth table of the exclusive – NOR gate and EX – OR gate.  
 Realize the same using basic gates also. (06 Marks)  
 c. Simplify the following Bodean expressions :  
 i)  $Y = A + \bar{A}B + ABC + A\bar{C}$  ii)  $Y = (A + \bar{B} + \bar{C})(A + \bar{B} + C)$ .  
 and realize using basic gates. (08 Marks)

**Module-4**

- 7 a. What is flipflop? Explain the operation of clocked RS flip flop. (06 Marks)  
 b. Explain the operation of NOR gate latch. (06 Marks)  
 c. With a neat block diagram, describe 8051 microcontroller. (08 Marks)

**OR**

- 8 a. Explain the operation of NAND gate latch. (05 Marks)  
 b. List the salient features of 8051 micro controller. (07 Marks)  
 c. Interface stepper motor to 8051 microcontroller with a neat block diagram. Explain its working principle, full step and half step sequence. (08 Marks)

**Module-5**

- 9 a. Explain the block diagram of communication system. (06 Marks)  
 b. The total power content of an AM wave is 2.64KW at a modulation index of 80%.  
 Determine the power content of i) carrier ii) each sideband. (04 Marks)  
 c. Write a note on i) thermistor ii) photo electric transducer. (10 Marks)

**OR**

- 10 a. Give a comparison of AM and FM. (06 Marks)  
 b. With a neat circuit diagram, explain the demodulation of AM signal. (06 Marks)  
 c. Give the classification of transducers. Also mention the desirable properties of a good transducer. (08 Marks)

\*\*\*\*\*