

--	--	--	--	--	--	--	--	--	--

**First/Second Semester B.E. Degree Examination, Dec.2015/Jan.16**  
**Basic Electronics**

Time: 3 hrs.

Max. Marks: 100

- Note:** 1. Answer any FIVE full questions, choosing at least two from each part.  
 2. Answer all objective type questions only in OMR sheet page 5 of the answer booklet.  
 3. Answer to objective type questions on sheets other than OMR sheet will not be valued.

**PART – A**

- 1 a. Choose the correct answers for the following : (04 Marks)
- Ripple factor of full wave rectifier is \_\_\_\_\_.  
 A) 1.21                      B) 0.483                      C) 0.5                      D) none of these
  - For half-wave rectified sine wave  
 A)  $I_{rms} = \frac{I_m}{2}$                       B)  $I_{rms} = \frac{I_m}{\pi}$                       C)  $I_{rms} = \frac{I_m}{\sqrt{2}}$                       D) none of these
  - Ripple factor  $\gamma$  for full wave rectifier with capacitor filter is \_\_\_\_\_.  
 A)  $\gamma = \frac{1}{2\sqrt{3}fcR_L}$                       B)  $\gamma = \frac{1}{4\sqrt{3}fcR_L}$                       C)  $\gamma = \frac{1.19}{LC}$                       D) none of these
  - A junction diode can be used as \_\_\_\_\_.  
 A) voltage regulator                      B) limiter                      C) rectifier                      D) amplifier
- b. Explain the operation of full wave rectifier with centre tap. Sketch output waveform. (06 Marks)
- c. Explain the operation of Zener regulator. (06 Marks)
- d. If the input voltage for a bridge rectifier is 50 V and each diode has a forward resistance of 25  $\Omega$ . Find the current through a load resistance of 2950  $\Omega$  and the dc voltage. (04 Marks)
- 2 a. Choose the correct answers for the following : (04 Marks)
- Current gain  $\beta =$  \_\_\_\_\_.  
 A)  $\frac{\Delta I_C}{\Delta I_E}$                       B)  $\frac{\Delta I_C}{\Delta I_B}$                       C)  $\frac{\Delta I_E}{\Delta I_B}$                       D)  $\frac{\Delta I_B}{\Delta I_C}$
  - The most widely used transistor configuration is \_\_\_\_\_.  
 A) CB                      B) CE                      C) CC                      D) none of these
  - The CB transistor is used in \_\_\_\_\_.  
 A) impedance matching                      B) high frequency applications  
 C) buffer circuit                      D) audio frequency applications
  - If  $\alpha = 0.95$ ,  $I_E = 1$  mA, the transistor base current is \_\_\_\_\_.  
 A) 0.05 mA                      B) 0.95 mA                      C) 1.0 mA                      D) 1.95 mA
- b. Explain input and output characteristics of npn transistor in common base mode. (06 Marks)
- c. Explain Quiescent point and load line with respect to transistor characteristics. Mark Active, cut offs and saturation region with respect to characteristics. (06 Marks)
- d. Given  $I_E = 2.5$  mA,  $\alpha = 0.98$  and  $I_{CBO} = 10$   $\mu$ A, calculate  $I_B$  and  $I_C$ . (04 Marks)
- 3 a. Choose the correct answers for the following : (04 Marks)
- Most widely used bias circuit is \_\_\_\_\_.  
 A) fixed bias                      B) collector to base                      C) voltage divider                      D) none of these

- ii) Power gain in decibels is equal to  
 A)  $20 \log \frac{P_{out}}{P_{in}}$       B)  $10 \log \frac{I_{out}}{I_{in}}$       C)  $20 \log \frac{V_{out}}{V_{in}}$       D) none of these
- iii) In self bias circuit  $R_E$  resistor gives \_\_\_\_\_  
 A) positive feedback      B) negative feedback  
 C) positive-negative      D) none of these
- iv) Thermal stability problem is poor in \_\_\_\_\_.  
 A) voltage divider bias      B) fixed bias  
 C) collector-to-base bias      D) none of these
- b. Explain fixed bias circuit. Mention its advantages and disadvantages. (06 Marks)
- c. Explain voltage-divider bias with neat circuit diagram. Write design formulas. (06 Marks)
- d. Give comparison of basic bias circuits. (04 Marks)
- 4 a. Choose the correct answers for the following : (04 Marks)
- i) FET is \_\_\_\_\_ device.  
 A) Bipolar      B) unidirectional      C) unipolar      D) bidirectional
- ii) SCR is \_\_\_\_\_.  
 A) amplifier      B) oscillator      C) switch      D) none of these
- iii) UJT is used as \_\_\_\_\_.  
 A) switch      B) oscillator      C) amplifier      D) rectifier
- iv) FET has high \_\_\_\_\_.  
 A) output impedance      B) input impedance      C) gain      D) none of these
- b. Explain VI characteristics of SCR. (06 Marks)
- c. Explain transfer and output characteristics of FET. (06 Marks)
- d. Explain UJT characteristics. (04 Marks)

**PART - B**

- 5 a. Choose the correct answers for the following : (04 Marks)
- i) An oscillator converts \_\_\_\_\_ energy of the desired frequency.  
 A) AC to DC      B) DC to DC      C) AC to AC      D) DC to AC
- ii) Closed loop gain of an amplifier with positive feedback is given by  
 A)  $A_f = \frac{A_v}{1 - \beta A_v}$       B)  $A_f = \frac{A_v}{1 + \beta A_v}$       C)  $A_f = \frac{1}{1 - \beta A_v}$       D)  $A_f = \frac{1}{1 + \beta A_v}$
- iii) The condition  $\beta A =$  \_\_\_\_\_ is termed as Barkhausen criterion for oscillation.  
 A) 0      B) 1      C) >1      D) <1
- iv) Wein Bridge oscillator is \_\_\_\_\_ oscillator.  
 A) video      B) audio      C) RF      D) none of these
- b. Explain the advantages of negative feedback amplifier. (06 Marks)
- c. Explain the frequency response of single-stage CE amplifier with neat circuit diagram. (06 Marks)
- d. Explain the circuit operation of crystal oscillator. (04 Marks)
- 6 a. Choose the correct answers for the following : (04 Marks)
- i) Ideally the voltage gain of an OP-AMP is \_\_\_\_\_.  
 A) 0      B) 1      C)  $\infty$       D) very high
- ii) Slew rate of OP-AMP is \_\_\_\_\_.  
 A)  $\frac{\Delta V_o}{\Delta t}$       B)  $\frac{\Delta V_o}{\Delta I_o}$       C)  $\frac{\Delta V_c}{\Delta V_i}$       D) none of these

- iii) CMRR of OP-AMP is  
 A)  $\frac{A_c}{A_d}$                       B)  $\frac{A_d}{A_c}$                       C)  $1 + \frac{A_d}{A_c}$                       D) 0
- iv) In non-inverting OP-AMP, the closed loop gain is  
 A)  $-\frac{R_F}{R}$                       B) 0                      C)  $1 + \frac{R_F}{R}$                       D)  $1 + \frac{R}{R_F}$
- b. Mention ideal characteristics of OPAMP. (06 Marks)
- c. Explain the working of OP-AMP as summer circuit. (06 Marks)
- d. Explain an OP-AMP as voltage follower. What are its special features and where it is used? (04 Marks)
- 7 a. Choose the correct answers for the following : (04 Marks)
- i) \_\_\_\_\_ is the process of getting back the modulating signal from the modulated carrier.  
 A) detection                      B) clipping                      C) modulation                      D) rectification
- ii) The total power contained in AM is \_\_\_\_\_.  
 A)  $P_T = P_C \left(1 + \frac{m^2}{2}\right)$                       B)  $P_T = \frac{P_C m^2}{2}$                       C) high                      D) none of these
- iii)  $125_8$  to binary is \_\_\_\_\_.  
 A) 001011101                      B) 001010101                      C) 001010101                      D) 001001101
- iv)  $8000_{10}$  to hexadecimal is \_\_\_\_\_.  
 A)  $1C40_{16}$                       B)  $1A40_{16}$                       C)  $1F40_{16}$                       D)  $2A40_{16}$
- b. Explain with block diagram, basic communication system. (06 Marks)
- c. Convert: (i)  $1C00_{16}$  to decimal; (ii)  $342.56_{10} = (?)_2 = (?)_8$ . (06 Marks)
- d. Use 1's complement to perform the binary subtraction (i)  $01111 - 11010$  repeat by 2's complement method. (04 Marks)
- 8 a. Choose the correct answers for the following : (04 Marks)
- i)  $A \oplus 1 =$   
 A) A                      B)  $\bar{A}$                       C) 1                      D) 0
- ii) Bubbled AND is equivalent to \_\_\_\_\_ Gate.  
 A) NOR                      B) NAND                      C) EX-OR                      D) NOT
- iii) Complement of  $A + BC$  is \_\_\_\_\_.  
 A)  $A(\bar{B} + \bar{C})$                       B)  $\bar{A}(B + C)$                       C)  $\bar{A}(\bar{B} + \bar{C})$                       D) none of these
- iv) Simplifying  $A(A + B) =$  \_\_\_\_\_.  
 A) B                      B) A                      C) AB                      D)  $\bar{A}B$
- b. Simplify  $ABC + \bar{A}BC + A\bar{B}C + ABC$ . (06 Marks)
- c. Simplify  $\overline{AB + \bar{A}\bar{B}}$  using De Morgan's theorem. (06 Marks)
- d. Write logic circuit using basic gates for the simplified expression  $\overline{(A + B)(B + C)(A + C)}$ . (04 Marks)

\*\*\*\*\*