

First/Second Semester B.E. Degree Examination, Dec.2015 / Jan.2016

Basic Electronics

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting ONE full question from each module.

Module – 1

- Draw and explain the V-I characteristics of a silicon diode. (08 Marks)
 - What is a rectifier? With a neat circuit diagram and waveforms, explain the working of full wave rectifier. (08 Marks)
 - A full wave rectifier with a load of 1 K Ω . The ac voltage applied to the diode is 200-0-200 V, if diode resistance is neglected. Calculate:
 - Average dc current;
 - Average dc voltage. (04 Marks)
- Draw and explain the input and output characteristics of common emitter configuration. (08 Marks)
 - Explain full wave rectifier with capacitor filter with necessary waveforms. (07 Marks)
 - In common emitter transistor circuit if $\beta = 100$ and $I_B = 50 \mu A$, compute the values of I_C , I_E and α . (05 Marks)

Module – 2

- With a neat circuit diagram, explain the voltage divider bias circuit by giving its exact analysis. (08 Marks)
 - For the base bias circuit for npn transistor, find I_B , I_C and V_{CE} if $R_C = 2.2 K\Omega$, $R_B = 470 K\Omega$, $V_{CC} = 18 V$, $h_{fe} = 100$. Draw the dc load line and Q point. (08 Marks)
 - What is op-amp? List the ideal characteristics of an op-amp. (04 Marks)
- Define for an op-amp (i) CMRR, (ii) Slew rate, (iii) PSRR. (06 Marks)
 - Show how an op-amp can be used as integrator. Derive an expression for its output. (06 Marks)
 - For the circuit shown in Fig.Q4(c). Calculate the output voltage.

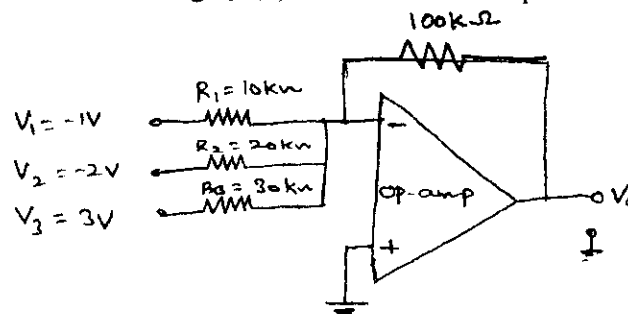


Fig.Q4(c)

- What is voltage follower? Explain. (04 Marks)

Module – 3

- Convert :
 - $(35.45)_{10} = ()_2$
 - $(475.25)_8 = ()_{10}$
 - $(3FD)_{16} = ()_2$

(06 Marks)

- b. State and prove Demorgan's theorems. (06 Marks)
- c. Show that:
- i) $\overline{ABC} + B + \overline{BD} + \overline{ABD} + \overline{AC} = B + C$
- ii) $\overline{AB} + \overline{A} + \overline{AB} = 0$
- iii) $AB + A(B + C) + B(B + C) = B + AC$ (06 Marks)
- d. What are universal gates? (02 Marks)
- 6 a. Realize two input EX-OR gate using only NAND gates. (05 Marks)
- b. Design full adder and implement it. (07 Marks)
- c. Subtract $(111001)_2$ from $(101011)_2$ using 2's complement method. (04 Marks)
- d. Realize OR gate using diodes and explain. (04 Marks)

Module – 4

- 7 a. Define flip flop. Explain R-S flip flop. (05 Marks)
- b. With neat block diagram, explain architecture of 8085 microprocessor. (10 Marks)
- c. List the difference between microprocessor and microcontroller. (05 Marks)
- 8 a. What is transducer? Distinguish between active and passive transducer. (05 Marks)
- b. With a neat sketch, explain construction and working of LVDT. (07 Marks)
- c. Explain the working of photo voltaic transducer. (08 Marks)

Module – 5

- 9 a. What is modulation? What is the need of modulation? (05 Marks)
- b. A 500 W, 1 MHz carrier is amplitude modulated with a sinusoidal signal of 1 kHz. The depth of modulation is 60%. Calculate the bandwidth, power in the sidebands and the total power transmitted. (07 Marks)
- c. Define AM. Draw the AM signal and its spectrum. Derive the necessary expressions for AM. (08 Marks)
- 10 a. With a block diagram, explain typical cellular mobile unit. (05 Marks)
- b. What is ISDN? Explain services of ISDN. (06 Marks)
- c. Explain advantages and applications of optical fibers. (05 Marks)
- d. Give the comparison between AM and FM. (04 Marks)

* * * * *