

First/Second Semester B.E. Degree Examination, July/August 2021 Basic Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions.

1.
 - a. Draw and explain the V – I – characteristics of Si – diode and Ge – diode. (06 Marks)
 - b. With neat circuit diagram, explain the working principles of full wave bridge rectifier. (06 Marks)
 - c. Calculate I_C and I_E for a transistor that has $\alpha_{dc} = 0.98$ and $I_B = 100\mu A$ and also determine the value of β_{dc} for the transistor. (04 Marks)

2.
 - a. Distinguish between Avalanche break down and Zener break down. (04 Marks)
 - b. A half wave rectifier uses a diode whose Internal resistance is 30Ω to supply power to $1.1k\Omega$ load from $110V$ (rms) source of supply. Calculate i) DC Load Voltage ii) DC Load Current iii) AC Load Current iv) Efficiency of the rectifier. (06 Marks)
 - c. Draw and explain the input and output characteristics of a transistor in common emitter configuration. (06 Marks)

3.
 - a. For the base bias circuit $V_{CC} = 18V$, $R_C = 2.2K\Omega$, $R_B = 470 K\Omega$, $\beta = 100$ and $V_{BE} = 0.7V$. Find I_B , I_C and V_{CE} . (06 Marks)
 - b. Explain the Ideal Op – Amp characteristics. (04 Marks)
 - c. Show how an Op-amp can be used as an differentiator. Derive expression for output voltage. (06 Marks)

4.
 - a. Explain Voltage divider bias circuit, with neat circuit diagram. (05 Marks)
 - b. With a neat circuit diagram and waveform, explain how Op-amp can be used as a Inverting amplifier. (06 Marks)
 - c. Determine the output voltage of the following circuit.

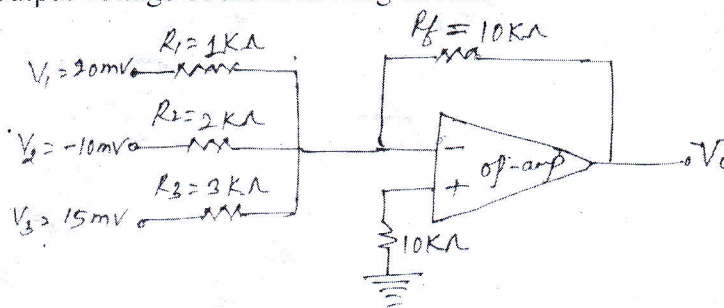


Fig. Q4(c)

(05 Marks)

5.
 - a. Convert i) $(59)_{10} = (?)_2$ ii) $(10000101)_2 = (?)_{10}$ iii) $(AEF5)_{16} = (?)_2$ iv) $(1543)_8 = (?)_{10}$. (06 Marks)
 - b. Realize the i) OR ii) AND iii) NOT gates using NAND and NOR gate only. (06 Marks)
 - c. Design a half adder circuit and realize using Basic gates. (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg. +2.8 - 50, will be treated as malpractice.

- 6 a. Factorize the following Boolean equations :
- $Y = \overline{A} \overline{B} \overline{C} \overline{D} + \overline{A} \overline{B} \overline{C} D + A \overline{B} \overline{C} \overline{D} + A \overline{B} \overline{C} D.$
 - $Y = ABC + A \overline{B} C + AB \overline{C} + \overline{A} BC.$ (06 Marks)
- b. Perform $(22 - 17)$ using 1's and 2's Complement method. (04 Marks)
- c. Draw and explain the Full adder circuit. (06 Marks)
- 7 a. What is Flip – Flop? Explain the operation of NAND – gate latch with its truth table. (04 Marks)
- b. With neat diagram, explain the architecture of 8051 micro controller. (06 Marks)
- c. Explain the working of clocked R – S Flip – flop with logic diagram and truth table. (06 Marks)
- 8 a. Explain R – S Flip – Flop using its circuit diagram, logic symbol the truth table. (06 Marks)
- b. Explain with neat diagram, Microcontroller based stepper motor control system. (06 Marks)
- c. Identify the value of Q and \overline{Q} for the Fig. Q8(c), when i) $R = S = 0$ ii) $R = S = 1$
 iii) $R = 0, S = 1$ and iv) $R = 1, S = 0.$ (04 Marks)

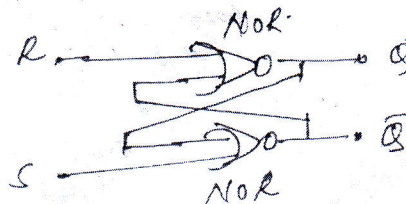


Fig.Q8(c)

- 9 a. Explain the elements of Communication system, with a neat block diagram. (06 Marks)
- b. What is Modulation? Derive the expression for Amplitude Modulation. (06 Marks)
- c. What is Transducer? Differentiate between Active and Passive transducer. (04 Marks)
- 10 a. A 500W, 1MHz carrier is amplitude modulated with a Sinusoidal signal of 1KHz. The depth of modulation is 60%. Calculate the i) Bandwidth ii) Power in the sidebands and iii) The total power transmitted. (06 Marks)
- b. Explain the working of LVDT, with neat diagram. (05 Marks)
- c. Explain the differences between Amplitude and Frequency modulation. (05 Marks)

* * * * *