

--	--	--	--	--	--	--	--	--	--

**First/Second Semester B.E. Degree Examination, June/July 2013**  
**Basic Electronics**

Time: 3 hrs.

Max. Marks:100

**Note:**

1. Answer any FIVE full questions, choosing at least two from each part.
2. Answer all objective type questions only on OMR sheet page 5 of the answer booklet.
3. Answer to objective type questions on sheets other than OMR will not be valued.

**PART – A**

- 1 a. Choose the correct answers for the following : (04 Marks)
- i) When forward – biased, a diode
 

A) blocks current	B) conducts current
C) has a high resistance	D) drops a large voltage
  - ii) The knee voltage of a Silicon diode is
 

A) 0.3 V	B) 0.5 V	C) 0.7 V	D) None of these
----------	----------	----------	------------------
  - iii) The ripple factor of half wave rectifier is about \_\_\_\_\_
 

A) 40.6	B) 0.46	C) 1.21	D) 81.2
---------	---------	---------	---------
  - iv) The rms value of a load current in case of a full wave rectifier is
 

A) $\frac{\pi}{2}$	B) $\frac{I_m}{2}$	C) $\frac{I_m}{\sqrt{2}}$	D) $\frac{I_m}{\pi}$
--------------------	--------------------	---------------------------	----------------------
- b. Deduce the following for HWR (04 Marks)
- i)  $I_{rms}$  ii)  $I_{dc}$ .
- c. With a neat circuit diagram, explain the working principles of full wave bridge rectifier. (06 Marks)
- d. Draw the circuit of full wave rectifier and show that the ripple factor = 0.48 and efficiency = 81%. (06 Marks)
- 2 a. Choose the correct answers for the following : (04 Marks)
- i) The current relationship between two current gain in a transistor is
 

A) $\beta = \frac{\alpha}{1-\alpha}$	B) $\beta = \frac{1+\alpha}{1-\alpha}$
C) $\beta = \frac{1-\alpha}{1+\alpha}$	D) $\beta = \frac{\beta+1}{\beta}$
  - ii) The  $\beta_{dc}$  of a transistor is its
 

A) current gain	B) voltage gain
C) power gain	D) internal resistance
  - iii) In a transistor the current conduction is due to \_\_\_\_\_ carries.
 

A) majority	B) minority
C) both (A) and (B)	D) None of these
  - iv) In a transistor circuit,
 

A) $I_E = I_C$	B) $I_E > I_C$	C) $I_E < I_C$	D) $I_E \ll I_C$
----------------	----------------	----------------	------------------
- b. Draw input and output characteristics of an NPN transistor in common base configuration and explain. (08 Marks)
- c. Calculate the value of  $I_C$ ,  $I_E$  and  $\beta_{dc}$  for a transistor with  $\alpha = 0.99$  and  $I_B = 110 \mu A$ . (04 Marks)
- d. Obtain the relation between ' $\alpha_{dc}$ ' and ' $\beta_{dc}$ '. (04 Marks)

- 3 a. Choose the correct answers for the following : (04 Marks)
- The intersection of a dc load line and the output characteristics of a transistor is called
    - Q – point
    - Quiescent point
    - Operating point
    - All of these
  - For an emitter follower, the voltage gain is
    - unity
    - greater than unity
    - less than unity
    - zero
  - The best biasing stability is achieved by using \_\_\_\_\_ biasing circuit.
    - fixed
    - collector to base
    - voltage divider
    - None of these
  - In self bias or emitter bias circuit \_\_\_\_\_ is connected between emitter and ground
    - inductor
    - capacitor
    - resistor
    - transformer
- b. Explain the concepts of base bias techniques using NPN transistor. (10 Marks)
- c. Calculate the Q – point values for the circuit of collector to base circuit. Given  $R_B = 100\text{ K}\Omega$ ,  $R_C = 10\text{ K}\Omega$ ,  $V_{CC} = 12\text{ V}$  and  $\beta_{dc} = 100$ . (06 Marks)

- 4 a. Choose the correct answers for the following : (04 Marks)
- A SCR has \_\_\_\_\_ number of layers
    - one
    - two
    - three
    - Four
  - The minimum point in VI characteristic of UJT is known as \_\_\_\_\_ point
    - negative
    - valley
    - latching
    - conducting
  - The FET is a \_\_\_\_\_ controlled device
    - current
    - voltage
    - power
    - None of these
  - The relaxation oscillator uses
    - MOSFET
    - SCR
    - BJT
    - UJT.
- b. Draw two transistor equivalent circuit of SCR. Also plot V – I characteristics and explain various regions of operations. (10 Marks)
- c. Explain with suitable diagram and waveforms, how UJT can be used as a relaxation oscillator. (06 Marks)

### PART – B

- 5 a. Choose the correct answers for the following : (04 Marks)
- Oscillator uses \_\_\_\_\_ type of feedback
    - positive
    - negative
    - both
    - None of these
  - A phase shift oscillator has
    - three RC circuits
    - three LC circuits
    - a T - type circuit
    - a  $\pi$  type circuit
  - The frequency of Hartley oscillator is  $f =$  \_\_\_\_\_
    - $\frac{1}{2\pi\sqrt{LC}}$
    - $\frac{1}{2\pi\sqrt{RC}}$
    - $\frac{1}{2\pi\sqrt{C}}$
    - $\frac{1}{2\pi LC}$
  - The upper and lower critical frequencies are sometimes called the
    - power frequencies
    - half power frequencies
    - 6 dB points
    - None of these
- b. Explain with a neat diagram, the working of single stage RC coupled amplifiers with its frequency response. (08 Marks)
- c. Give any four advantages of negative feedback in amplifier. (04 Marks)
- d. In a colpitts oscillator, if the desired frequency is 800 KHz, determine the values of L and  $C_{eq}$  if  $C_1 = C_2 = 10\text{ picofarad}$ . (04 Marks)

- 6 a. Choose the correct answers for the following : (04 Marks)
- The CMRR is given by \_\_\_\_  
 A)  $A_d \times A_c$       B)  $A_c / A_d$       C)  $A_d / A_c$       D)  $20 \log A_c / A_d$
  - The gain of the inverting amplifier using  $R_f = 10 \text{ K}\Omega$  and  $R_1 = 1 \text{ K}\Omega$  is \_\_\_\_  
 A) -10      B) -11      C) 10      D) 11
  - The gain of the voltage follower is \_\_\_\_  
 A) zero      B) infinite      C) negative      D) unity
  - The screen of CRT is coated with \_\_\_\_  
 A) chromium      B) phosphor      C) carbon      D) germanium
- b. Calculate the output voltage of a three input summing amplifier : Given  $R_1 = 200 \text{ K}\Omega$ ,  $R_2 = 250 \text{ K}\Omega$ ,  $R_3 = 500 \text{ K}\Omega$  and  $R_f = 1 \text{ M}\Omega$ ,  $V_1 = -2\text{V}$ ,  $V_2 = 2\text{V}$  and  $V_3 = 1 \text{ V}$ . (06 Marks)
- c. Show, how an op amp can be used as an integrator. Derive an expression for output voltage. (06 Marks)
- d. Give any four applications of CRO. (04 Marks)
- 7 a. Choose the correct answers for the following : (04 Marks)
- The modulating frequency is \_\_\_\_ carrier frequency  
 A) lower than      B) higher than      C) equal to      D) None of these
  - The modulation is done in \_\_\_\_  
 A) transmitter      B) receiver  
 C) none of the above      D) between transmitter and receiver.
  - The 2's complement of 1010 gives  
 A) 1111      B) 0110      C) 0010      D) 0101
  - In binary numbers, shifting the binary point one place to right  
 A) divides by 2      B) decreases by 10  
 C) increases by 10      D) multiplies by 2
- b. With suitable block diagram, explain the function of superheterodyne receiver. (08 Marks)
- c. Convert  $(ABCD)_{16} = ( )_2 = ( )_8 = ( )_{10} = ( )_{BCD}$ . (04 Marks)
- d. Subtract :  $(28)_{10} - (19)_{10}$  using both 1's complement and 2's complement methods. (04 Marks)
- 8 a. Choose the correct answers for the following : (04 Marks)
- When demorganis theorem applied to  $(A+B)$ , we get \_\_\_\_  
 A)  $A+B$       B)  $\bar{A}\bar{B}$       C) A      D) B
  - $Y = \bar{A}B + \bar{B}A$  is a Boolean expression for \_\_\_\_  
 A) EX - OR      B) EX - NAND  
 C) EX - NOR      D) none of these
  - The example for universal gate is \_\_\_\_  
 A) NOT      B) NOR      C) OR      D) AND
  - The expression for half adder carry 'C' with inputs 'A' and 'B' is given by  
 A)  $A+B$       B)  $AB$       C)  $\bar{A}\bar{B}$       D) none of these
- b. i) Realize the NAND gate using minimum number of NOR gates  
 ii) Simplify  $M = XYZ + X\bar{Y}Z + \bar{Z}XY$  and realize using of NOR gates. (08 Marks)
- c. Realize a full adder using two half adders and an OR gate with truth table. (08 Marks)

\* \* \* \* \*

