

- 3 b. Prove that the voltage gain for a common collector amplifier is approximately unity. (04 Marks)
- c. What is the output voltage V_{OUT} , the load current I_L , the emitter current I_{E2} , collector to emitter voltage V_{CE2} and the currents I_{R1} and I_{R2} in the circuit shown in Fig.Q3(c)? (06 Marks)

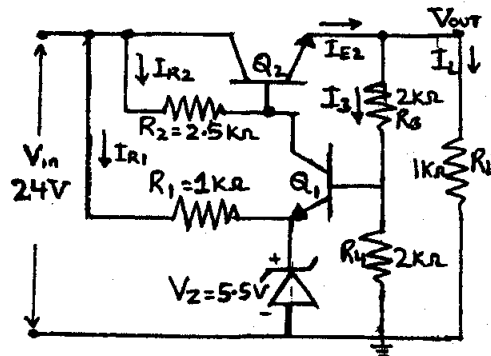


Fig.Q3(c)

- 4 a. List the important characteristics of class - A, B, AB and C amplifiers in terms of conduction angle, operating region, application and efficiency. (08 Marks)
- b. With the aid of a circuit diagram, discuss the working of class-B push-pull power amplifier along with its advantages and disadvantages. (06 Marks)
- c. Calculate the bandwidth, maximum dissipated power in the transistor and maximum output power for the tuned amplifier circuit shown in Fig.Q4(c). (06 Marks)

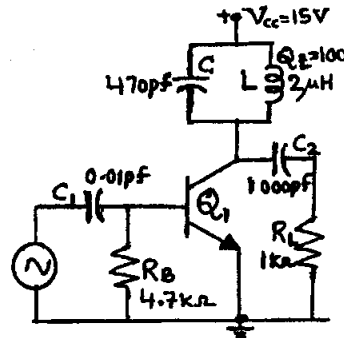


Fig.Q4(c)

PART - B

- 5 a. Draw and explain the working of D-MOSFET with the help of drain curve and transconductance curve. When a +ve voltage is applied to the gate of a P-channel D-MOSFET, is the current flow depleted or enhanced. (09 Marks)
- b. What are the major differences between D-MOSFET and E-MOSFET? What type of voltage is necessary at the gate of a P-channel E-MOSFET to cause a current flow? What are the induced carriers and where do they come from? (07 Marks)
- c. A square wave drives the gate of E-MOSFET switch shown in Fig.Q5(c). If the 10KHz square wave has peak value large enough to drive the lower MOSFET into the ohmic region, what is the output waveform? (04 Marks)

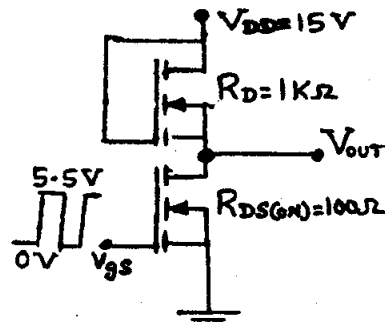


Fig.Q5(c)

- 6 a. Draw and explain the frequency response curve of an ac amplifier and the significance of cut-off frequency. Write the expression for voltage gain beyond mid band. (07 Marks)
- b. Determine the output current, current gain and load power for the LM741 OPAMP circuit shown in Fig.Q6(b). Also determine the closed-loop bandwidth for $f_{2(o)} = 120\text{Hz}$ and $(1 + A_{vol} B) = 5000$. (04 Marks)

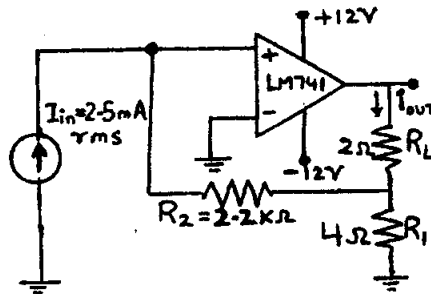


Fig.Q6(b)

- c. Draw the equivalent circuit of a trans-resistance amplifier. List down its important characteristics. Derive an expression for voltage gain of OPAMP based voltage amplifier. (09 Marks)
- 7 a. With the help of a circuit diagram, waveforms, hysteresis plot and relevant formulas, explain the working of OPAMP based Schmitt trigger. (08 Marks)
- b. With the aid of circuit pin diagram and waveforms, explain the operation of 555 timer as an ASTABLE multi vibrator to get 50% duty cycle. (07 Marks)
- c. Explain the working of RAMP generator and the importance of current mirror. (05 Marks)
- 8 a. Define locking range and capture range in PLL and its importance. Name any two applications where PLL's are used. (05 Marks)
- b. An LM317 adjustable regulator shown in Fig.Q8(b) is used for obtaining regulated DC output voltage. Calculate the approximate output voltage and the maximum, minimum efficiency, if the input voltage V_{in} varies between 30V and 48V. What would be the output voltage if R_2 value is doubled? Assume $V_{REF} = 1.25\text{V}$. (04 Marks)

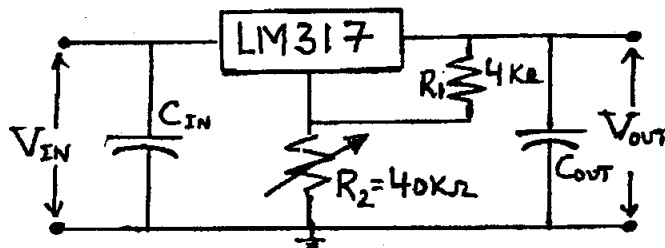


Fig.Q8(b)

- c. Explain the significance of line and load regulation. (04 Marks)
- d. With the aid of a circuit diagram, explain the working of step-up Boost regulator. (07 Marks)

12/11/11