

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, June/July 2013
Electronic Circuits

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. Explain negative clipper, with output waveforms. For the Fig. Q1 (a) show output voltages. Give the applications of clippers. (06 Marks)

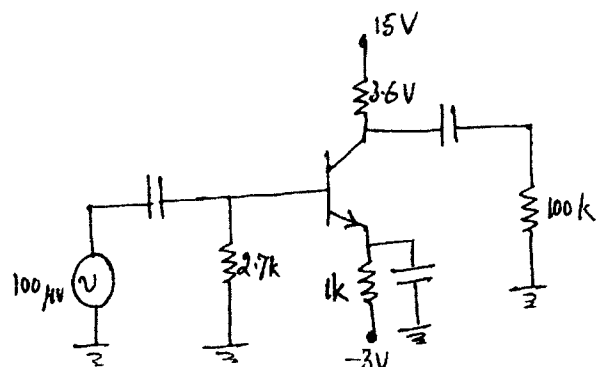
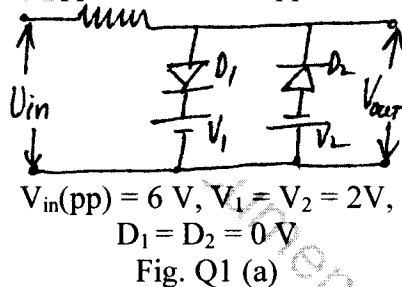


Fig. Q1 (c)

- b. What are optocouplers? Explain with diagram. (04 Marks)
- c. For the TSEB amplifier circuit (Fig. Q1 (c)), make the dc analysis and draw the waveforms at different instances of the dc values calculated. Also draw the ac equivalent T model. (10 Marks)
- 2 a. Define coupling capacitor and its importance. Using Fig. Q2 (a), if $R = 2\text{ K}\Omega$ and the frequency range is from 20 Hz to 20 kHz, find the value of C needed to act as a good coupling capacitor. (04 Marks)

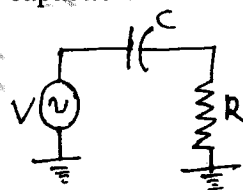


Fig. Q2 (a)

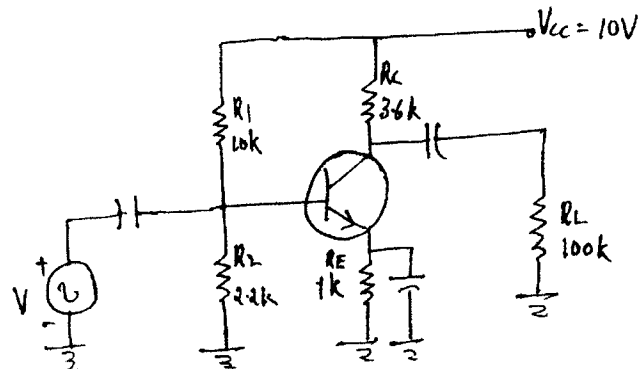


Fig. Q2 (c)

- b. Draw ac equivalent circuits for : base-biased amplifier; UDB amplifier and TSEB amplifier. (12 Marks)
- c. For the circuit of Fig. Q2 (c) show the DC circuit and AC π model. (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 3 a. What is the voltage gain in Fig. Q3 (a)? The output voltage across the load resistor? (dc emitter current is 1.1 mA) (04 Marks)

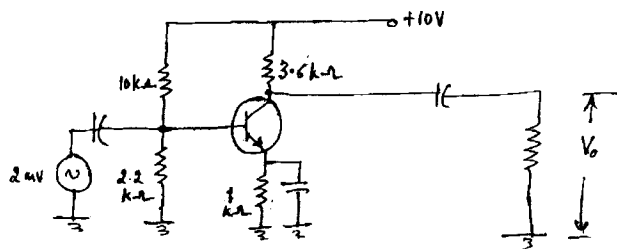


Fig. Q3 (a)

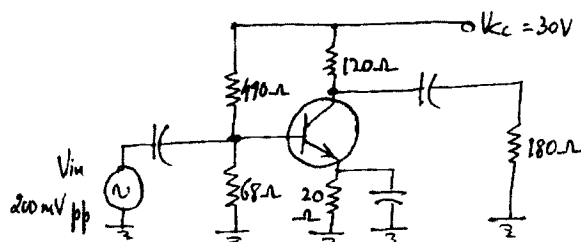


Fig. Q4 (a)

- b. With a neat diagram, explain the operation of a swamped amplifier. Draw the ac equivalent circuit. Derive the equations for voltage gain and Z_{in} (base). (10 Marks)
- c. Draw the figure of transistor voltage regulator and explain its working. (06 Marks)
- 4 a. What is the transistor power dissipation and efficiency of Fig. Q4 (a). Given : If peak to peak output voltage = 18 V. (06 Marks)
- b. With figure explain class B push-pull amplifier with advantages and disadvantages. (08 Marks)
- c. Explain about transistor power rating. (06 Marks)

PART - B

- 5 a. The D-MOSFET amplifier shown in Fig. Q5 (a) has $V_{ts(off)} = -2 V$, $I_{DSS} = 4 mA$ and $g_{mo} = 2000 \mu S$. What is the circuits output voltage? (05 Marks)

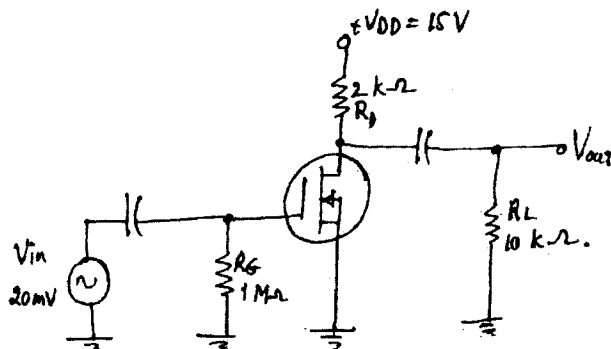


Fig. Q5 (a)

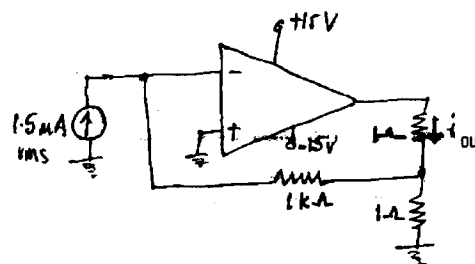


Fig. Q6 (c)

- b. Explain the operation of D MOSFET. Draw the drain and Transconductance curve. (07 Marks)
- c. With figure, explain about active-load and passive-load switching. (08 Marks)
- 6 a. Explain the frequency response of an AC amplifier with necessary figure and illustrate about cut off frequencies, mid band and outside the midband. (10 Marks)
- b. Four types of negative feedback exist. Name them with figures. (04 Marks)
- c. What is the load current and load power in Fig. Q6 (c)? If the load resistance is changed to 2Ω , what are the load current and power? (06 Marks)
- 7 a. Explain with figure inverting Schmitt trigger with hysteresis response. (06 Marks)
- b. With neat circuit diagram and output response waveform, explain relaxation oscillator. (06 Marks)
- c. Explain with figure the working of monostable operation using 555IC. (08 Marks)
- 8 a. Draw the circuit of two-transistor series regulator and explain its working. Also what is headroom voltage, power dissipation and efficiency of about circuit. (10 Marks)
- b. Explain working of series regulator with foldback current limiting circuit and show the graph of load voltage versus load current with foldback current limiting. (10 Marks)
