

USN

--	--	--	--	--	--	--	--	--	--

**Third Semester B.E. Degree Examination, June/July 2011**

**Logic Design**

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions selecting at least TWO questions from each part.**

**PART – A**

- 1 a. Explain the significance of DeMorgan's theorem. (04 Marks)
- b. Simplify the following function using k-map and design it by using NAND gates (use only four gates):  
 $f = w'xz + w'yz + x'yz' + wxy'z$  ;  $d = wyz$  (08 Marks)
- c. Define prime implicant and essential prime implicant. Find prime implicant and essential prime implicant for the following function using Quine-Mcclusky method :  
 $f(a, b, c, d) = \sum m(0, 2, 3, 6, 7, 8, 10, 12, 13)$  (08 Marks)
- 2 a. What is multiplexer? Design 4 : 1 multiplexer and implement using gates. (04 Marks)
- b. Implement the following function using decoder :  
 $F_1(A, B, C) = \sum m(0, 4, 6)$  ;  $F_2(A, B, C) = \sum m(0, 5)$  ;  $F_3(A, B, C) = \sum m(1, 2, 3, 7)$ . (08 Marks)
- c. Implement the following function using PLA :  
 $X = A'B'C + AB'C' + B'C$  ;  $Y = A'B'C + AB'C'$  ;  $Z = B'C$ . (08 Marks)
- 3 a. i) Convert the following decimal numbers into their binary equivalent :  
 A) 10      B) 15      C) 2      D) 4
- ii) Represent all the above numbers as :  
 A) Unsigned binary numbers      B) Sign magnitude numbers  
 C) 1's complement of each number      D) 2's complement of each number
- iii) Illustrate the following operators:  
 A) +67, -98 (8 bit binary addition)      B) +16, -38 (8 bit binary subtraction) (08 Marks)
- b. Explain the working principle of 2-bit fast adder with neat diagram. (08 Marks)
- c. Write HDL design of full adder. (04 Marks)
- 4 a. Draw the state transition of the circuit shown in Fig.Q4(a) : (06 Marks)

 


Fig.Q4(a)

- b. With the help of neat diagram explain the working of Master-Slave JK Flip Flop. Mention its advantages. (10 Marks)
- c. Write HDL design of D-Flip Flop. (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

## PART – B

- 5 a. Design a mod-6 synchronous upcounter using JK-Flip-Flop. (08 Marks)  
 b. Define shift register? Explain 4-bit switched tail counter with neat diagram. (08 Marks)  
 c. Design 3-bit ripple counter. (04 Marks)
- 6 a. Design a sequence detector that receives binary data stream at its input X and signals when a combination "1011" arrives at the input by masking its output Y high which otherwise remains low. Consider data is coming from left, that is, the first bit to be identified is 1, second is 1, third is 0 from input sequence. (06 Marks)  
 b. Differentiate between Mealy machine and Moore machines. (04 Marks)  
 c. Reduce state diagram shown in Fig.Q6(c) (Moore model) using following methods:  
 i) Row elimination method                      ii) Implication table method (10 Marks)

 


Fig.Q6(c)

- 7 a. Explain A/D converter by using counter method. (08 Marks)  
 b. Explain the following with neat diagram :  
 i) TTL NOR                                      ii) 2-input CMOS NOR  
 iii) TTL NAND                                      iv) 2-input CMOS NAND (12 Marks)
- 8 a. With the help of the circuit diagram explain the working of a 4-bit D/A converter. (08 Marks)  
 b. Write short notes on: (12 Marks)  
 i) Magnitude comparator  
 ii) CMOS characteristics  
 iii) Racing  
 iv) Totem pole.

\*\*\*\*\*