

--	--	--	--	--	--	--	--	--	--

**Third Semester B.E. Degree Examination, June/July 2013**  
**Logic Design**

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting  
atleast TWO questions from each part.**

**PART – A**

- 1 a. Why NAND and NOR gates are universal gates? Simplify the following Boolean expression using k – map and implement the same using
  - i) NAND gates only (SOP form)
  - ii) NOR gates only (POS form)
$$F(A, B, C, D) = \sum_m(0, 1, 2, 4, 5, 12, 14) + dc(8, 10). \quad (10 \text{ Marks})$$
- b. Find the prime implicants and essential prime implicants for the following Boolean expression using Quine McClusky's method.
 
$$F(A, B, C, D) = \sum'_m(1, 3, 6, 7, 9, 10, 12, 13, 14, 15). \quad (10 \text{ Marks})$$
- 2 a. Realize the Boolean expression
 
$$F(A, B, C, D) = \sum'_m = (2, 3, 4, 5, 13, 15) + dc(8, 9, 10, 11)$$
 using 8 : 1 multiplexers and external gates. (08 Marks)
- b. Generate the Boolean expression for
 
$$Y_0 = A' B', y_1 = ABC, y_2 = AB, y_3 = AB' C$$
 using PROM. (08 Marks)
- c. Write the HDL code for full adder. (04 Marks)
- 3 a. Design a 2 – bit carry look ahead adder and explain, with an example. (10 Marks)
- b. Draw the block diagram of 4 – bit adder/ subtractor circuit using full adder and explain the same. (05 Marks)
- c. Compute the sum in each of the following :
  - i)  $7_8 + 3_8$
  - ii)  $8_{16} + F_{16}$ .(05 Marks)
- 4 a. What is a flipflop? Explain the different types of flipflops along with truth table, circuit diagram, and excitation table. (10 Marks)
- b. Convert the SR flipflop into JK and D flipflops. (06 Marks)
- c. Write a note on edge triggered flipflops. (04 Marks)

**PART – B**

- 5 a. What is a register? Explain the types of register along with their applications. (10 Marks)
- b. Design a synchronous mod- 5 counter using JK flipflop. (05 Marks)
- c. What are presettable counters? Explain with an example. (05 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 6 a. Differentiate Mealy and Moore models. (05 Marks)  
 b. Design an asynchronous sequential logic circuit for the following state transition diagram. (05 Marks)

 


Fig. Q6(b)

- c. Draw the state transition diagram by row elimination method for the following :

 


Fig. Q6(c)

(10 Marks)

- 7 a. Draw and explain the 4-bit binary ladder D/A converter. (10 Marks)  
 b. Discuss any two methods of A/D conversion. (10 Marks)
- 8 a. Define : i) TTL parameters ii) Open – collector gate. (05 Marks)  
 b. What are CMOS characteristics? Explain. (05 Marks)  
 c. With the aid of a circuit diagram, explain the operation of a 2 – input TTL NAND gate with an open – collector method. (10 Marks)

\*\*\*\*\*