

USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

10IT35

**Third Semester B.E. Degree Examination, Dec.2017/Jan.2018**  
**Electronic Instrumentation**

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting  
atleast TWO questions from each part.**

**PART - A**

- 1 a. The expected value of the voltage across a resistor is 80V. But, the measurement gives a value of 79V. Calculate  
 (i) Absolute Error (ii) % Error (iii) Relative Accuracy (iv) % of Accuracy. (05 Marks)
- b. Fig.Q1(b) shows a series circuit of  $R_1$  and  $R_2$  connected to a 100 V dc source. If the voltage across  $R_2$  is to be measured by voltmeters having  
 (i) a sensitivity of 1 k $\Omega$ /V and (ii) a sensitivity of 20 k $\Omega$ /V  
 Find which voltmeter will read the accurate value of voltage across  $R_2$ , if both the voltmeters are used on the 50 V range. (10 Marks)

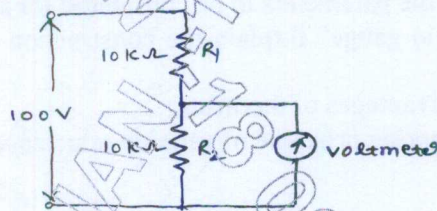


Fig.Q1(b)

- c. Draw the circuit diagram of decoupled peak voltmeter and illustrate the working principle. Mention the limitations of peak responding voltmeter. (05 Marks)
- 2 a. Discuss about the principle of operation of integrating type DVM with the help of block diagram and associated waveforms. (08 Marks)
- b. With the help of block diagram, explain how a time base with a range of 1  $\mu$ s – 1 sec can be generated using fixed frequency crystal oscillator. (05 Marks)
- c. Define the resolution and sensitivity of digital voltmeter. (04 Marks)
- d. Mention the advantages and limitations of Ramp type DVM. (03 Marks)
- 3 a. With the help of block diagram, explain the role of vertical amplifier in deciding the sensitivity and bandwidth of oscilloscope. (08 Marks)
- b. Draw the block diagram of dual beam CRO and illustrate its working principle. (07 Marks)
- c. Discuss the need for delay line in the vertical section of an oscilloscope. (05 Marks)
- 4 a. Explain the working principle of sampling oscilloscope with a neat block diagram and associated waveforms. (10 Marks)
- b. With a neat block diagram and associated waveforms explain the working principle of digital storage oscilloscope. (10 Marks)

**PART – B**

- 5 a. Draw the block diagram of modern laboratory signal generator and explain the function of its constituent blocks. (10 Marks)
- b. Specify the requirements of a pulse which can be generated using pulse generator. (03 Marks)
- c. With a neat block diagram explain how output frequency can be automatically varied over predetermined range using sweep frequency generator. (07 Marks)
- 6 a. Obtain the Thevenin's equivalent circuit of a slightly unbalanced Wheatstone's bridge. Calculate the current through the galvanometer connected between bridge output terminals if the resistance of 3 arms of the bridge is  $700 \Omega$  each and the resistance of 4<sup>th</sup> arm of the bridge is  $735 \Omega$ . (10 Marks)
- b. Derive the expression for unknown capacitance and its leakage resistance in a capacitance comparison bridge. (07 Marks)
- c. Mention the applications of Maxwell bridge and Wein bridge. (03 Marks)
- 7 a. Discuss about the parameters to be considered for any electrical transducer. (05 Marks)
- b. What is a strain gauge? Explain the construction and working principle of semiconductor strain gauge. (06 Marks)
- c. Mention the advantages of thermistor. (04 Marks)
- d. Explain the working principle of variable reluctance type transducer. (05 Marks)
- 8 a. Explain the following with respect to thermocouple:  
(i) Seebeck effect  
(ii) Thomson effect  
(iii) Thermocouple types (07 Marks)
- b. Mention the classification of display devices. (05 Marks)
- c. With a neat sketch explain how RF power can be measured using Bolometer bridge. (08 Marks)

\*\*\*\*\*