

**Third Semester B.E. Degree Examination, Aug./Sept.2020**  
**Analog Electronic Circuits**

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO full questions from each part.

**PART - A**

- 1 a. Define DC and AC resistance of a diode. Determine  $V_0$  for the circuit shown in Fig.Q.1(a). Assume diode is ideal. (07 Marks)


 


Fig.Q.1(a)

- b. For the circuit shown in Fig.Q.1(b), obtain the output voltage  $V_0(t)$  waveform and transfer characteristic plot for the input  $V_i(t) = 30\sin\omega t$ . Assume diodes are ideal. (08 Marks)


Fig.Q.1(b)

 

- c. Explain the operation of a positive clamper. (05 Marks)

- 2 a. For the Voltage-Divider bias configuration shown in Fig.Q.2(a). Determine  $I_B$ ,  $I_C$ ,  $V_{CE}$ ,  $V_C$ ,  $V_E$  and  $V_B$ . Assume  $\beta = 80$  and  $V_{BE} = 0.7V$ . (07 Marks)

Fig.Q.2(a)

 

- b. Design an Emitter stabilized network at  $I_C = \frac{1}{2} I_{C_{sat}}$  and  $V_{CEQ} = \frac{1}{2} V_{CC}$ . Use  $V_{CC} = 20V$ ,  $I_{C_{sat}} = 10mA$ ,  $\beta = 120$  and  $R_C = 4R_E$ . Assume  $V_{BE} = 0.7V$  (07 Marks)


- c. Derive the expressions for  $S(I_{CO})$ ,  $S(V_{BE})$  and  $S(\beta)$  for the fixed bias BJT configuration. (06 Marks)

- 3 a. Derive the expressions for  $Z_i$ ,  $Z_o$  and  $A_v$  for the voltage divider bias BJT configuration using  $r_e$  equivalent model. (08 Marks)

- b. Write the Hybrid equivalent model of common base configuration (for pnp transistor). (05 Marks)

- c. For the circuit shown in Fig.Q.3(c), determine  $r_e$ ,  $Z_i$ ,  $Z_o$  and  $A_v$ . Assume  $\beta = 110$  and  $V_{BE} = 0.7V_e$ . (07 Marks)

Fig.Q.3(c)

 

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

- 4 a. Derive the expression for the miller input capacitance and output capacitance. (10 Marks)  
 b. Determine the lower cutoff frequency for the circuit shown in Fig.Q.4(b) using low frequency response analysis for the following parameters  $C_S = 10\mu\text{F}$ ,  $C_E = 20\mu\text{F}$ ,  $C_C = 1\mu\text{F}$ ,  $R_S = 1\text{K}\Omega$ ,  $R_1 = 40\text{K}\Omega$ ,  $R_2 = 10\text{K}\Omega$ ,  $R_E = 2\text{K}\Omega$ ,  $R_C = 4\text{K}\Omega$ ,  $R_L = 2.2\text{K}\Omega$ ,  $\beta = 100$ ,  $r_0 = \infty$  and  $V_{CC} = 20\text{V}$ . (10 Marks)

 


Fig.Q.4(b)

**PART - B**

- 5 a. For the circuit shown in Fig.Q.5(a), calculate  $I_B$ ,  $I_E$ ,  $V_E$ ,  $V_B$ ,  $Z_i$  and  $Z_o$ . Assume  $\beta_D = 8000$ ,  $V_{BE} = 1.6\text{V}$ ,  $r_i = 5\text{K}\Omega$ ,  $V_{CC} = 18\text{V}$ . (10 Marks)

 


Fig.Q.5(a)

- b. Derive the expressions for the input impedance and output impedance of voltage-shunt feedback amplifier. (10 Marks)
- 6 a. For class B amplifier providing a 22V peak signal to a  $8\Omega$  load and a power supply of  $V_{CC} = 25\text{V}$ . Determine the input power, output power, circuit efficiency, maximum input power and maximum output power. (10 Marks)  
 b. Explain the working of series-fed class A amplifier and prove that the maximum efficiency is 25%. (10 Marks)
- 7 a. Write the circuit diagram of Wein Bridge Oscillator circuit and explain. Write the expression for frequency of oscillation. (10 Marks)  
 b. Explain BJT crystal controlled operating in parallel resonant mode. (05 Marks)  
 c. In a transistor Colpitts oscillator find the value of L for a frequency of 110kHz. Assume  $C_1 = 2\text{nF}$  and  $C_2 = 80\text{nF}$ . (05 Marks)
- 8 a. Obtain the small signal model of a MOSFET. (10 Marks)  
 b. Obtain the expression for  $Z_i$ ,  $Z_o$  and  $A_v$  of JFET fixed bias configuration. (10 Marks)

\*\*\*\*\*