

Third Semester B.E. Degree Examination, January 2013
Analog Electronic Circuits

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. Explain the diode equivalent circuit with its characteristics. (06 Marks)
- b. Explain transition and diffusion capacitance in an P-N junction diode. (06 Marks)
- c. Plot the transfer characteristic for the circuit shown in Fig. Q1(c) and write the transfer characteristic equation. Sketch V_o if $V_i = 40\sin\omega t$. Assume $V_K = 1\text{ V}$ for the diode. (08 Marks)

 


Fig. Q1 (c)

- 2 a. Define operating point. Explain its significance. (04 Marks)
- b. Derive an expression for I_B , I_C and V_{CE} for an collector feedback bias. (08 Marks)
- c. Design an emitter stabilized network shown in Fig. Q2(c) using the following data: (08 Marks)

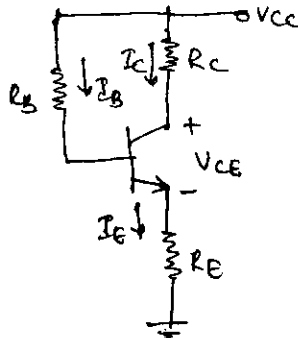


Fig. Q2 (c)

$$I_{CQ} = \frac{1}{2} I_{C(sat)}, V_{CEQ} = \frac{1}{2} V_{CC}$$

$$V_{CC} = 20\text{ V}, I_{C(sat)} = 10\text{ mA}$$

$$\beta = 120, R_C = 4R_E$$

Assume $I_E \cong I_C$

- 3 a. Derive an expression for Z_i , Z_o , A_v and A_i for common-emitter configuration using emitter bias with unbypassed R_E . (Using r_e model) (10 Marks)
- b. For the fixed bias configuration shown in Fig. Q3(b), calculate
 - i) A_{VNL} , Z_i and Z_o
 - ii) A_v , A_{VS} and A_i
 - iii) Calculate V_o , if $V_s = 20\text{ mV}$. Take $\beta = 100$ (10 Marks)

 


Fig. Q3 (b)
1 of 3

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 4 a. Derive an expression for Miller input capacitance and Miller output capacitance. (10 Marks)
 b. For the circuit shown in Fig. Q4(b), calculate the following:
- i) r_e , ii) Input resistance R_i iii) Mid band voltage gains $A_v = \frac{V_o}{V_i}$ and $A_{v_s} = \frac{V_o}{V_s}$
 iv) lower cutoff frequency due to C_C . For transistor $\beta = 100$ and $r_o = \infty$. (10 Marks)

 


Fig. Q4 (b)

PART - B

- 5 a. Explain the difference between cascade and cascode connections and its application. (05 Marks)
 b. Derive an expression for Z_i , Z_o , A_v for Darlington emitter follower. (10 Marks)
 c. Explain feed back amplifier topologies. (05 Marks)
- 6 a. With a neat circuit diagram, explain transformer coupled class A amplifier and derive the expression for AC power delivered to the load, show maximum efficiency is 50%. (10 Marks)
 b. The following readings are available for a power amplifier. Calculate the second harmonic distortion in each case:
 i) $V_{CEQ} = 10\text{ V}$, $V_{CE(max)} = 18\text{ V}$, $V_{CE(min)} = 1\text{ V}$
 ii) $V_{CEQ} = 10\text{ V}$, $V_{CE(max)} = 19\text{ V}$, $V_{CE(min)} = 1\text{ V}$ (05 Marks)
 c. For the circuit shown in Fig. Q6 (c) the input signal results in a peak base current of 1 mA
 i) Calculate the ac output power.
 ii) Calculate the dc input power dissipated by the circuit.
 iii) Calculate the efficiency. (05 Marks)

 


Fig. Q6 (c)

- 7 a. Explain the basic principle of oscillators. (06 Marks)
 b. Explain with a neat circuit diagram the operation of R-C phase shift oscillator. (08 Marks)
 c. A crystal has the following parameters:
 $L = 0.334\text{ H}$, $C = 0.065\text{ pF}$, $C_M = 1\text{ pF}$, $R = 5.5\text{ k}\Omega$
 i) Calculate the series resonant frequency.
 ii) Calculate the parallel resonant frequency.
 iii) Find the Q of the crystal. (06 Marks)

- 8 a. Derive an expression for A_v , Z_i and Z_o for an JFET source follower. (10 Marks)
- b. For the network shown in Fig. Q8 (b), $V_{GSQ} = -2.86$ V, $I_{DQ} = 4.56$ mA, $I_{DSS} = 16$ mA, $V_P = -4$ V, $Y_{OS} = 30$ μ s. Determine i) g_m ii) r_d iii) z_i and iv) z_o without r_d and v) A_v without r_d . (10 Marks)

 


Fig. Q8 (b)
