

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, June 2012

Analog Electronic Circuits

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. What is transition and diffusion capacitance? State the expressions for both and explain the terms. (06 Marks)
- b. For the diode clipping circuit shown in Fig. Q1 (b), sketch the input and output waveforms for $R = 10\text{ K}$ for $v_i = 20\sin\omega t$ and $v_R = 10\text{V}$. Assume $R_f = 100\Omega$, $R_r = \infty$ and $V_r = 0$. (06 Marks)

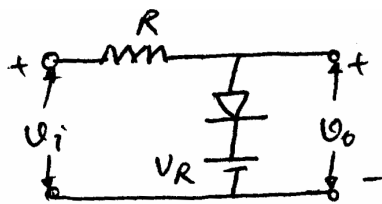


Fig. Q1 (b)

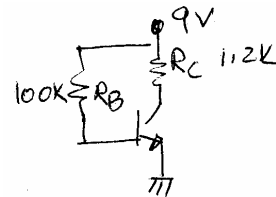


Fig. Q2 (b)

- c. What is a clamper circuit? With circuit diagram explain the working of simple negative Clamper. Also sketch the output waveform for the sinusoidal input. Also sketch positive clamper. (08 Marks)
- 2 a. Explain the factors against which an amplifier needs to be stabilized. Define the stability factor $S(I_{CO})$. Calculate ΔI_C , if $\Delta I_{CO} = 100\mu\text{A}$, $S(I_{CO}) = 5$. (06 Marks)
- b. For the circuit shown in Fig. Q2 (b), calculate I_B , I_C , I_E and V_{CE} . Assume $\beta = 45^\circ$ and $V_{BE} = 0.7$ (06 Marks)
- c. Name different biasing methods of transistor. With the circuit diagram analyze how stability is achieved by collector to base bias circuit. (08 Marks)
- 3 a. Given $I_E = 3.2\text{ mA}$, $h_{fe} = 150$, $h_{oe} = 25\ \mu\text{mho}$ and $h_{ob} = 0.5\ \mu\text{mho}$. Determine and draw
 - i) The common-emitter hybrid equivalent circuit.
 - ii) The common-base r_e model. (07 Marks)
- b. For the network shown in Fig. Q3 (b),
 - i) Determine r_e .
 - ii) Find Z_i (with $r_0 = \infty\Omega$)
 - iii) Calculate z_o (with $r_0 = \infty\Omega$)
 - iv) Determine A_v (with $r_0 = \infty\Omega$). Assume $\beta = 100$. (08 Marks)

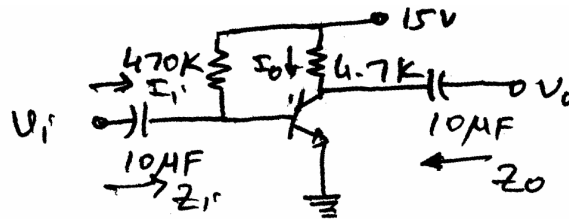


Fig. Q3 (b)

- c. Compare common emitter, common-base and common collector configured transistor amplifier with respect to impedance, voltage gain, current gain and phase shift. (05 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

- 4 a. Draw the single stage-RC coupled BJT amplifier and discuss the effect of,
 i) Input capacitor C_s ,
 ii) Emitter bypass capacitor C_e and
 iii) Output capacitor, C_c on frequency response. **(10 Marks)**
 b. Four identical non-interacting cascades stages have an overall upper 3 dB frequency of 50 kHz and a lower 3 dB frequency of 50 Hz. Determine f_L and f_H of each stage. Also find the bandwidth of each stage. **(05 Marks)**
 c. Prove that Miller effect capacitance, $C_{Mi} = (1 - A_v)C_f$ **(05 Marks)**

PART - B

- 5 a. With the help of circuit diagram discuss the importance of,
 i) Cascode connection and
 ii) Darlington connection. **(08 Marks)**
 b. Name four basic ways of connecting the feedback signal. Draw their block diagrams, indicating input and out signals, the forward and feedback path gain. **(08 Marks)**
 c. Derive an expression for input impedance of an voltage-series feedback amplifier. **(04 Marks)**
 6 a. For a power amplifier circuit shown in Fig. Q6 (a), supplied with input voltage that results in a base current of 10 mA peak. Determine the i) input power ii) output power and iii) efficiency. **(08 Marks)**

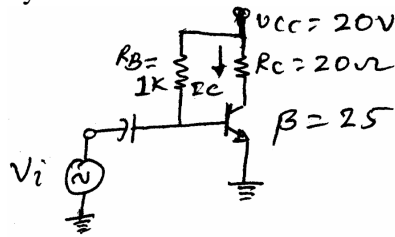


Fig. Q6 (a)

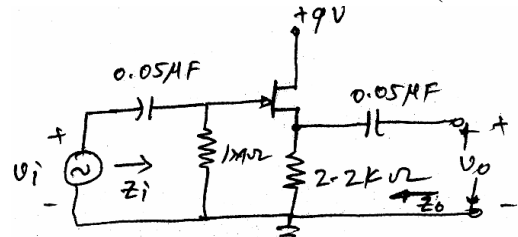


Fig. Q8 (b)

- b. Draw the transformer-coupled class A amplifier circuit and discuss
 i) Transformer action ii) Voltage transformation iii) Current transformation and
 iv) Impedance transformation in terms of turns ratio. **(08 Marks)**
 c. Write a note on amplifier distortion and harmonics in power amplifier circuits. **(04 Marks)**
 7 a. With the help of block diagram, explain the oscillator operation. **(06 Marks)**
 b. With the help of circuit diagram, explain the working of Colpits oscillator. For the circuit $C_1=C_2=C$ and $L = 100\mu H$, frequency of oscillation is 500 kHz. Determine value of C_{eQ} . **(10 Marks)**
 c. A crystal has $L = 0.4 H$, $C = 0.085 PF$ and $CM = 1 PF$ with $R = 5 K\Omega$, find
 i) Series resonant frequency
 ii) Parallel resonant frequency and
 iii) Quality factor of crystal. **(04 Marks)**
 8 a. With the help of circuit diagram of JFET self-bias configuration and its equivalent circuit derive an expression for,
 i) input impedance, Z_i
 ii) output impedance and
 iii) voltage gain, A_v
 (Assume R_s is bypassed with C_s). **(10 Marks)**
 b. The network shown in Fig. Q8 (b) has $V_{GSQ} = -2.86V$, $I_{DQ} = 4.56mA$, $I_{DSS} = 16 mA$, $V_P = -4 V$ and $Y_{OS} = 30 \mu S$. Determine i) g_m ii) r_d iii) Z_i iv) Z_o without r_d and v) A_v without r_d . **(10 Marks)**
