

Third Semester B.E. Degree Examination, June 2012

Analog Electronic Circuits


Time: 3 hrs.

Max. Marks:100


- Note: 1. Answer FIVE full questions, selecting at least TWO questions from each part.**
2. Missing data may be assumed suitably.
3. Draw equivalent circuit wherever necessary.

PART – A

 
- 1 a. Define :
 i) Transition capacitance ; ii) Diffusion capacitance ; iii) Reverse recovery time. (06 Marks)
 b. For the circuit shown in Fig.Q.1(b), sketch the output waveform and transfer characteristics for cut-in voltage = 0.7 V. (08 Marks)



 - c. Sketch the output voltage waveform for the circuit shown in the Fig.Q.1(c). Assume $S_i = 0.7 V$. (06 Marks)



- 2 a. Determine the levels of I_{CQ} and V_{CEQ} for the voltage divider configuration using the EXACT and APPROXIMATE techniques. Use $V_{CC} = 18 V$, $R_1 = 82 k\Omega$, $R_2 = 22 k\Omega$, $R_C = 5.6 k\Omega$, $R_E = 1.2 k\Omega$, $\beta = 50$. (08 Marks)
 b. For the circuit shown in Fig.Q.2(b), determine the range of possible values of V_C . Assume silicon transistor with $\beta = 200$, $V_{CC} = 15V$. (06 Marks)

 


- c. Derive an expression for the stability factor $S(\beta)$ for a collector feedback bias circuit with $R_E = 0\Omega$. (06 Marks)

- 3 a. Derive the expression for A_v , A_i , Z_i and Z_o of a voltage divider bias circuit using r_e model. (10 Marks)
 b. For the circuit shown in Fig.Q.3(b), calculate r_e , z_i , z_o , A_v , A_i , $\beta = 120$, $r_o = 40 k\Omega$ for un bypassed (R_E). (10 Marks)


Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

Fig.Q.3(b)

 

- 4 a. Use the network shown in Fig.Q.4(a). i) Determine f_{H_i} and f_{H_o} ; ii) Find $F_{(B)}$ and F_T .

Fig.Q.4(a)

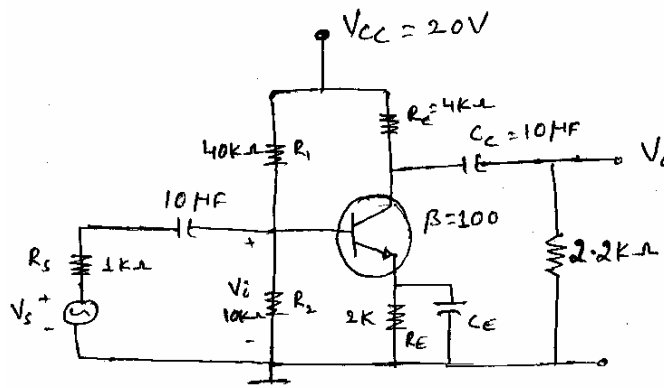


Take $C_{\pi}(c_{bc}) = 36 \text{ pF}$, $C_u(c_{bc}) = 4 \text{ pF}$, $C_{cc} = 1 \text{ pF}$, $C_{wi} = 6 \text{ pF}$, $C_{wo} = 8 \text{ pF}$, $r_o = \infty \Omega$. (12 Marks)

- b. Define f_{α} , f_{β} and f_T and state the relation between f_{β} and f_T . (08 Marks)

PART - B

- 5 a. Obtain the expression for Z_{in} , Z_o and A_v for a Darlington Emitter follower. List the advantages of Darlington Emitter follower. (10 Marks)
 b. List the general characteristics of negative feedback amplifiers. (04 Marks)
 c. Determine the voltage gain, input and output impedance with feedback for voltage series having $A = -100$, $R_i = 10 \text{ k}\Omega$ and $R_o = 20 \text{ k}\Omega$ for feedback $\beta = -0.1$. (06 Marks)
- 6 a. Explain with a neat sketches, how power amplifiers are classified. (08 Marks)
 b. With a neat circuit diagram, explain the working of a complementary symmetry class B amplifier. (08 Marks)
 c. Calculate the 2nd harmonic distortion for an O/P waveform displayed on an oscilloscope provides the following measurements : $V_{CE \text{ Min}} = 1\text{V}$, $V_{CE \text{ Max}} = 22\text{V}$, $V_{CEQ} = 12\text{V}$. (04 Marks)
- 7 a. What is Barkhausen criterion? Explain how oscillations start in an oscillator. (06 Marks)
 b. Differentiate between RC phase shift oscillator and Wein Bridge oscillator. (06 Marks)
 c. Explain with a neat circuit diagram of a Hartley oscillator. Write the expression for the frequency of oscillations. (08 Marks)
- 8 a. With necessary equivalent circuit obtain the expression for Z_i and A_v for a JFET common gate configuration. (10 Marks)
 b. Design the values of R_D and R_S for the network shown in Fig.Q.8(b) that will result in a gain of 8 using a relatively high level of g_m for this device defined at $V_{GSQ} = 1/4 V_p$. (10 Marks)

Fig.Q.8(b)

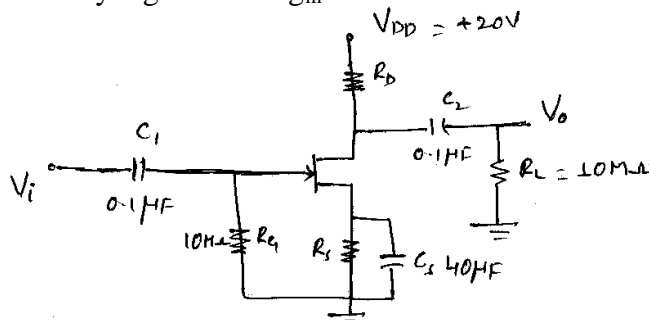

$I_{DSS} = 10\text{mA}$
 $V_p = -4\text{V}$
 $Y_{OS} = 20\mu\text{s}$
 $g_{mo} = 5\text{ms}$
