

USN

--	--	--	--	--	--	--	--	--	--

06ES32

**Third Semester B.E. Degree Examination, June/July 2011**  
**Analog Electronic Circuits**

Time: 3 hrs.

Max. Marks:100

**Note: 1. Answer any FIVE full questions, selecting at least TWO questions from each part.**  
**2. Missing data may be assumed suitably.**

**PART – A**

- 1 a. Define the following pertaining to the diode:  
i) Dynamic resistance ii) Diffusion capacitance and iii) Reverse recovery time. (06 Marks)
- b. Discuss the approximate and piecewise linear model of a diode. (06 Marks)
- c. Sketch the output voltage  $v_o(t)$  for the circuit shown in Fig.Q1(c), if  $v_i(t) = 50 \sin \omega t$ . Assume diodes  $D_1$  and  $D_2$  as ideal. (08 Marks)

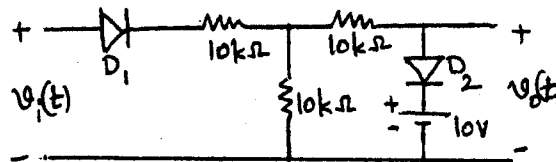


Fig.Q1(c)

- 2 a. What is biasing of a transistor? Explain the factors that affect selection of Q-point anywhere in the active region for the transistor to operate as an amplifier. (06 Marks)
- b. What is bias stabilization? Discuss the stability of the operating point against variation in its parameters. (06 Marks)
- c. Design a voltage divider bias circuit for the following specifications:  
 $V_{CC} = 15 \text{ V}$ ,  $V_{CE} = 7.5 \text{ V}$ ,  $I_C = 2 \text{ mA}$ ,  $S(I_{CO}) \leq 15$ ,  $\beta = 100$  and  $V_E = 1.5 \text{ V}$ . (08 Marks)
- 3 a. For the CE amplifier circuit derive the expression for  $A_I$ ,  $Z_i$ ,  $A_V$  and  $Y_o$  in terms of transistor h-parameters. (10 Marks)
- b. For the circuit shown in Fig.Q3(b), find  $A_I$ ,  $R_i$ ,  $A_V$  and  $Z_o$ . The transistor h-parameters are  $h_{ie} = 1 \text{ k}\Omega$ ,  $h_{re} = 2 \times 10^{-4}$ ,  $h_{fe} = 85$  and  $h_{oe} = 2 \mu\text{S}$ . (10 Marks)

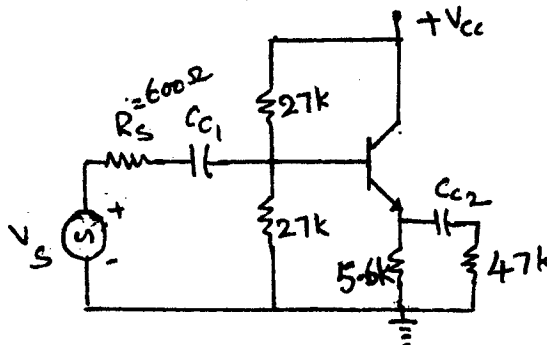


Fig.Q3(b)

- 4 a. Derive the expression for Miller's effect capacitances. (06 Marks)
- b. Derive the expression for overall lower and higher cut off frequencies of multistage amplifier. (06 Marks)
- c. At  $I_C = 1 \text{ mA}$  and  $V_{CE} = 10\text{V}$ , a certain transistor data shows  $C_c = C_{b'c} = 3 \text{ pF}$ ,  $h_{fe} = 200$  and  $\omega_t = -500 \text{ mrad/sec}$ . Calculate  $g_m$ ,  $r_{b'e}$ ,  $C_{b'e}$  and  $\omega_\beta$ . (08 Marks)

Important Note : 1. On completing your answers, carefully draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

## PART - B

- 5 a. What is an emitter follower circuit? Discuss Darlington emitter following circuit. (08 Marks)
- b. Fig.Q5(b) shows a circuit schematic of a feedback amplifier for which the parameters are  $A = -2000$ ,  $\beta = 1/150$ ,  $R_s = R_E = 1 \text{ k}\Omega$ ,  $R_C = 3 \text{ k}\Omega$ ,  $h_{ie} = 2 \text{ k}\Omega$ ,  $h_{fe} = 200$  and  $h_{re} = h_{oe} = 0$ . Show that  $v_i = -200 [V_s - V_f]$ . Calculate  $A_{V_f} = \frac{V_o}{V_s}$  (12 Marks)

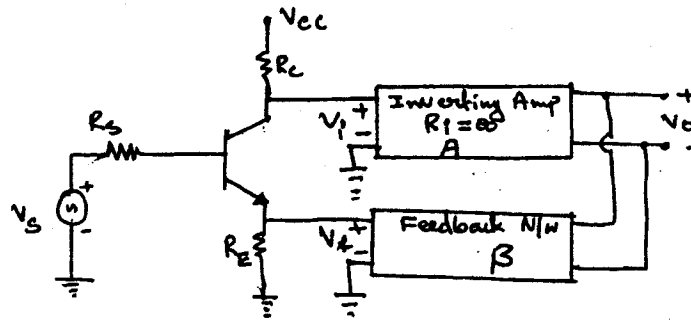


Fig.Q5(b)

- 6 a. Explain the operation of transformer coupled class A power amplifier. (06 Marks)
- b. Show that maximum efficiency of the push pull class B power amplifier circuit is 78.5%. (06 Marks)
- c. A complementary symmetry push pull amplifier is operated using  $V_{CC} = \pm 10\text{V}$  and deliver power to a load  $R_L = 5 \Omega$ . Calculate i) Maximum power output ii) Power rating of transistors iii) DC input at maximum power output. (08 Marks)
- 7 a. Obtain the Brakhausem criterion for operation of the oscillator using basic feedback circuit and hence, explain the operation of the oscillator. (08 Marks)
- b. With neat circuit diagram, explain the operation of tuned oscillator. (06 Marks)
- c. A crystal has  $L = 2\text{H}$ ,  $C = 0.01 \text{ pF}$  and  $R = 2 \text{ k}\Omega$ . Its mounting capacitance is  $2 \text{ pF}$ . Calculate its series and parallel resonating frequency. (06 Marks)
- 8 a. Explain the small signal model of the FET. (04 Marks)
- b. Derive the expression for  $Z_i$ ,  $Z_o$  and  $A_v$  for FET Self biased configuration (with  $R_s$  bypassed) (06 Marks)
- c. For the Fig.Q8(c),  $V_{GS} = -2.86\text{V}$  and  $I_D = 4.56 \text{ mA}$ , find i)  $g_m$  ii)  $r_d$  iii)  $Z_i$  iv)  $Z_o$  and v)  $A_v$ . Assume  $I_{DSS} = 16 \text{ mA}$ ,  $V_p = -4\text{V}$  and  $y_{os} = 25 \mu\text{S}$ . (10 Marks)

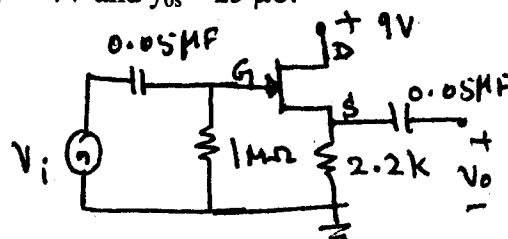


Fig.Q8(c)

\*\*\*\*\*