

--	--	--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, June / July 2014
Analog Electronic Circuits

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. Explain the stray capacitance of a diode at high frequency when it is (i) Forward biased and (ii) Reverse biased. (04 Marks)
- b. In the circuit shown in Fig. Q1 (b) when the input varies linearly from 0 to 150 volts, sketch the output voltage to the time scale assuming the ideal diodes. (08 Marks)

 


Fig. Q1 (b)

- c. Explain the working of circuit shown in Fig. Q1 (c) and also sketch the output waveform. Also calculate the value of resistance R required to have a time constant equal to five times the product of RC during the discharge period. Given $V_r = 0.7$ volt for Si diode. (08 Marks)

 


Fig. Q1 (c)

- 2 a. Find the quiescent collector current I_C and voltage V_{CE} for the circuit shown in Fig. Q2 (a) using exact analysis. Assume $V_{BE} = 0.7$ volt and $B = 80$. (08 Marks)

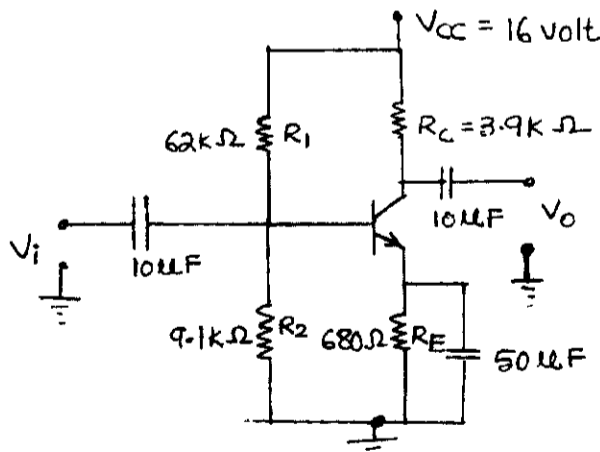


Fig. Q2 (a)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

- 2 b. Derive the expression for the stability factor $S_{(I_{CO})}$, $S_{(V_{BE})}$ and $S_{(B)}$ for the fixed bias circuit. (06 Marks)
- c. Determine the value of R_B and R_C for the circuit shown in Fig. Q2 (c). Given $V_{BE} = 0.7$ volt and $I_{C_{sat}} = 20$ mA. Select the base current I_B , 50% more to ensure saturation. (06 Marks)

 


Fig. Q2 (c)

- 3 a. Find Z_i , Z_o , A_v and A_i for the common base circuit shown in Fig. Q3 (a) using approximate hybrid model. (10 Marks)

 


Fig. Q3 (a)

- b. For the network shown in Fig. Q3 (b) determine the following parameters using complete hybrid equivalent model:
 (i) Z_i and Z'_i (ii) Voltage gain A_v (iii) Current gain A_i (iv) Z_o . (10 Marks)

 


Fig. Q3 (b)

Given $h_{fe} = 110$, $h_{ie} = 1.6$ K Ω , $h_{re} = 2 \times 10^{-4}$, $h_{oe} = 20 \mu A/volt$

- 4 a. Describe the Miller effect capacitance and derive an equation for Miller input and output capacitances. (06 Marks)
- b. Three amplifiers with voltage gain 10, 100 and 1000 are connected in cascade. Find
 (i) The overall voltage gain in dB.
 (ii) The output voltage when the input voltage is 1 μV . (04 Marks)

- 4 c. Determine the lower cut off frequency f_{LS} for the network shown in Fig. Q4 (c).
 Given : $V_{CC} = 20\text{ V}$, $r_0 = \infty$, $B = 100$, $R_E = 2\text{ K}\Omega$, $R_C = 4\text{ K}\Omega$, $R_L = 2.2\text{ K}\Omega$. (10 Marks)

 


Fig. Q4 (c)

PART - B

- 5 a. For the two stage cascade amplifier shown in Fig. Q5 (a), determine
 (i) The loaded voltage gain of each stage.
 (ii) The total gain of the system A_V and A_{VS} .
 (iii) The loaded current gain at each stage. (08 Marks)

 


Fig. Q5 (a)

- b. Draw the current series feedback circuit and derive an expression to find the output impedance. (06 Marks)
- c. What is negative feedback and write the advantages of negative feedback? (06 Marks)
- 6 a. Explain the working of a series fed class A power amplifier and also derive an expression to find the max efficiency of the amplifier. (08 Marks)
- b. A class B push pull amplifier with $V_{CC} = 25\text{ volt}$ driving a $8\ \Omega$ load find,
 (i) Maximum input power.
 (ii) Maximum output power.
 (iii) Maximum circuit efficiency.
 (iv) Maximum collector dissipation. (08 Marks)
- c. What is cross over distortion and how it can be eliminated? (04 Marks)
- 7 a. What is an oscillator? Explain the Bark hausen criterion for sustained oscillations. (04 Marks)
- b. A quartz crystal has $L = 3\text{ Henry}$, $C = 0.05\text{ pf}$, $R = 2\text{ K}\Omega$ and $C_M = 10\text{ pf}$. Find the series and parallel resonance frequency. (06 Marks)
- c. Draw the circuit diagram of a Weinbridge oscillator and write the expression to calculate frequency of oscillation and loop gain. (05 Marks)
- d. In a collpitts oscillator $C_1 = 100\text{ pF}$ and $C_2 = 60\text{ pF}$, find the value of inductor L if the frequency of oscillation required is 50 KHz . (05 Marks)

- 8 a. Draw the ac equivalent for the network shown in Fig. Q8 (a) using small signal ac model and find (i) Input impedance Z_i (ii) Output impedance Z_o (iii) Voltage gain A_v .
(10 Marks)

 


Fig. Q8 (a)

- b. For the JFET in common drain configuration shown in Fig. Q8 (b), calculate
(i) The input impedance Z_i .
(ii) Output impedance Z_o .
(iii) Find V_o if $V_i = 20$ m volt (p-p)
Given : $I_{DSS} = 10$ mA, $V_p = -5$ volt, $r_d = 40$ K Ω , $V_{GSQ} = -2.85$ volt
(10 Marks)

 


Fig. Q8 (b)
