

CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15EC32

Third Semester B.E. Degree Examination, June/July 2017 Analog Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Draw r_e and h-parameter models of a transistor in common – emitter configuration. Also give relation between r_e and h-parameter (05 Marks)
- b. Draw the emitter follower circuit. Derive expressions for i) Z_i ii) Z_o iii) A_v using r_e model. (06 Marks)
- c. Draw and explain the hybrid- π model of transistor in CE configuration mentioning significance of each component in model. (05 Marks)

OR

- 2 a. Derive expressions for Z_i , Z_o , A_v and A_i for common–emitter fixed bias configuration using hybrid equivalent model. (08 Marks)
- b. For the circuit shown below, taking $r_o = \infty\Omega$ calculate i) r_e ii) Z_i iii) Z_o iv) A_v . (08 Marks)

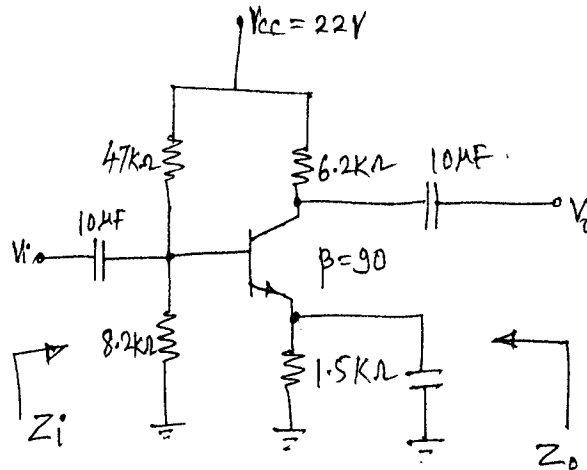


Fig.Q2(b)

Module-2

- 3 a. With circuit diagram of JFET small signal model, determine g_m and r_d . (08 Marks)
- b. For the JFET common-source amplifier using fixed-bias configuration. Derive expressions for Z_i , Z_o and A_v using AC equivalent circuit. (08 Marks)

Important Note - 1 On completing your answers compulsorily draw diagonal cross lines on the remaining blank pages.

OR

- 4 a. For the JFET common-gate configuration shown below, calculate Z_i , Z_o and A_v . (08 Marks)

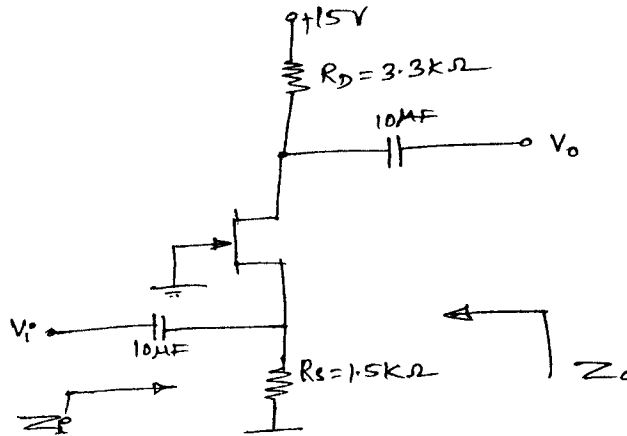


Fig.Q4(a)

- b. With neat diagram, explain construction of n-channel JFET, and also draw its characteristics. (08 Marks)

Module-3

- 5 a. Describe Miller-effect and derive an equation for miller input and output capacitance. (08 Marks)
 b. Discuss low frequency response of BJT amplifier and give expressions for low frequency due to input coupling capacitor C_S and output coupling capacitor C_C . (08 Marks)

OR

- 6 a. Explain high-frequency response of FET amplifier, and derive expression for cutoff frequencies defined by input and output circuits (f_{iH} and f_{iO}). (08 Marks)
 b. For the circuit shown.

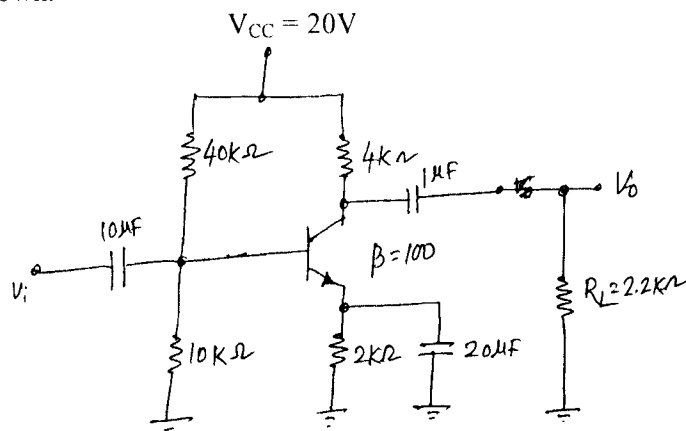


Fig.Q6(b)

$r_0 = \infty\Omega$, $C_{\pi}(cbe) = 36\text{pF}$, $C_u(cbc) = 4\text{pF}$, $C_{cc} = 1\text{pF}$, $C_{wi} = 6\text{pF}$, $C_{wo} = 8\text{pF}$

- i) determine f_{iH} and f_{iO}
 ii) find f_{β} and f_T .

(08 Marks)

Module-4

- 7 a. What is Barkhausen criterion? Explain how oscillations start in an oscillator. (04 Marks)
 b. With the help of a neat circuit diagram, explain transistor colpitts oscillator. Write the expression for frequency of oscillations. (08 Marks)
 c. A quartz crystal has $L = 0.12\text{H}$, $C = 0.04\text{ pF}$, $C_M = 1\text{ pF}$ and $R = 9.2\text{ k}\Omega$, Find :
 i) series resonant frequency ii) Parallel resonant frequency. (04 Marks)

OR

- 8 a. Explain characteristics of a quartz crystal. With a neat diagram explain the crystal oscillator in parallel resonant mode. (08 Marks)
 b. The following component values are given for the Wein-bridge oscillator of the circuit of $R_1 = R_2 = 33\text{k}\Omega$, $C_1 = C_2 = 0.001\text{ }\mu\text{F}$, $R_3 = 47\text{ k}\Omega$, $R_4 = 15\text{k}\Omega$.
 i) Will this circuit oscillate?
 ii) Calculate the resonant frequency. (08 Marks)

Module-5

- 9 a. Explain series – fed class – A power amplifier. Show that its maximum conversion efficiency is 25%. (08 Marks)
 b. Explain with circuit diagram the operation of Class-B push-Pull amplifier using complementary–symmetry transistor pair. Also mention advantages and disadvantages of the circuit. (08 Marks)

OR

- 10 a. An ideal class –B push-pull power amplifier with input and output transformers has $V_{CC} = 20\text{V}$, $N_2 = 2N_1$ and $R_L = 20\Omega$. The transistors has $h_{fe} = 20$. Let the input be sinusoidal. For the maximum output signal at $V_{CE(P)} = V_{CC}$, determine :
 i) The output signal power
 ii) The collector dissipation in each transistor
 iii) Conversion efficiency. (08 Marks)
 b. The following distortion readings are available for a power amplifier, $D_2 = 0.2$, $D_3 = 0.02$, $D_4 = 0.06$, with $I_1 = 3.3\text{A}$ and $R_C = 4\Omega$.
 i) Calculate the total harmonic distortion
 ii) Determine the fundamental power component
 iii) Calculate the total power. (08 Marks)

* * * * *