

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, Jan./Feb.2021 Analog Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. With necessary equivalent diagram obtain the expression for Z_{in} , A_v , Z_o for Darlington Emitter follower. (10 Marks)
- b. For an Emitter bias circuit (capacitor bypassed), determine r_e , Z_i , Z_o and A_v . Given $R_B = 470 \text{ K}\Omega$, $R_C = 2.2 \text{ K}\Omega$, $V_{CC} = 20 \text{ V}$, $R_E = 0.56 \text{ K}\Omega$, $C_E = 10 \mu\text{F}$, $\beta = 120$, $r_o = 40 \text{ K}\Omega$, $C_c = 10 \mu\text{F}$. (06 Marks)

OR

- 2 a. Derive the expression for A_v , A_i , Z_i and Z_o for C_E fixed bias configuration using complete hybrid equivalent model. (10 Marks)
- b. Consider a single stage CE amplifier with $R_S = 1 \text{ K}$ and $R_L = 1.2 \text{ K}\Omega$. Calculate A_i , R_i , A_v , A_{is} , if $h_{ie} = 1.1 \text{ K}$, $h_{re} = 2.5 \times 10^{-4}$, $h_{fe} = 50$ and $h_{oe} = 25 \mu\text{A/V}$. (06 Marks)

Module-2

- 3 a. Derive the expression for transconductance g_m for FET. (06 Marks)
- b. For the circuit shown in the Fig. Q3 (b), calculate (a) V_{GS} (b) I_{DQ} (c) V_{DSQ} (d) V_D . (10 Marks)

 


Fig. Q3 (b)

OR

- 4 a. With necessary equivalent circuit obtain the expression for A_v , Z_{in} , Z_o for a fixed biased JFET amplifier. (08 Marks)
- b. Derive the expression for Z_i , Z_o , A_v considering common drain amplifier circuit. (08 Marks)

Module-3

- 5 a. Derive the expression for lower cut-of frequencies due to various RC networks in CE amplifiers. (10 Marks)
- b. Determine the lower cut-off frequency for the emitter follower using BJT amplifier with $C_s = 0.1 \mu\text{F}$, $R_s = 1 \text{ K}\Omega$, $R_1 = 12 \text{ K}\Omega$, $R_2 = 4 \text{ K}\Omega$, $R_E = 1.5 \text{ K}\Omega$, $C_C = 0.1 \mu\text{F}$, $\beta = 100$, $r_o = \infty$, $V_{CC} = 15 \text{ V}$, $V_{BE} = 0.7 \text{ V}$. (06 Marks)

OR

- 6 a. Describe Miller effect and derive an equation for Miller input and output capacitance. (08 Marks)
- b. Calculate the overall lower 3 dB and upper 3 dB frequencies for a 3 stage amplifier having an individual $f_1 = 40$ Hz and $f_2 = 2$ MHz. (08 Marks)

Module-4

- 7 a. Derive the expression for input resistance for a voltage of series and current series feedback. (08 Marks)
- b. With a neat circuit diagram, explain FET based phase shift oscillator. (08 Marks)

OR

- 8 a. With the help of neat circuit diagram. Explain the operation of Colpitts and Hartley oscillator. Write the expression for the frequency of oscillation. (12 Marks)
- b. In a transistor Colpitts oscillator $C_1 = 1$ nF, $C_2 = 100$ nF. Find the value of L for a frequency of 100 kHz. (04 Marks)

Module-5

- 9 a. Show that the transformer coupled class A power amplifier has maximum efficiency of 50%. (08 Marks)
- b. A single transistor amplifier with transformer coupled load produces harmonic amplitudes in the output as,
 $B_0 = 1.5$ mA, $B_1 = 120$ mA, $B_2 = 10$ mA, $B_3 = 4$ mA, $B_4 = 2$ mA, $B_5 = 1$ mA
- (i) Determine the percentage total harmonic distortion.
- (ii) Assume a second identical transistor is used along with a suitable transformer to provide push pull operation. Use the above harmonic amplitudes to determine the new total harmonic distortion. (08 Marks)

OR

- 10 a. Explain with the block diagram, the basic types of voltage regulation circuit. (08 Marks)
- b. Explain the operation of complementary symmetry class B amplifier. (08 Marks)

* * * * *