

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Digital Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing
ONE full question from each module.

Module-1

- 1 a. Define combinational logic. Design a combinational circuit which takes two, 2 bit binary numbers as its input and generates an output equal to 1, when the sum of the two numbers is even. (10 Marks)
- b. Simplify using Karnaugh map. Write the Boolean equation and realize using NAND gates.
 $D = f(w, x, y, z) = \sum m(0, 2, 4, 6, 8) + \sum d(10, 11, 12, 13, 14, 15)$. (06 Marks)

OR

- 2 a. Define canonical SOP and canonical POS. Expand $f = (\bar{a} + b + c)(a + c + \bar{d})$ into canonical POS. (04 Marks)
- b. Solve using Quine-McCluskey tabulation method,
 $f(a, b, c, d) = \sum m(0, 1, 4, 5, 9, 10, 12, 14, 15) + \sum \phi(2, 8, 13)$
Obtain the minimal form of the given function. Verify the result using k-map. (12 Marks)

Module-2

- 3 a. Define decoder. Implement full subtractor using a decodes. Write the truth table. (08 Marks)
- b. Compare ripple carry adder and look ahead carry adder. Explain the circuit and operation of a 4 bit binary adder with look ahead carry. (08 Marks)

OR

- 4 a. Design and implement one bit comparator. (04 Marks)
- b. Implement the multiple functions :
 $f_1(a, b, c, d) = \sum(0, 4, 8, 10, 14, 15)$ and
 $f_2(a, b, c, d) = \sum(3, 7, 9, 13)$
using two 3 to 8 decoders, i.e. 74138 ICs. (06 Marks)
- c. Implement full adder circuit using 8 : 1 multiplexer. (06 Marks)

Module-3

- 5 a. What is gated SR Latch? Explain the operation of gated SR Latch, with a logic diagram, truth table and logic symbol. (08 Marks)
- b. Derive the characteristic equation of SR, JK, D and T flip-flops with the help of function tables. (08 Marks)

OR

- 6 a. Explain the operation of a switch debouncer built using SR Latch. Draw the supporting waveforms. (04 Marks)
- b. Explain 0s and 1s catching problem of Master Slave JK flip flop with waveform. Suggest the solution for this problem. (04 Marks)
- c. What is edge triggered flip flop? With a neat circuit diagram, explain the operation of positive edge triggered D flip flop, using NAND gates. (08 Marks)

Module-4

- 7 a. With the help of neat diagram, explain PISO and PIPO operation of unidirectional shift registers. (08 Marks)
 b. Design a 4 bit binary ripple 'UP' counter using negative edge triggered JK flip flop. Show the up counter execution with the help of timing diagram. (08 Marks)

OR

- 8 a. Implement a Mod 8 twisted ring counter using D flip flops. Give the counting sequence and decoding gate inputs. (06 Marks)
 b. Design a synchronous MOD-6 counter using JK flip flop for the following count sequence 0, 2, 3, 6, 5, 1 and repeat. Write the transition table, logic equations and the counter implementation diagram. (10 Marks)

Module-5

- 9 a. Compare Mealy and Moore sequential circuit models with suitable example. (04 Marks)
 b. For the logic diagram shown in Fig.Q9(b), write the state and output equations. Give the transition table and the state diagram. (12 Marks)

 


Fig.Q9(b)

OR

- 10 a. Write the basic recommended steps for the design of a clocked synchronous sequential circuit. (06 Marks)
 b. How to convert a Mealy machine to a Moore machine? (02 Marks)
 c. A sequential circuit has one input and one output. The state diagram is shown in Fig.Q10(c). Design a sequential circuit using D flip flop. (08 Marks)

 


Fig.Q10(c)
