

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC34

Third Semester B.E. Degree Examination, Dec.2019/Jan.2020 Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Express the following functions into a canonical form:
 - i) $f_1 = a + bc + bcd$
 - ii) $f_2 = a(b + c)(b + c + d)$ (08 Marks)
- b. Represent the number of days in a month for a non-leap year by a truth table, indicating the output of a invalid inputs if any by '0'. (06 Marks)
- c. Simplify the given function using K-map method
 $f(abcd) = \sum m(1, 2, 4, 11, 13, 14, 15) + d(0, 5, 7, 8, 10)$. (06 Marks)

OR

- 2 a. Find all prime implicants of the function using Quine-industry method and verify the same by K-map method. $f(abcd) = \sum m(0, 2, 3, 4, 8, 10, 12, 13, 14)$ (10 Marks)
- b. Find minimal sum and minimal product for the incomplete Boolean function using K-map
 $f(abcd) = \sum m(6, 7, 9, 10, 13) + d \sum(1, 4, 5, 11, 15)$. (10 Marks)

Module-2

- 3 a. Design two bit magnitude comparator. (10 Marks)
- b. Design 4:2 priority encoder with a valid output where highest priority is given to the highest bit position. (10 Marks)

OR

- 4 a. Design and realize the Boolean function using IC-74139.
 $f_1(ab) = \sum(0, 2)$, $f_2(abc) = \sum(1, 3, 5, 7)$. (05 Marks)
- b. Explain how look ahead carry adder circuit will reduce the propagation delay with the help of carry propagate and carry generate function. (08 Marks)
- c. Implement the Boolean function $f(abcd) = \sum(0, 2, 4, 5, 7, 9, 10, 14)$ using multiplexers with two 4:1 MUX with variable 'a' and 'b' are connected to their select lines in first level and one 2:1 MUX with variable 'c' connected to its select line in second level. (07 Marks)

Module-3

- 5 a. With the help of logic circuit and waveforms. Explain switch bouncing applications using SR latch. (06 Marks)
- b. Write the characteristics equation for SR, JK flip flop. (06 Marks)
- c. With neat logic diagram, and waveform. Explain the operation of master-slave J-K flip-flop. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 6 a. List the difference between combinational and sequential circuit. (06 Marks)
 b. Explain the operation of clocked SR flip-flop using NAND-gate. s (06 Marks)
 c. What is the significance of Edge triggering? Explain the working of positive edge triggered D flip-flop with their function table. (08 Marks)

Module-4

- 7 a. With neat diagram, explain the operation of universal shift register. (08 Marks)
 b. Design 3 bit binary synchronous down counter using JK Flip Flop. Write excitation table, transition table, and logic diagram. (12 Marks)

OR

- 8 a. What is register? With neat circuit diagram, explain the operation of 4-bit ring counter. (07 Marks)
 b. With logic diagram, sequence table, decoding logic. Explain the operation of mod-7 twisted ring counter. (07 Marks)
 c. Explain the working of 4 bit binary ripple counter using positive edge triggered T-flip-flop also draw timing diagram, truth table. (06 Marks)

Module-5

- 9 a. Write the difference between Moore and Mealy model with necessary block diagram. (08 Marks)
 b. Design asynchronous circuit using positive edge triggered J-K flip-flop with minimal combinational gating to generate the following sequence. 0-1-2-0: if input $X = 0$ and $0 - 2 - 1 - 0$; if input $X = 1$, provide an output which goes high to indicate the non-zero state in the 0-1-2-0 sequence. Is this a mealy machine? (12 Marks)

OR

- 10 a. Design a cyclic mod-8 synchronous binary counter using JK flip-flop. (10 Marks)
 b. Analyze the given sequential circuit show in Fig.Q.10(b) and obtain.
 i) Flip-flop Input and Output Equation
 ii) Transition Equation
 iii) Transition Table (N)
 iv) State Table
 v) State Diagram.

 


Fig.Q.10(b)

(10 Marks)
