

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC34

Third Semester B.E. Degree Examination, Jan./Feb. 2021 Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define the following:
- Combinational circuit
 - Sequential circuit
 - Canonical SOP
 - Canonical POS
 - Prime Implicant
 - Essential prime implicant. (08 Marks)
- b. Express the following equations into decimal notations:
- $H = f(A, B, C) = A'BC + A'BC + ABC$
 - $T = f(a, b, c) = (a + b' + c)(a + b' + c')(a' + b' + c)$ (08 Marks)
- c. Write mirror image version 5-variable K-map. (04 Marks)

OR

- 2 a. Obtain minimal expression using k-map for the following incompletely specified function $F(a, b, c, d) = \sum m(0, 1, 4, 6, 7, 9, 15) + \sum d(3, 5, 11, 13)$ and draw circuit diagram using gates. (10 Marks)
- b. Simplify the following using Quine-Mcclusky method
 $s = f(w, x, y, z) = \sum(1, 3, 13, 15) + \sum d(8, 9, 10, 11)$ (10 Marks)

Module-2

- 3 a. Explain the analysis and design procedure for combinational circuit with example. (10 Marks)
- b. Implement full subtractor using 3:8 decoder and write truth table. (10 Marks)

OR

- 4 a. Design full adder using i) 8:1 MUX ii) 4:1 MUX. (10 Marks)
- b. Design 4 to 16 decoder using 3 to 8 decoder. (05 Marks)
- c. Explain look ahead carry adder and give its advantages and disadvantages. (05 Marks)

Module-3

- 5 a. What is flipflop? Discuss working principle of SR flipflop with its TT and write characteristics equations. (10 Marks)
- b. Sketch timing diagram for JK flipflop and D-flipflop. (05 Marks)
- c. Explain the operation of a switch debouncer built using SR-latch with the help of waveforms. (05 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 6 a. Explain the working of a master-slave JK flip-flop with timing diagram. Show how race around condition is eliminated. (10 Marks)
- b. Explain setup time, hold time and propagation delay for timing considerations. (05 Marks)
- c. Write characteristics equation for D and T flip-flop. (05 Marks)

Module-4

- 7 a. Explain with diagram, operation and waveforms Serial In Serial Out (SISO) shift left mode register. (10 Marks)
- b. Design BCD ripple counter using JK flip-flop. (10 Marks)

OR

- 8 a. Design an synchronous mod 5 counter using JK flip-flop and draw its timing diagram. (10 Marks)
- b. Explain ring counter with timing sequence. (05 Marks)
- c. Write a note on Johnson counter. (05 Marks)

Module-5

- 9 a. Draw and explain the block diagram of Moore and Mealy model with example and also compare both. (10 Marks)
- b. Define, present state, next state, state diagram state table and state assignment. (05 Marks)
- c. Draw and explain Moore JK-flipflop state diagram. (05 Marks)

OR

- 10 a. Analyze the synchronous sequential circuit show below in Fig.Q.10(a).

 


Fig.Q.10(a)

- b. Design a synchronous counter using JK flipflops to count the sequence 0, 1, 2, 4, 5, 6, 0, 1, 2. Use state diagram and state table. (12 Marks)
- (08 Marks)
