

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, December 2010
Electronic Instrumentation

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1
 - a. Define accuracy, precision and significant figure. (06 Marks)
 - b. A true value of voltage across a resistor is 50V, the instrument reads 49V. Calculate the absolute error and percentage error. (04 Marks)
 - c. Explain with a circuit diagram, how a basic D' Arsonval movement can be converted into a DC voltmeter. Calculate a multiplier resistance required to measure voltage range of (0 - 25)V, when $R_M = 50$ ohms, $I_g = 50 \mu A$. (10 Marks)
- 2
 - a. With a neat block diagram, explain the working principle of true RMS voltmeter. (07 Marks)
 - b. Write the advantages of a digital instrument over analog instruments. (03 Marks)
 - c. With a neat circuit diagram, explain the working of Ramp type DVM. (10 Marks)
- 3
 - a. With a neat block diagram, explain the working of digital frequency meter. (07 Marks)
 - b. Draw and explain the block diagram of CRT. (07 Marks)
 - c. Discuss the operation of electronic switch in oscilloscope. (06 Marks)
- 4
 - a. What is Barkhausen criterion? With a neat block diagram, explain the working of standard signal generator. (10 Marks)
 - b. What is sweep frequency generator? (04 Marks)
 - c. Draw and explain the block diagram of sampling oscilloscope. (06 Marks)

PART – B

- 5
 - a. What is a transducer? Explain the working of resistive position transducer. (07 Marks)
 - b. With a neat diagram, explain the principle and working of a LVDT. (09 Marks)
 - c. A resistance strain gauge with a gauge factor of 4 is connected to a steel member which is subjected to a strain of 1×10^{-6} . If the original gauge resistance is 150 ohms. Calculate the change in resistance. (04 Marks)
- 6
 - a. Derive an expression for capacitance comparison bridge at balance condition and calculate capacitance impedance at a frequency of 2 kHz, the bridge components are $C_3 = 100 \mu F$, $R_3 = 100 k\Omega$, and $R_2 = 50 k\Omega$. (09 Marks)
 - b. Derive the bridge balance equation for the Kelvin's double bridge. (07 Marks)
 - c. Explain the sources and detectors in the bridge circuits. (04 Marks)
- 7
 - a. What is bolometer? Explain RF power measurement using bolometer bridge. (07 Marks)
 - b. Give the classification of digital displays. Compare the LEDs and LCDs. (08 Marks)
 - c. Explain in brief, the working of the photovoltaic transducer. (05 Marks)
- 8

Explain the following:

 - a. Piezo-electric transducer
 - b. Signal conditioning circuits
 - c. Photo transistor
 - d. Wagner earth connection

* * * * *

(20 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

