

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, December 2011
Electronic Instrumentation

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting
at least TWO questions from each part.**

PART – A

- 1 a. Explain the following in brief :
i) Gross errors ; ii) Relative errors ; iii) Accuracy ; iv) Resolution. (08 Marks)
- b. Explain the working of a true RMS voltmeter with the help of a suitable block diagram. (08 Marks)
- c. Define sensitivity. Determine the value of the multiplier resistance on the 50V range of a dc voltmeter that uses a 250 μ A meter movement with an internal resistance of 100 Ω . (04 Marks)
- 2 a. Explain the ramp type digital voltmeter with the help of a block diagram. (10 Marks)
- b. With block diagram, explain the principle and operation of digital frequency meter. (10 Marks)
- 3 a. Explain the CRT features briefly. (05 Marks)
- b. Draw the basic block diagram of an oscilloscope. Explain the functions of each block. (10 Marks)
- c. Describe the following modes of operation available in a dual trace oscilloscope :
i) ALTERNATE mode ; ii) CHOP mode. (05 Marks)
- 4 a. Explain why time delay is necessary in oscilloscopes. (04 Marks)
- b. Explain the principle and operation of sampling oscilloscope with relevant block diagrams. (08 Marks)
- c. Explain the operation of digital storage oscilloscope with the help of a block diagram. Mention the advantages. (08 Marks)

PART – B

- 5 a. With block diagram, explain conventional standard signal generator. Mention the applications. (10 Marks)
- b. Explain the operation of a function generator with the help of a block diagram. (10 Marks)
- 6 a. Explain the Wheatstone bridge and derive the balance equation for Wheatstone bridge. Mention the limitations. (08 Marks)
- b. Find the equivalent parallel resistance and capacitance that causes a wein bridge to null with the following component values :
 $R_1 = 3.1 \text{ k}\Omega$, $C_1 = 5.2 \mu\text{F}$, $R_2 = 25 \text{ k}\Omega$, $f = 2.5 \text{ kHz}$ and $R_4 = 100 \text{ k}\Omega$. (06 Marks)
- c. Write a note on Wagner's earth connection. (06 Marks)
- 7 a. What are the factors to be considered for the selection of better transducer? Explain. (08 Marks)
- b. Explain the construction, principle and operation of LVDT. (12 Marks)
- 8 a. Explain piezo electric transducer, with circuit diagram. (08 Marks)
- b. Compare LED and LCD types of displays. (06 Marks)
- c. Write a short note on signal conditioning system. (06 Marks)

* * * * *

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.