

USN

--	--	--	--	--	--	--	--	--	--

10IT35

Third Semester B.E. Degree Examination, January 2013
Electronic Instrumentation

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting
at least TWO questions from each part.**

PART – A

- 1
 - a. Discuss briefly the different types of static errors of a measuring instrument. (06 Marks)
 - b. Calculate the value of the multiplier resistance on the 100 V range of a dc voltmeter that uses a 100 mA meter movement with an internal resistance of 100 Ω . (06 Marks)
 - c. Explain the principle and operation of a true rms responding voltmeter with the help of a suitable block diagram. (08 Marks)
- 2
 - a. List the advantages of digital instruments over analog instruments. (04 Marks)
 - b. Explain with the help of a neat diagram the working of a digital frequency meter. (07 Marks)
 - c. A 3½ digit voltmeter is used for measuring voltage,
 - i) Find the resolution of the instrument.
 - ii) How would be a reading 15.53 be displayed on 100 V range? (04 Marks)
 - d. Discuss briefly the general specifications of a digital voltmeter. (05 Marks)
- 3
 - a. Draw the basic block diagram of an oscilloscope and explain the functions of each block. (08 Marks)
 - b. Explain the functions of various controls on the front panel of a CRO. (04 Marks)
 - c. Write an explanatory note on dual beam CRO with a block diagram. (08 Marks)
- 4
 - a. Explain the operation of a sampling oscilloscope with a block diagram. Mention the advantage of a sampling oscilloscope. (10 Marks)
 - b. Discuss the operation of a digital storage oscilloscope with a neat block diagram. (10 Marks)

PART – B

- 5
 - a. Explain the operation of a sweep frequency generator with the help of a suitable block diagram. Mention its applications. (08 Marks)
 - b. What is a frequency synthesizer? Explain the operation with a suitable block diagram. (08 Marks)
 - c. Write a brief note on function generator. (04 Marks)
- 6
 - a. With the help of a neat circuit diagram, explain the operation of the wien bridge. Derive the expression for the frequency. Mention the limitations of this bridge. (08 Marks)
 - b. What is meant by 'Wagner's earth connection'? Explain with a suitable diagram. (06 Marks)
 - c. A highly sensitive galvanometer can detect a current as low as 0.1 μ A. This galvanometer is used in the wheatstone bridge as a detector. The resistance of the galvanometer is negligible. Each arm of the bridge has a resistance of 1 K Ω . The input voltage applied to the bridge is 20 V. Calculate approximately the smallest change in resistance which can be detected. (06 Marks)

- 7 a. List the factors to be considered while selecting a transducer for a given application. (04 Marks)
- b. Explain the method of measuring displacement using LVDT with a suitable diagram. State the advantage and disadvantages of LVDT. (10 Marks)
- c. A 100Ω strain gage with a gage factor of 1 is affixed to a metal bar. The bar is stretched and this causes a change in resistance of 0.001Ω . Find the change in length if the original length is 10 cm. (06 Marks)
- 8 a. Describe the operation of a piezo electric transducer with a diagram. Mention its disadvantage. (06 Marks)
- b. What are the advantages of LCD displays over LED displays? (04 Marks)
- c. Explain the procedure of measuring power using a bolometer in a bridge circuit. Mention the range of power which can be measured in this method. (06 Marks)
- d. Write an explanatory note on signal conditioning. (04 Marks)

* * * * *