

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, June/July 2011
Electronic Instrumentation

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions.
selecting at least TWO questions from each part.

PART – A

- 1 a. Define the following terms as applied to an electronic instrument :
 - i) Precision
 - ii) Accuracy
 - iii) Resolution
 - iv) Significant figures. (08 Marks)
- b. Explain the multirange voltmeter using multipliers connected in series string. (06 Marks)
- c. Calculate the value of the multiplier resistance on the 50V range of a DC voltmeter that uses a 200 μ A meter movement with an internal resistance of 100 Ω . (06 Marks)

- 2 a. Explain the working of dual slope type digital voltmeter, with the help of a block diagram. (06 Marks)
- b. A 4½ digit voltmeter is used for voltage measurements
 - i) Find its resolution
 - ii) How would 12.98 V be displayed on a 10 V range?
 - iii) How would 0.6973 be displayed on 1V and 10 V ranges? (06 Marks)
- c. Explain the operation of digital meter used for time measurement, with the help of block diagram. (08 Marks)

- 3 a. Explain the operation of vertical amplifier used in cathode ray oscilloscope, with the help of block diagram. (06 Marks)
- b. With neat block diagram approach, explain the operation of dual beam cathode ray oscilloscope. (06 Marks)
- c. Explain the operation of electronic switch used in CRO using basic block diagram, and circuit diagram. (08 Marks)

- 4 a. Explain the need for a delayed-time-base oscilloscope. Draw the block diagram of a delayed time base, and explain how it operates. (10 Marks)
- b. Explain the basic operation of a digital storage oscilloscope, and discuss the relationship between sampling rate and bandwidth. (10 Marks)

PART – B

- 5 a. Explain the operation of conventional standard signal generator with the help of block diagram. (06 Marks)
- b. Explain the operation of function – generator, with the help of block diagram. (06 Marks)
- c. Explain the operation of the frequency synthesizer uses a phase – locked – loop (PLL) system, with the help of block diagram. (08 Marks)

- 6 a. Explain the operation of the Maxwell's bridge, with a neat circuit diagram. Derive an expression for unknown values of resistance and inductance. What are the limitations of Maxwell's bridge? (08 Marks)
- b. Find the equivalent parallel resistance and capacitance that causes a Wien bridge to null with the following components (values)
- $R_1 = 3.1 \text{ k}\Omega$
 $C_1 = 5.2 \mu\text{F}$
 $R_2 = 25 \text{ k}\Omega$
 $f = 2.5 \text{ kHz}$
 $R_4 = 100 \text{ k}\Omega$. (06 Marks)
- c. Write a note on Wagner's earth (ground) connection. (06 Marks)
- 7 a. Explain the operation of resistive position transducer, with neat diagram. (06 Marks)
- b. What is resistance transducer? Explain briefly with diagram. Mention the advantages and disadvantages of the resistance transducer. (08 Marks)
- c. Write a note on differential output transducers. (06 Marks)
- 8 a. Explain the operation of the photo-transistor with construction, symbol, output characteristics and relay circuit. (06 Marks)
- b. Explain the operation of the measurement of power by means of bolometer bridge, with the help of suitable circuit. (08 Marks)
- c. Write a note on light emitting diodes. (06 Marks)
