

USN

--	--	--	--	--	--	--	--	--	--

10IT35

**Third Semester B.E. Degree Examination, June/July 2013**  
**Electronic Instrumentation**

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting at least TWO questions from each part.**

**PART – A**

- 1 a. Explain with suitable example accuracy and precision. (05 Marks)  
b. A Permanent Magnet Moving Coil instrument (PMMC) with Full Scale Deflection (FSD) of  $100 \mu\text{A}$  and coil resistance is  $1 \text{ K}\Omega$  is to be connected into a voltmeter. Determine the required multiplier resistance if the voltmeter is to be measure  $50 \text{ V}$  at full scale. Also calculate the applied voltage when the instrument indicates 0.8, 0.5 and 0.2 of FSD. (08 Marks)  
c. Explain with neat circuit diagram and wave forms full wave rectifier type AC voltmeter. (07 Marks)
- 2 a. Explain basic operation of digital multimeter with neat block diagram. (07 Marks)  
b. Suppose the converter can measure a maximum of  $5 \text{ V}$ . i.e.  $5 \text{ V}$  corresponds to the maximum count of 11111111, if the test voltage is  $V_{in} = 1 \text{ V}$ . Show the steps take place in the table format in the measurement for the successive approximation type Digital Volt Meter (DVM). (06 Marks)  
c. Explain with neat block diagram Digital Frequency Meter. (07 Marks)
- 3 a. Explain sweep or time base generator with neat circuit diagram and wave forms, for a continuous sweep CRO and triggered sweep CRO. (12 Marks)  
b. Explain dual trace oscilloscope with neat block diagram. (08 Marks)
- 4 a. Discuss need for delayed sweep in digital storage oscilloscope. (04 Marks)  
b. Explain basic principle of sampling oscilloscope with neat diagram and wave forms. (06 Marks)  
c. Explain two types of storage techniques used in storage oscilloscope with neat diagram. (10 Marks)

**PART – B**

- 5 a. Explain with neat block diagram, operating principle of function generator. (08 Marks)  
b. Elaborate with neat block diagram, conventional standard signal generator. (06 Marks)  
c. Explain with neat block diagram and waveforms, frequency synthesizer in signal generators. (06 Marks)

- 6 a. Derive an expression for galvanometer current ( $I_g$ ) when the wheatstones bridge is unbalanced. (05 Marks)
- b. An unbalanced wheat stones bridge is shown in Fig. Q6 (b). Calculate current in the galvanometer. (05 Marks)

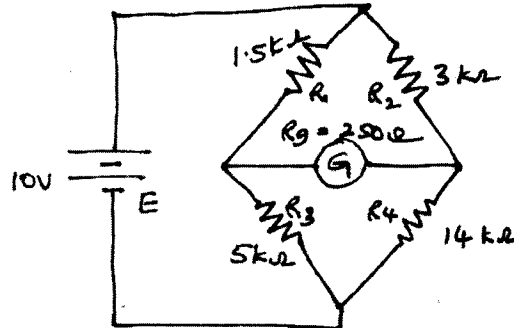


Fig. Q6 (b)

- c. Derive an expression for  $L_x$  and  $R_x$  which is a series impedance in the Maxwell's bridge. And find series equivalent unknown impedance, when  $C_1 = 0.01 \mu\text{f}$ ,  $R_1 = 470 \text{ K}\Omega$ ,  $R_2 = 5.1 \text{ K}\Omega$ ,  $R_3 = 100 \text{ K}\Omega$  (10 Marks)

- 7 a. List at least five advantages of electrical transducer. (05 Marks)
- b. A displacement transducer with a shaft stroke of 3.0 inch, is applied to the circuit as shown in Fig. Q7 (b) below. The total resistance of the potentiometer is 5 KΩ, the applied voltage  $V_t$  is 5 V. When the wiper is at 0.9 inch from B. What is the value of output voltage  $V_o$ . (05 Marks)

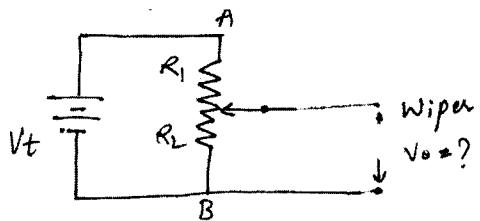


Fig. Q7 (b)

- c. Define Gauge factor. Derive expression for gauge factor of bounded resistance wire strain gauge. (10 Marks)
- 8 a. Explain photo transistor. With neat diagram and output characteristics. How is it used as a transducer? (05 Marks)
- b. List at least five classifications of digital displays. (05 Marks)
- c. List out the requirement of a dummy load. And explain measurement of power by means of a bolometer bridge. (10 Marks)

\* \* \* \* \*