

USN

--	--	--	--	--	--	--	--	--	--

10ES33

**Third Semester B.E. Degree Examination, December 2011**  
**Logic Design**

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting  
at least TWO questions from each part.**

**PART – A**

- 1 a. Expand  $f_1 = a + bc + a\bar{c}d$  into minterms and  $f_2 = a(b + c)(a + c + \bar{d})$  into maxterms. (06 Marks)
- b. Simplify  $f(a, b, c, d) = \sum m(1, 2, 4, 11, 13, 14, 15) + dc(0, 5, 7, 8, 10)$  using Karnaugh map technique. (05 Marks)
- c. Obtain a minimal SOP expression for the function  $f(a, b, c, d, e) = \sum m(3, 7, 11, 12, 13, 14, 15, 16, 18) + dc(24, 25, 26, 27, 28, 29, 30, 31)$  using Karnaugh map method. (05 Marks)
- d. Explain canonical form of Boolean equations with an example. (04 Marks)
  
- 2 a. Minimize  $f(a, b, c, d) = \pi(0, 6, 7, 8, 9, 13) + \pi dc(5, 15)$  using quine Mc cluskey method. (12 Marks)
- b. Simplify  $f(a, b, c, d) = \sum m(2, 3, 4, 5, 13, 15) + dc(8, 9, 10, 11)$  taking least significant bit as map entered variable. (08 Marks)
  
- 3 a. Design and implement a 4 bit look ahead carry adder. (14 Marks)
- b. Implement 16:1 multiplexer using 4:1 multiplexers. (06 Marks)
  
- 4 a. Design and implement a 2 BIT digital comparator. (09 Marks)
- b. Implement a full subtractor using 3 – 8 line decoder with the decoder having high outputs and active low enable thermal. (05 Marks)
- c. Implement the Boolean function  $f(a, b, c, d) = \sum m(0, 1, 5, 6, 7, 9, 10, 15)$  using multiplexer with a, b connected to select lines  $s_1, s_0$ . (06 Marks)

**PART – B**

- 5 a. Give the NAND – NAND implementation of a gated SR latch with preset and clear facilities, such that when preset = 0, the output should be 1 while clear = 0, the output be 0. Give the truth table clearly indicating gate, clear, preset and input signals and the corresponding outputs. (07 Marks)
- b. Explain the working of a pulse triggered JK master slave flip flop with a truth table. (06 Marks)
- c. Explain the functioning of positive edge triggered D – flip flop. (07 Marks)

- 6 a. Explain 4 bit universal shift register using negative edge triggered D – flip flops. (08 Marks)  
 b. Give the circuit of a 4 bit JOHNSON counter using negative edge triggered D flip flops. Draw the timing waveforms with respect to clock starting with an initial state of  $Q_3Q_2Q_1Q_0 = 0000$ . What is the modulus of this counter? (08 Marks)  
 c. What is meant by triggering of flip flops? Name the different triggering methods. (04 Marks)
- 7 a. Compare synchronous and ripple counters. (03 Marks)  
 b. Draw the circuit of a 3 BIT, asynchronous, down counter using negative edge triggered JK flip flops and draw the timing waveforms. (05 Marks)  
 c. Design and implement a synchronous counter to count the sequence 0 – 3 – 2 – 5 – 1 – 0 using negative edge triggered JK flip flops. (12 Marks)
- 8 a. Explain Mealy and Moore machine models. (06 Marks)  
 b. Construct the excitation table, transition table, state table and state diagram for the Moore circuit shown in Fig.Q.8(b). (14 Marks)

 


Fig.Q.8(b)

\*\*\*\*\*