

USN

--	--	--	--	--	--	--	--	--	--

10ES33

### Third Semester B.E. Degree Examination, December 2012

### Logic Design

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting at least TWO questions from each part.**

#### PART – A

- 1 a. Define canonical Minterm form and canonical Maxterm form. (05 Marks)
- b. Design a three-input, one output minimal two-level gate combinational circuit which has an output equal to 1 when majority of its inputs are at logic 1 and has an output equal to 0 when majority of its inputs are at logic 0. (05 Marks)
- c. Minimize the following multiple output functions using K-MAP:  
 $f_1 = \sum m(0, 2, 6, 10, 11, 12, 13) + d(3, 4, 5, 14, 15)$   
 $f_2 = \sum m(1, 2, 6, 7, 8, 13, 14, 15) + d(3, 5, 12)$  (10 Marks)
- 2 a. Use a K-Map to simplify that following functions:  
 i)  $f(A, B, C, D) = (A + B + \bar{C})(\bar{B} + \bar{D})(\bar{A} + C)(B + C)$   
 ii)  $f(A, B, C, D) = \pi(1, 2, 4, 5, 7, 8, 10, 11, 13, 14)$  (10 Marks)
- b. Find all the prime implicants of the function  
 $f(a, b, c, d) = \sum(7, 9, 12, 13, 14, 15) + \sum d(4, 11)$   
 Using Quine Mc Clusky algorithm. (10 Marks)
- 3 a. Reduce the given function using MEV technique:  
 i)  $f = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}D + ABCE + ABC\bar{E} + d(\bar{A}\bar{B}CD + \bar{A}\bar{B}CE)$   
 ii)  $f = m_0 + m_1F + m_2 + m_4F + m_6(E + \bar{E}) + m_7F + m_{10}E$   
 $+ m_{12} + m_{15}F + d(m_5F + m_9\bar{F} + m_{11}\bar{E} + m_8E)$  (10 Marks)
- b. Write the condensed truth table for a 4 to 2 line priority encoder with a valid output where the highest priority is given to the highest bit position or input with highest index and obtain the minimal sum expressions for the outputs. (06 Marks)
- c. Describe general working principle of decoder. (04 Marks)
- 4 a. Explain the working principle of four-bit parallel fast look ahead carry adder. (10 Marks)
- b. Design a comparator to check if two n-bit numbers are equal. Configure this using cascaded stages of 1-bit comparators. (10 Marks)

#### PART – B

- 5 a. With a neat diagram, explain the working of Master-Slave JK flip-flop along with waveforms. (10 Marks)
- b. Explain switch debouncer using SR latch with waveforms. (10 Marks)
- 6 a. Explain universal shift register with the help of logic diagram, mode control table. (10 Marks)
- b. Design and implement a divide-by-10 asynchronous counter using T FFS. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 7 a. Design and implement a synchronous BCD counter using J-K FFS. (10 Marks)  
 b. A sequential circuit has one input and one output state diagram is as shown in Fig.Q7(b). Design the sequential circuit with J-K flip-flop.

 


Fig.Q7(b)

(10 Marks)

- 8 a. Design a sequence detector for the following sequence 1, 0, 1, 1, 1 with overlap. Write the state diagram and logic diagram. (10 Marks)  
 b. A sequential circuit has two flip-flops A and B, two inputs x and y, and an output z. The flip-flop input functions and the circuit output functions are as follows:

$$J_A = xB + \bar{y}\bar{B}; \quad K_A = x\bar{y}\bar{B}$$

$$J_B = x\bar{A}; \quad K_B = x\bar{y} + A$$

$$z = xyA + \bar{x}\bar{y}\bar{B}$$

Obtain the logic diagram, state table and state equations, also state diagram. (10 Marks)

\*\*\*\*\*