

--	--	--	--	--	--	--	--	--	--

**Third Semester B.E. Degree Examination, Dec. 2013/Jan. 2014**  
**Logic Design**

Time: 3 hrs.

Max. Marks: 100

**Note: Answer FIVE full questions, selecting  
atleast TWO questions from each part.**

**PART – A**

- 1 a. Two motors  $M_1$  and  $M_2$  are controlled by three sensors  $S_3$ ,  $S_2$  and  $S_1$ . One motor  $M_2$  is to run any time all three sensors are ON(true). The other motor is to run whenever sensors  $S_2$  or  $S_1$ , but not both are ON and  $S_3$  is OFF. For all sensor combinations where  $M_1$  is ON,  $M_2$  is to be OFF, except when all are OFF and then both sensors must be OFF. Generate truth table, and write the Boolean equations for both outputs. Also implement using logic gates. (08 Marks)
- b. Convert the following equations in to their canonical Boolean forms :  
 $X(\text{SOP}) = a'b + bc$   
 $Y(\text{POS}) = (a' + b)(b + c')$ . (06 Marks)
- c. Simplify the following Boolean equation using Karnaugh map and implement using logic gates.  $f(a, b, c, d) = \Sigma_m(0, 5, 8, 15) + dc(2, 7, 9, 10, 13)$ . (06 Marks)
- 2 a. Minimize the following Boolean equation using Quine – McClustey method  
 $f(a, b, c, d) = \Sigma_m(2, 3, 4, 6, 10, 12, 14)$ . (12 Marks)
- b. Simplify the following Boolean equation using VEM method.  
 $f(w, x, y, z) = \Sigma_m(1, 5, 8, 9, 12, 13, 14)$ . (08 Marks)
- 3 a. Realize a 2 : 4 decoder using logic gates. Also write the truth-table. (08 Marks)
- b. Implement the following Boolean functions using 3 : 8 decoder :  
 $f_1(a, b, c) = \Sigma_m(0, 1, 3, 5, 7)$   
 $f_2(a, b, c) = \Sigma_m(1, 2, 4, 6)$ . (06 Marks)
- c. Design and implement an Octal – to – Binary encoder. (06 Marks)
- 4 a. Realize the following Boolean function using 4 : 1 MUX  
 $f(a, b, c) = \Sigma_m(0, 1, 5, 6, 7)$ . (08 Marks)
- b. Design a full adder circuit using only NAND gates. (06 Marks)
- c. Realize a 1-bit comparator using logic gates. Write the truth table. (06 Marks)

**PART – B**

- 5 a. With a neat logic diagram and truth – table, explain the operation of SR – Latch. Discuss how SR latch can be used as a switch debouncer. (12 Marks)
- b. Discuss “Race – Around” condition. Explain how this problem can be overcome using Master – slave JK flip-flop. (08 Marks)
- 6 a. With function table and logic diagram, explain the following shift – register operations :  
i) SISO (right – shift only)      ii) PIPO. (08 Marks)
- b. Explain Johnson counter, with circuit diagram and truth – table. (06 Marks)
- c. Design a mod – 6 synchronous counter using JK flip – flops. (06 Marks)

- 7 a. Analyze the synchronous sequential circuit shown in Fig. Q7(a) below. (14 Marks)

 


Fig. Q7(a)

- b. Explain Moore and Mealy models for clocked synchronous sequential circuits. (06 Marks)
- 8 a. Design a synchronous counter for 4 → 6 → 7 → 3 → 1 → 4 - - - . Avoid lockout condition. Use JK flip – flops. (10 Marks)
- b. Obtain the transition table for the given state diagram and design the sequential network using JK flip – flops. (10 Marks)

 


Fig. Q8(b)

\*\*\*\*\*